

- (f) Input referred noise spectral density-identify $1/f$ noise corner. Show relative contributions from different devices at 10 MHz.
- (g) Input referred offset (For this, ignore current factor mismatch; Calculate σ_{VT} from the sizes, and use g_m values from the operating point; You can assume $g_m \gg g_{ds}$)
- (h) Power consumption
- (i) Show a schematic with all sizes and operating points (g_m , g_{ds} , $V_{GS}-V_T$, I_D) of all transistors and the node voltages.

Do not use an ideal current source in the tail. You can use one ideal reference current source of $1/10^{\text{th}}$ the tail current for bias generation. Design the bias generator block that generates bias currents and voltages required in the opamp.

Try to determine as many parameters as possible from the specifications and choose sensible starting points for the others. You can assume a gate overdrive of 200 mV in your initial calculations.

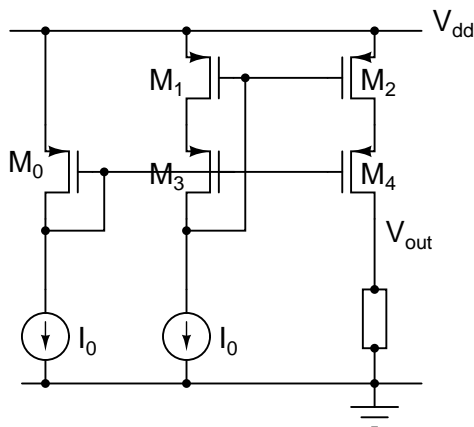


Figure 2: Cascode current source

3. Fig. 2 shows a cascode current source $M_{2,4}$ biased from $M_{0,1,3}$. M_1 and M_3 have an aspect ratio W/L . Determine the sizes of $M_{0,2,4}$ so that the load current is nI_0 and the output compliance (of V_{out}) is maximized.
4. Fig. 3 shows a common drain amplifier. Evaluate the small signal gain v_o/v_s and the output resistance

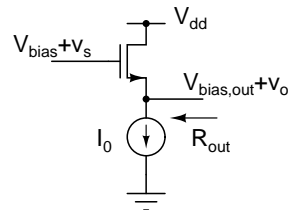


Figure 3: Common drain amplifier

R_{out} including body effect (i.e. model the transistor using g_m and g_{mb} assume $g_{ds} = 0$).

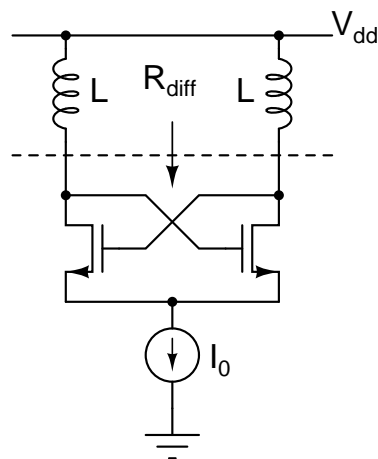


Figure 4:

5. Calculate the current flowing in each transistor in Fig. 4 in the quiescent condition. Calculate the small signal differential resistance R_{out} looking into the drains of the two transistors.

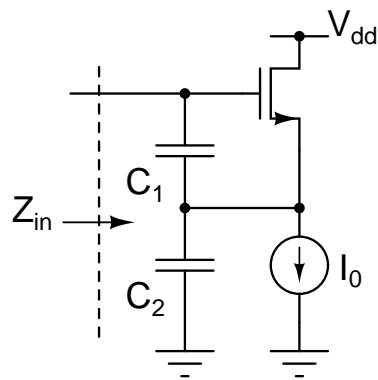


Figure 5:

6. Calculate the input impedance Z_{in} in Fig. 5. Is there

anything special about it? Model the transistor using only its g_m .

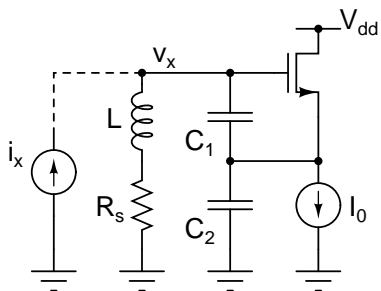


Figure 6:

- Calculate the small signal impedance v_x/i_x . What is the condition for this to be infinity? Model the transistor using only its g_m .