


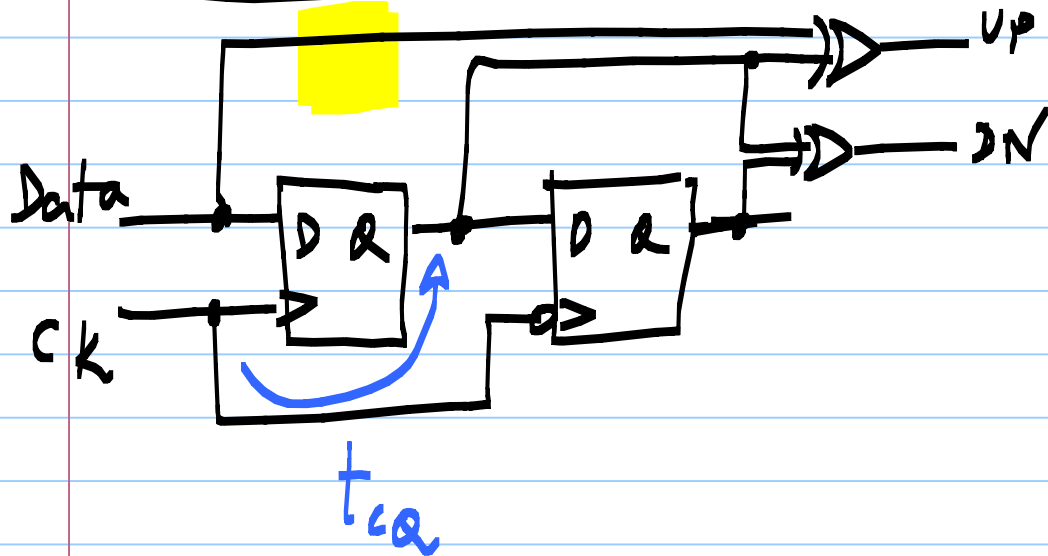
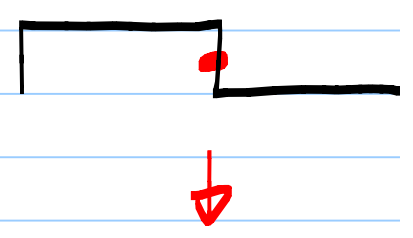
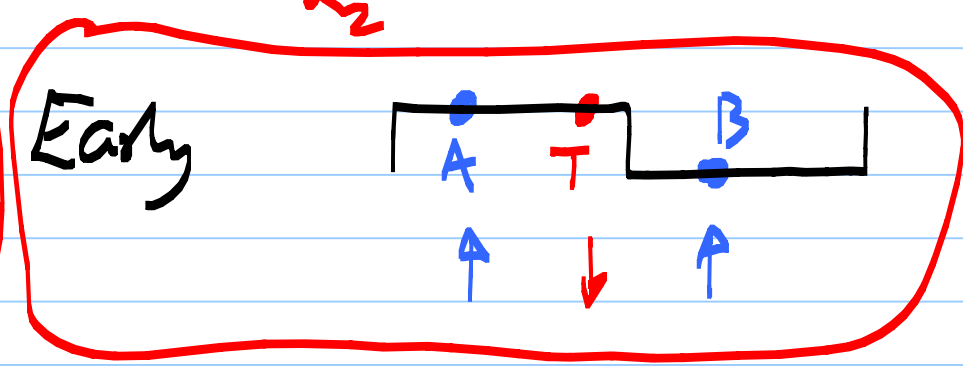
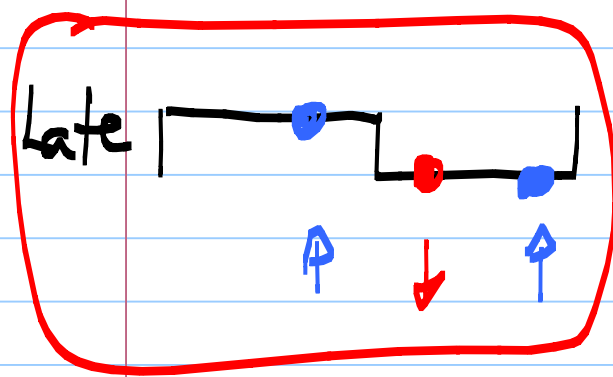
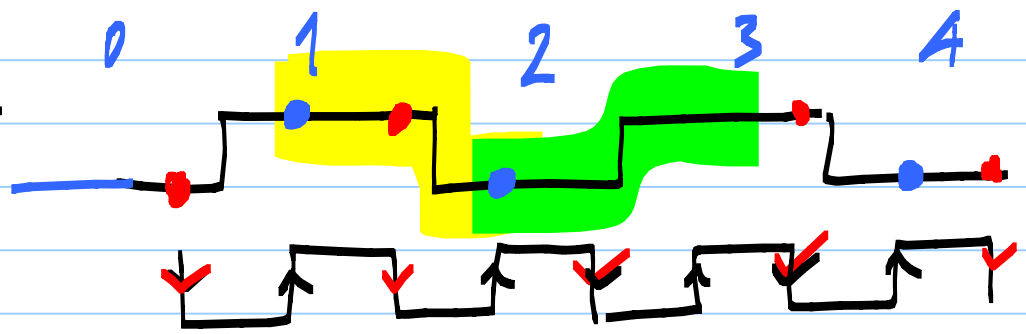
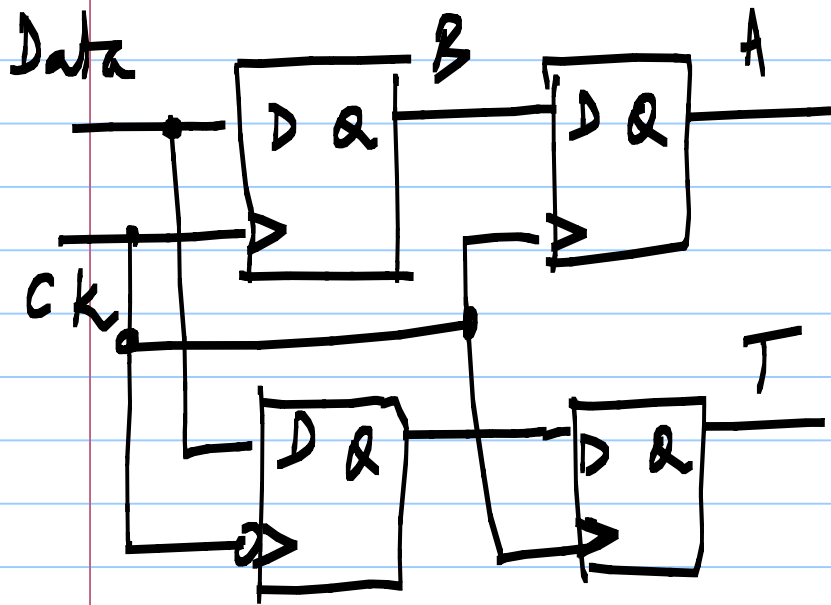
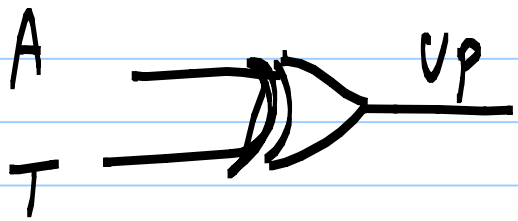


Linear phase detector

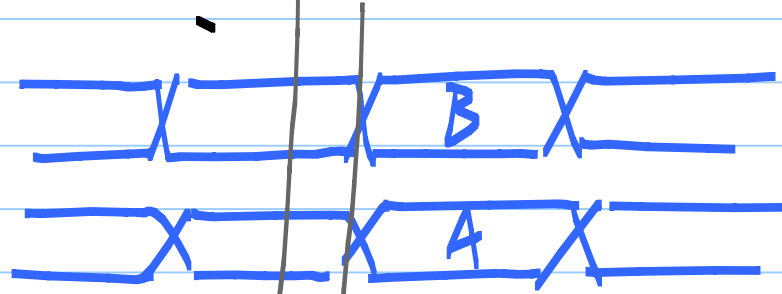


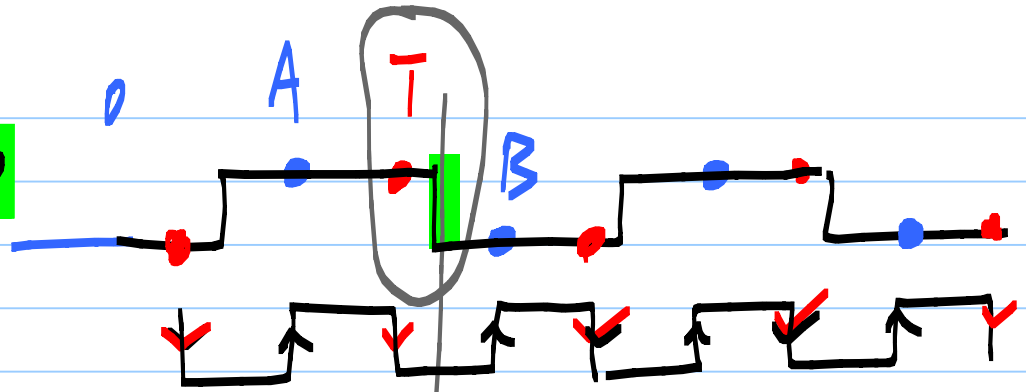

Data

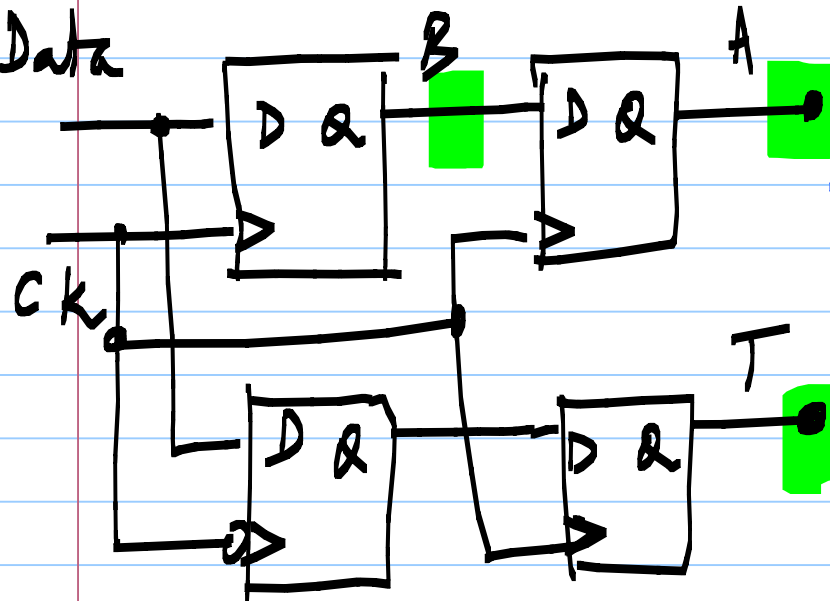


Late

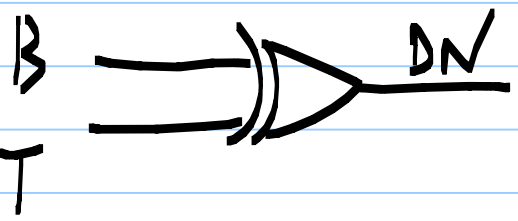

Early
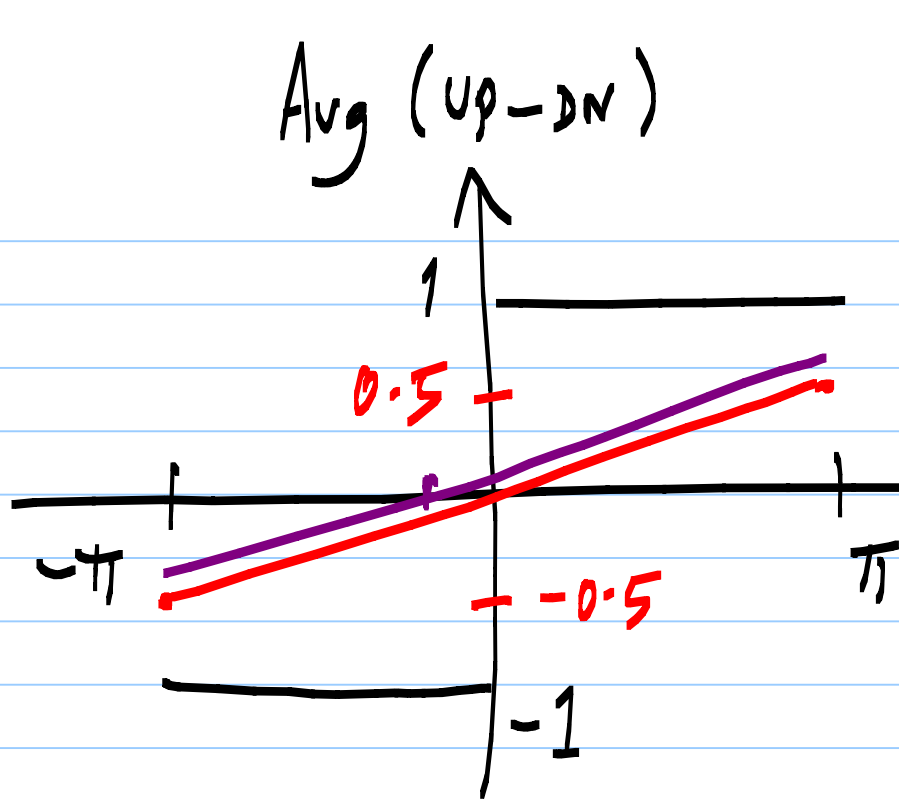
$$\text{Avg}(UP-DN) \text{ vs } \phi_D - \phi_{ck}$$



Binary phase detector
 Alexander phase detector
 Bang-Bang phase detector

$\phi_D - \phi_K$

Binary phase detector

- + No phase offset due to t_{ca}
- + Can be implemented at lower speed after digitization
- + Pulse width (up, dn) $\geq T_s$
- Bangbang jitter

Linear phase detector

- Phase offset due to t_{ca}
- Pulse width (up, dn) $= T_s/2$

