
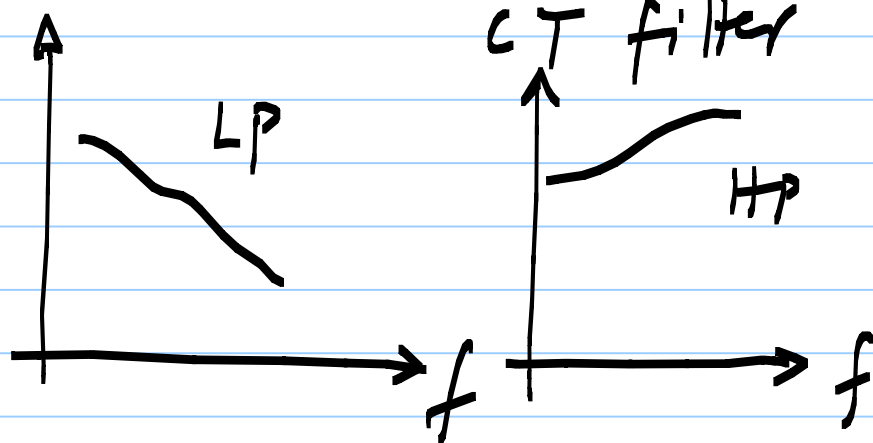


Equalization: Reduce ISI


CT equalization

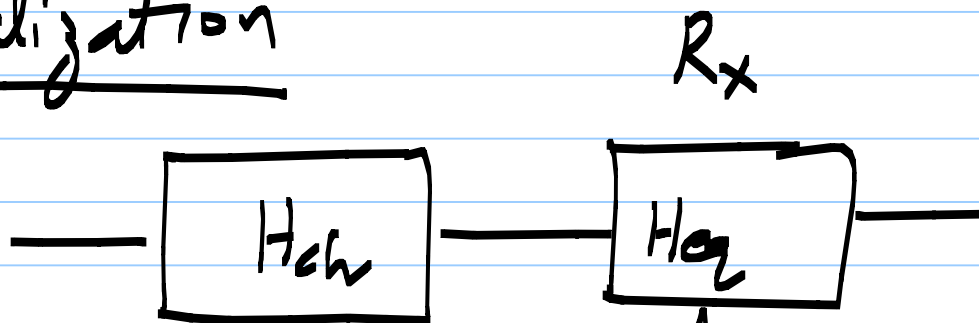


$$\frac{1 + \text{[redacted]}}{(1 + s/p_1) \underbrace{(1 + s/p_2)}}_{CT \text{ filter}}$$

Alternating data

f_0

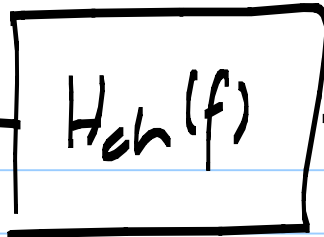


R_x CTLE: Independent of clock recovery

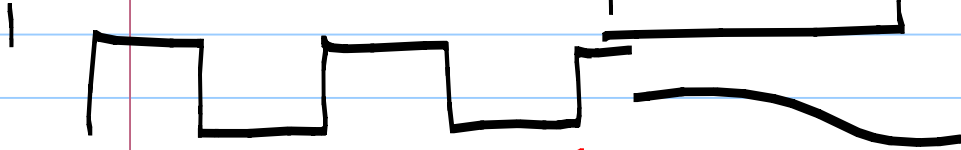

periodic @ $0.5f_0$


$0.5f_0$ and odd harmonics


$|H_{ch}(f)|$

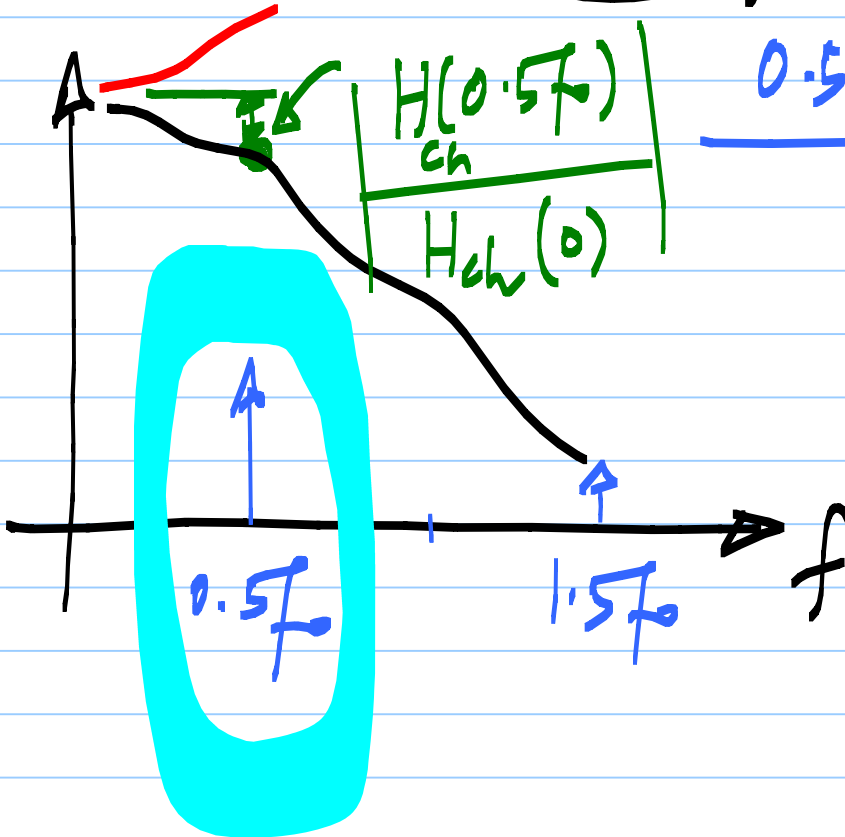


$H_{ch}(0.5f_0)$

\sim loss to be compensated at $0.5f_0$

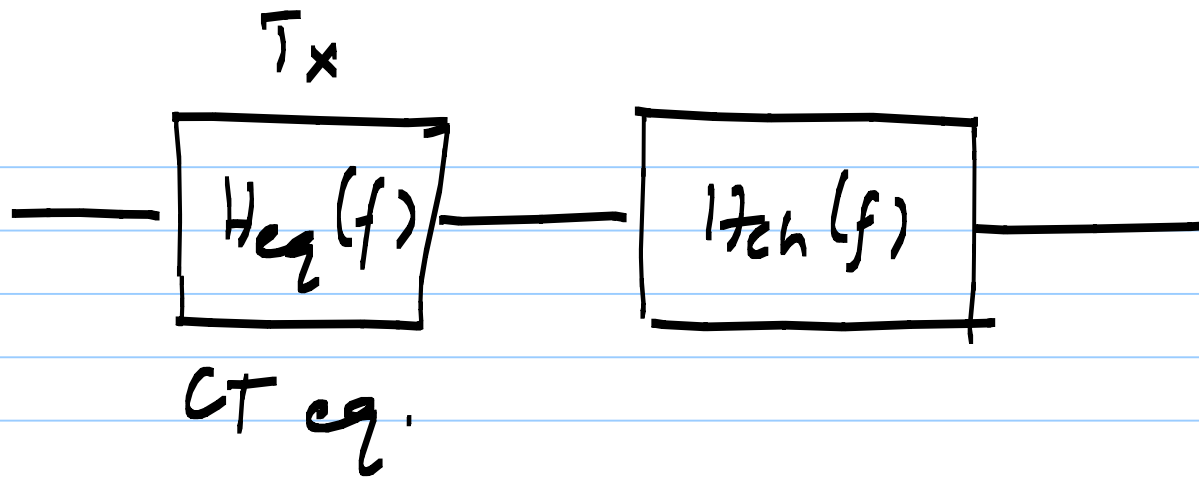

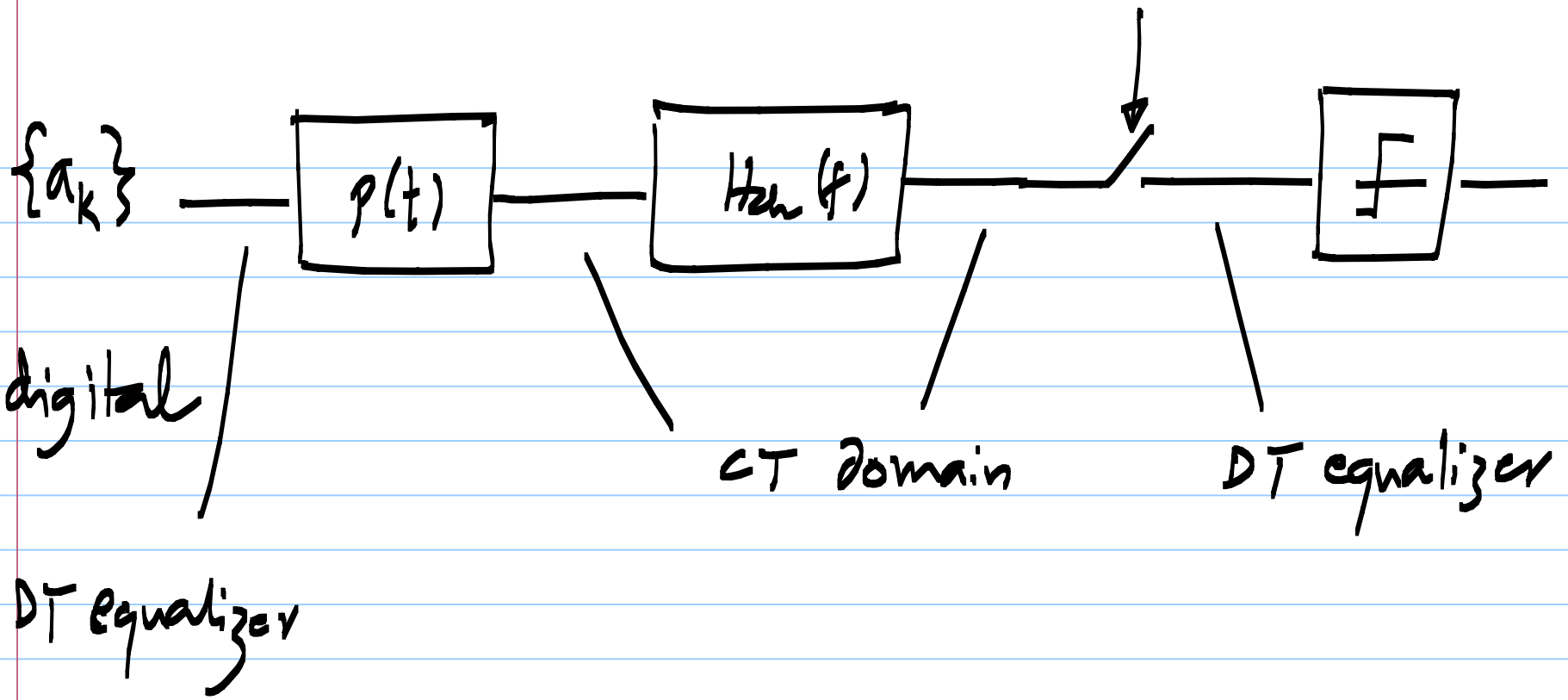

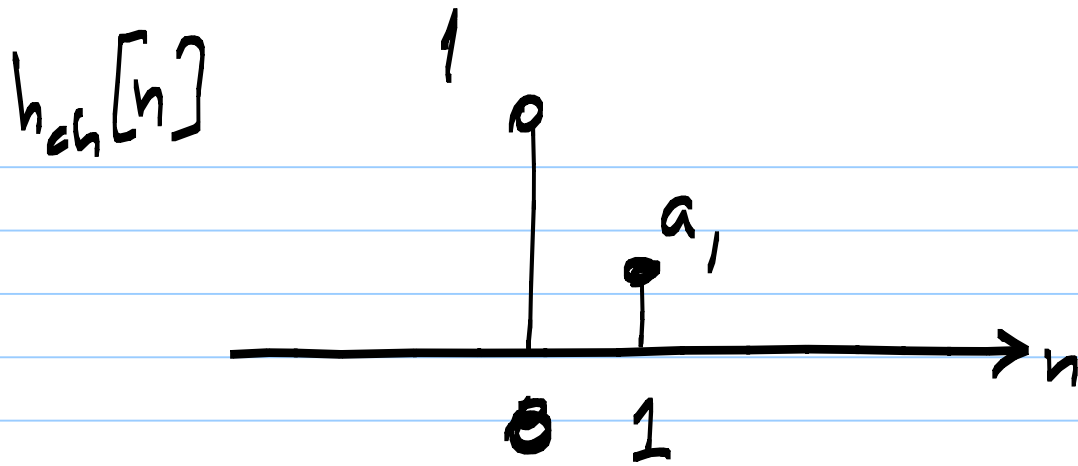


$$H_{ch}(z) = 1 + a_1 z^{-1}$$

$$H_{ch}(z) \cdot H_{eq}(z) = 1$$

$$H_{eq}(z) = \frac{1}{1 + a_1 z^{-1}}$$

IIR

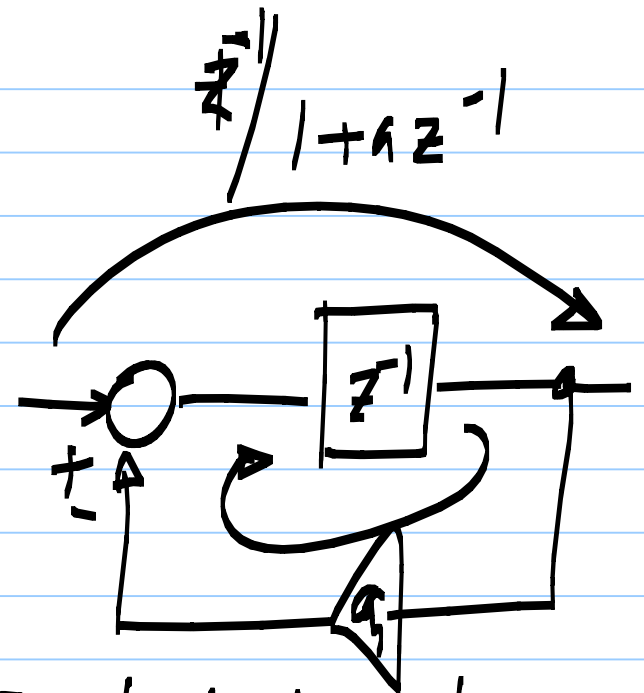


Feedback has to arrive within 1 cycle.

$$H_{ch}(z) \cdot H_{eq}(z) \approx 1$$

$$H_{eq} = \frac{1}{1 + a_1 z^{-1}} = 1 - a_1 z^{-1} + \dots$$

$$H_{eq}(z) = 1 - a_1 z^{-1}$$
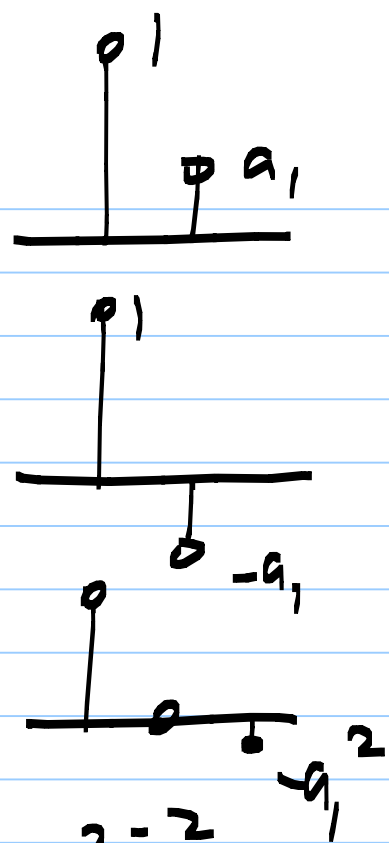
$$H_{ch} \cdot H_{eq} = (1 + a_1 z^{-1})(1 - a_1 z^{-1}) = 1 - a_1^2 z^{-2}$$






DT equalization:

* FIR realization preferred

— Difficult to close the fb loop @
high frequencies

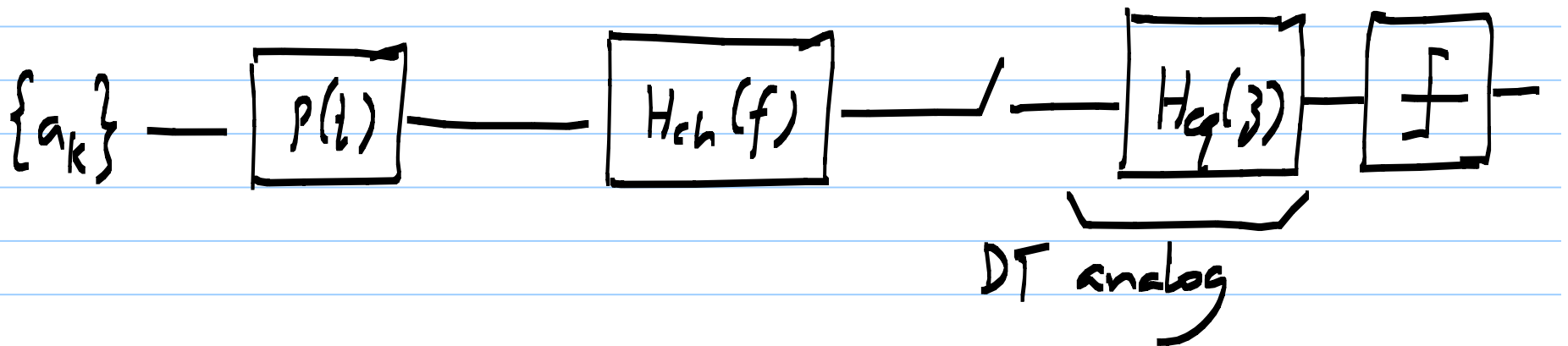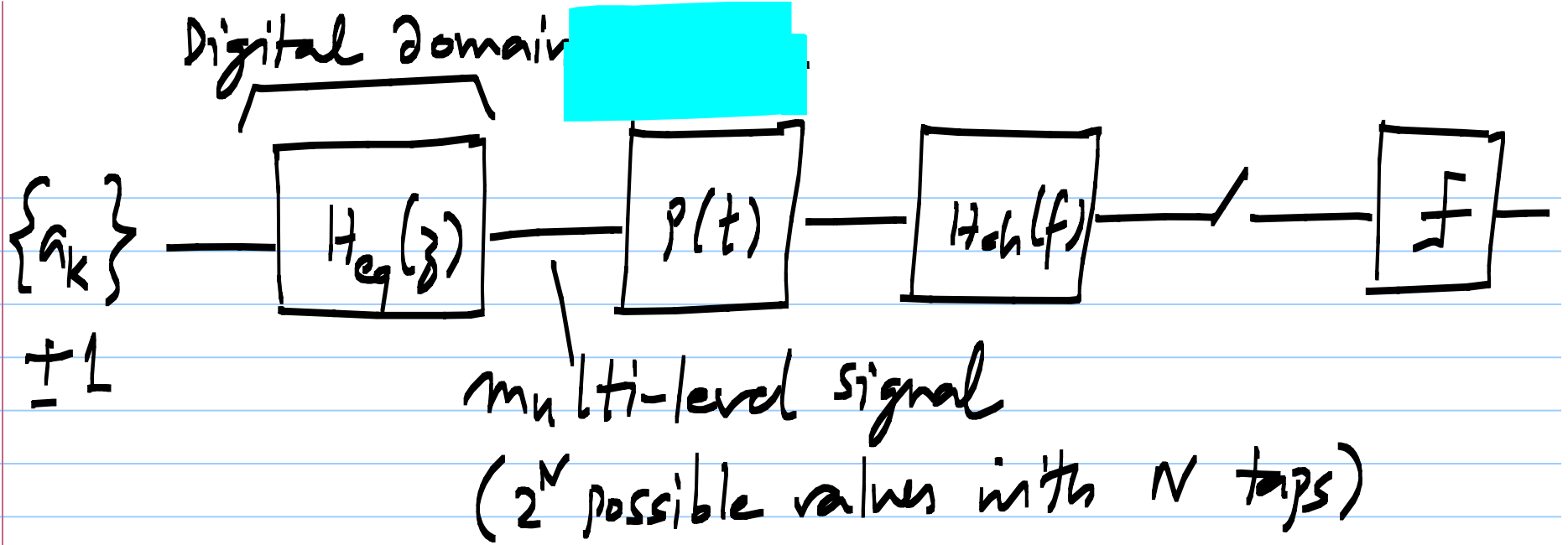* Make the combined impulse response
close to an impulse





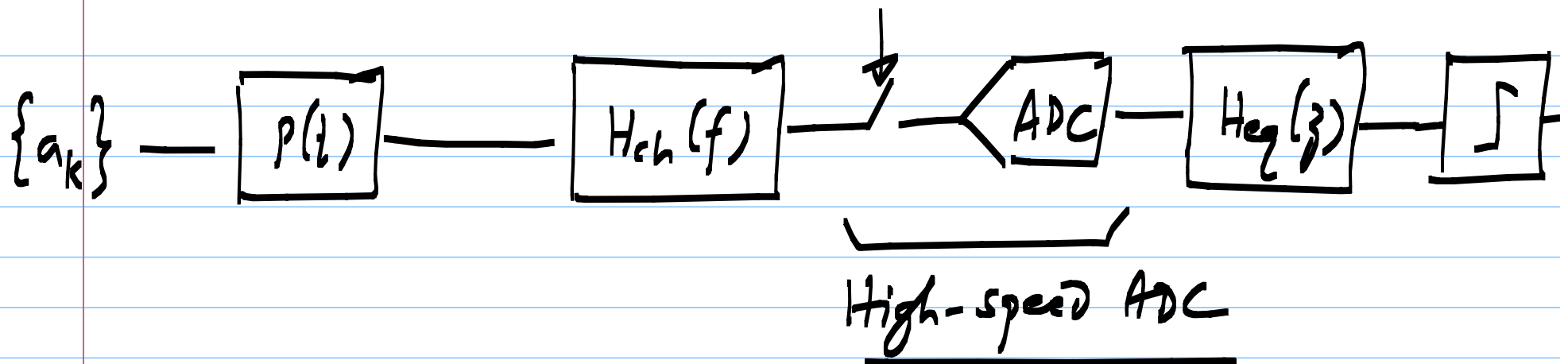


Semi-digital Tx equalizer


FIR:

Input: digital

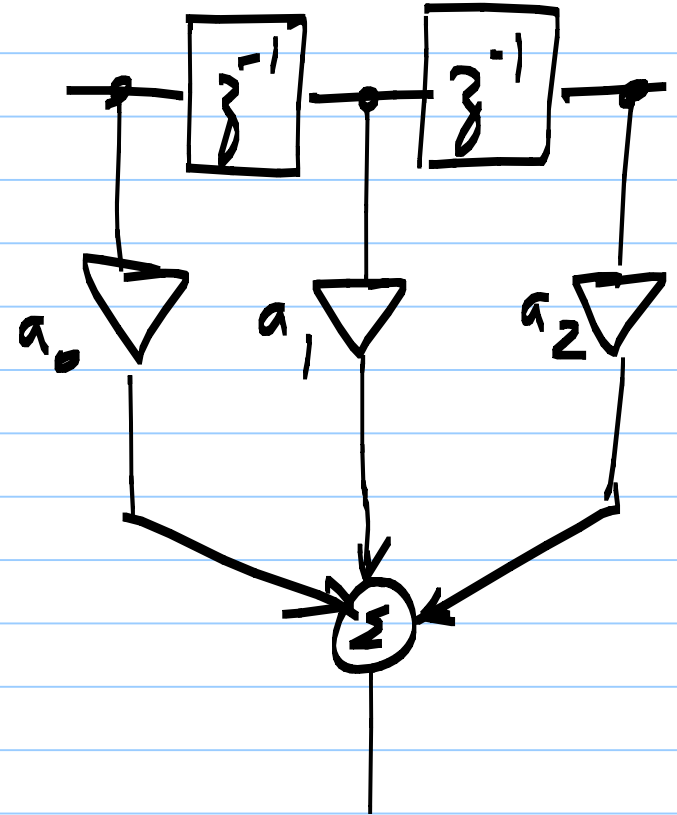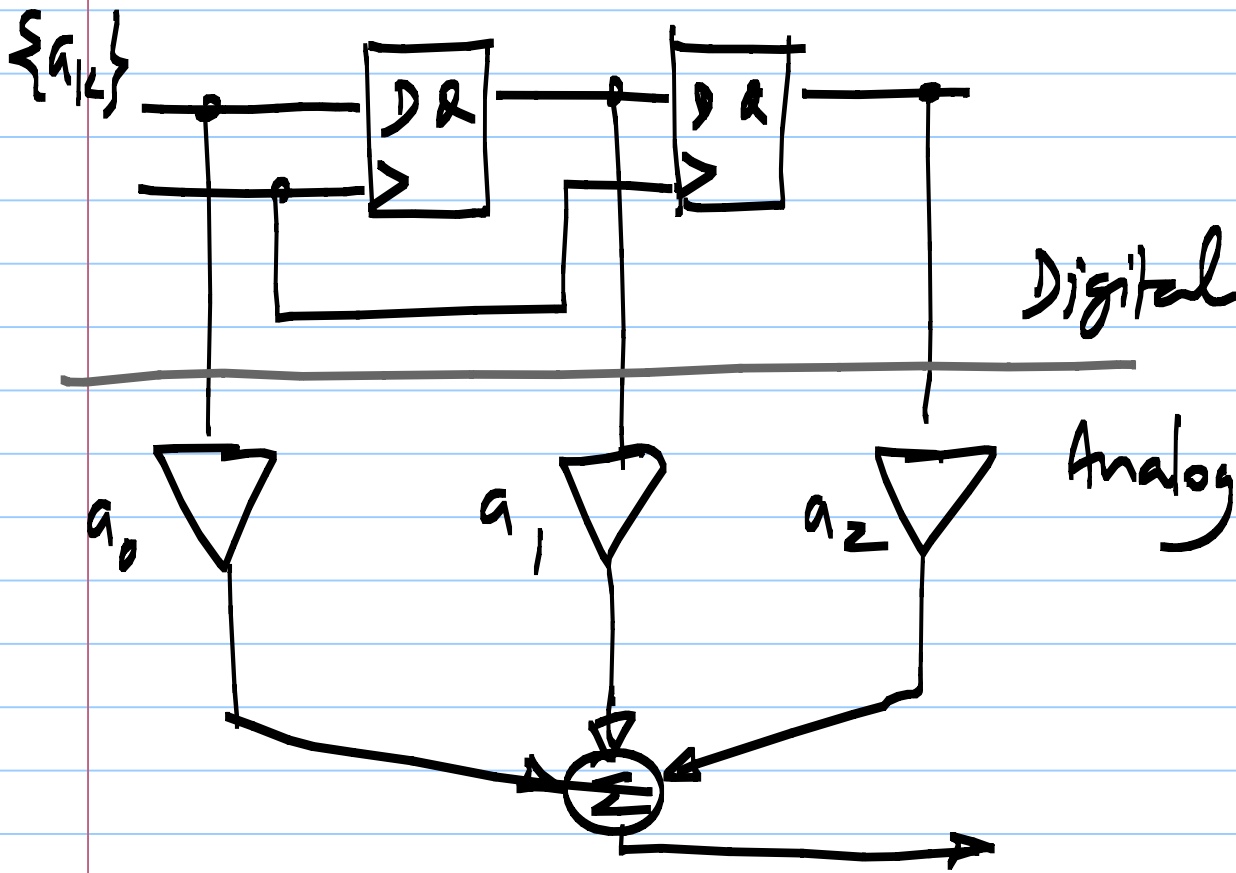

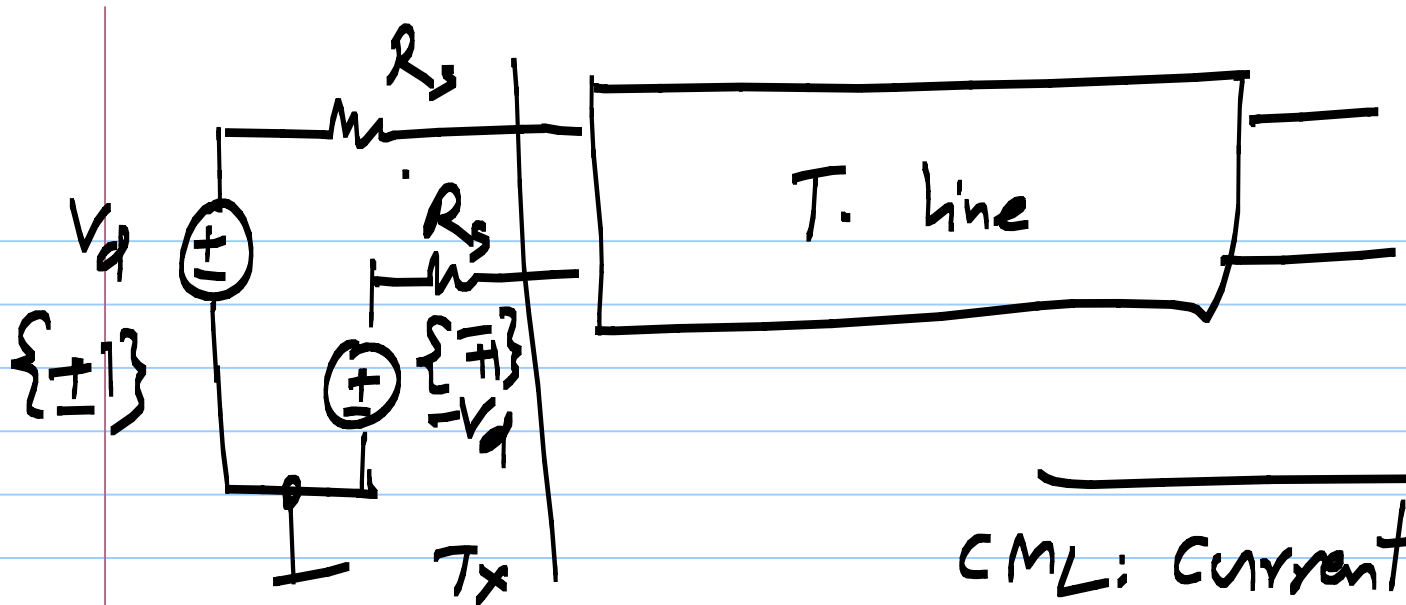

CML: current-mode logic

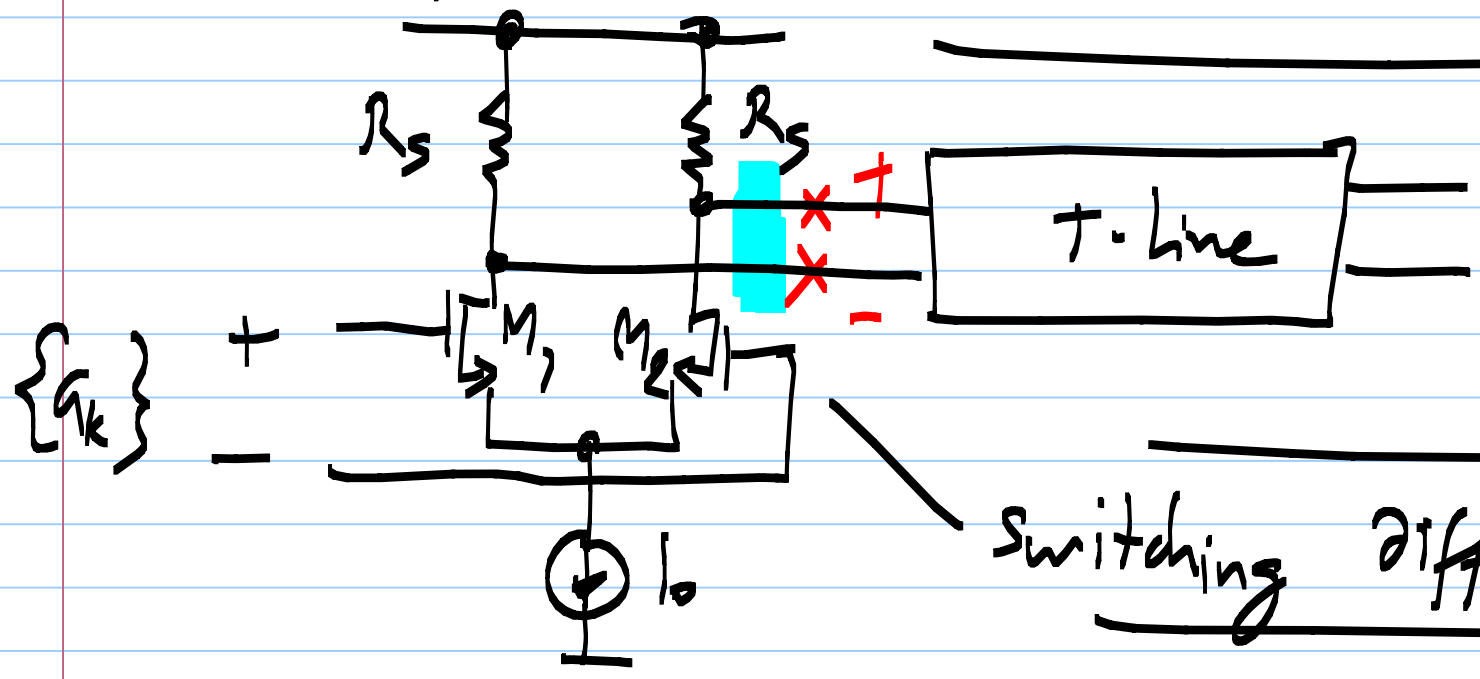


switching diff. pair


$a_1 z + a_0 + a_2 z^{-1}$
 PRECURSOR CURSOR

$+1 T_x$
 V_{DD}


$V_{DD} - I_0 R_S$

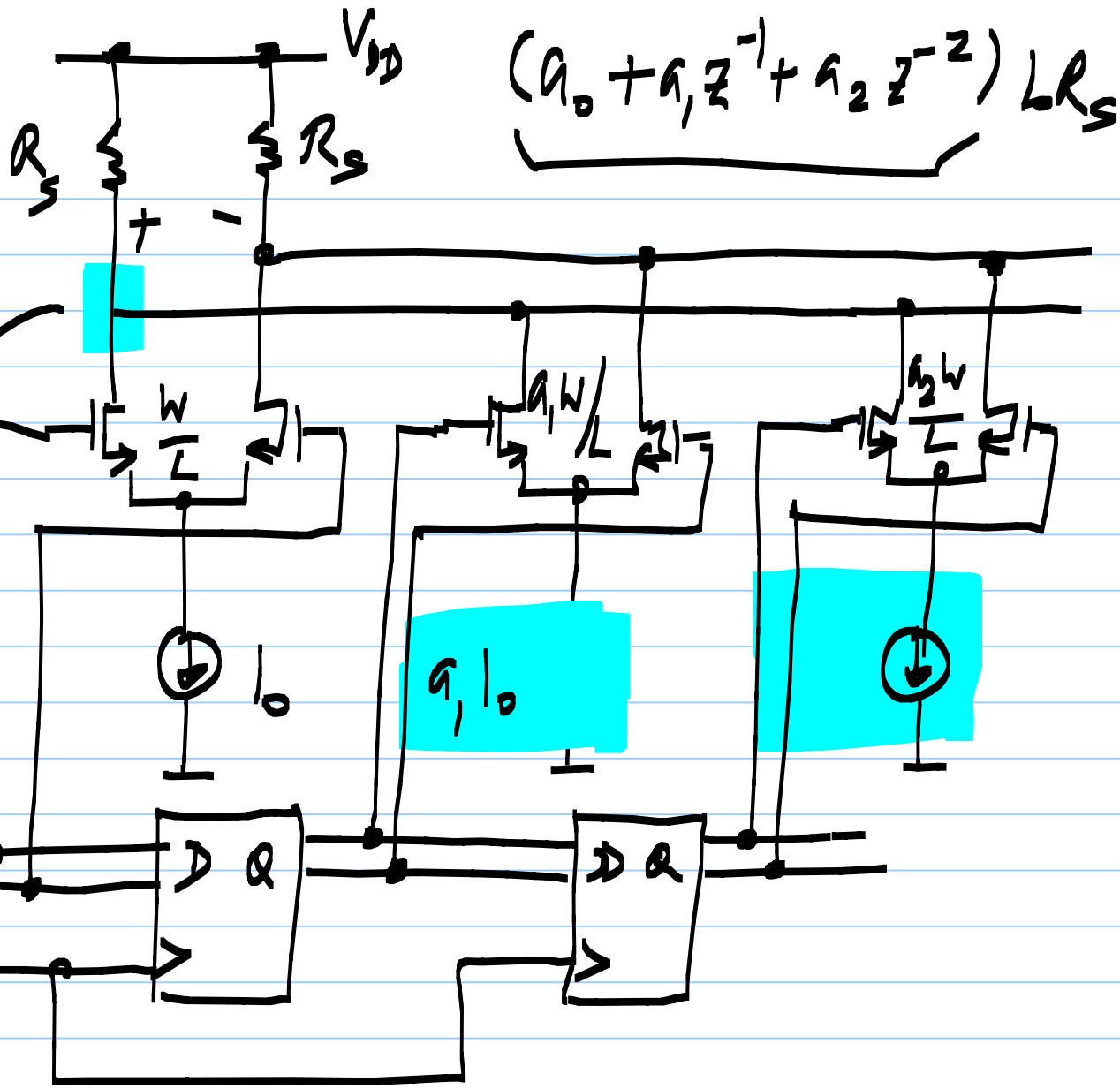$V_{DD} - \frac{I_0 R_S}{2} (1 + a_1 + a_2)$





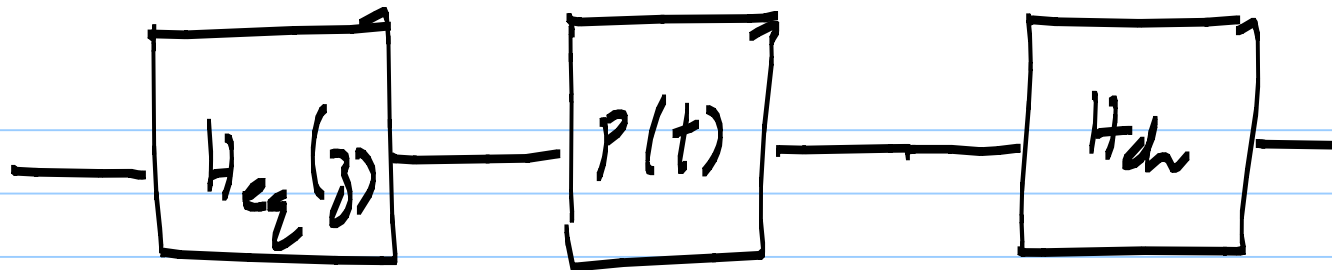


$$h_{ch}[n] = \begin{matrix} \bullet & \circ \\ | & | \\ \hline 1 & a_1 \end{matrix}$$

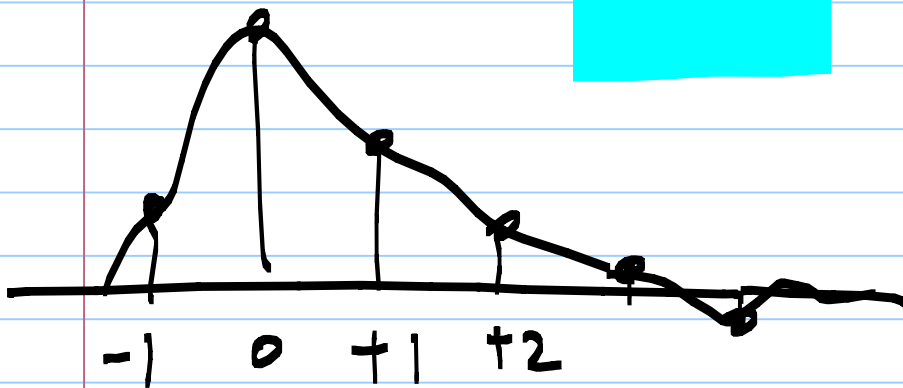


$$H_{ch}(z) = \frac{1}{1 + a_1 z^{-1}}$$

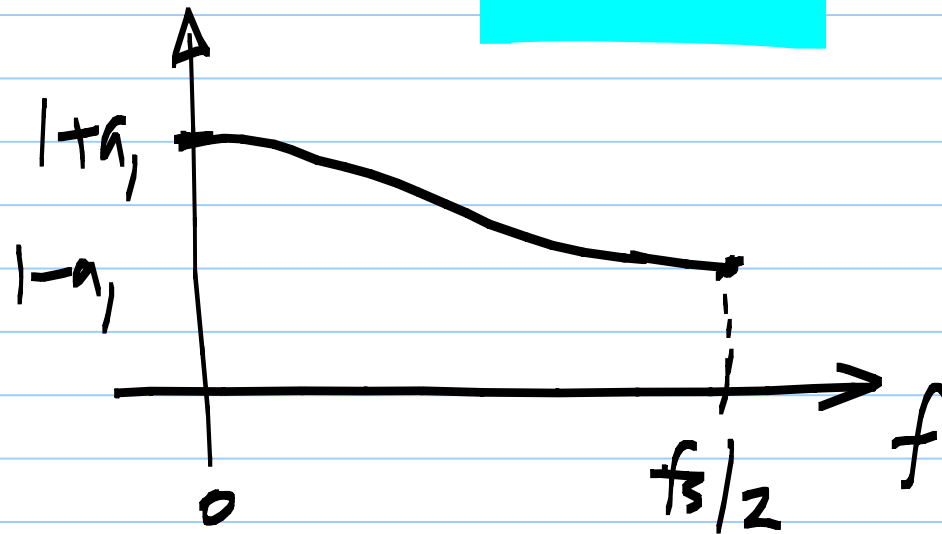

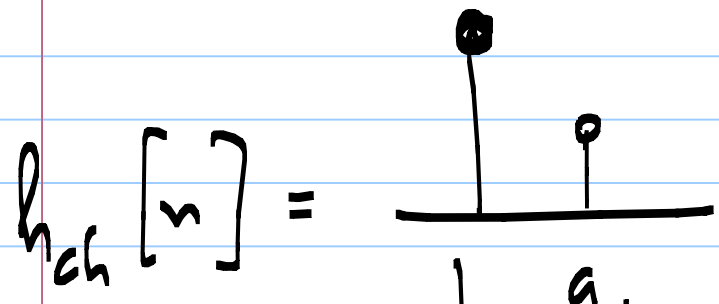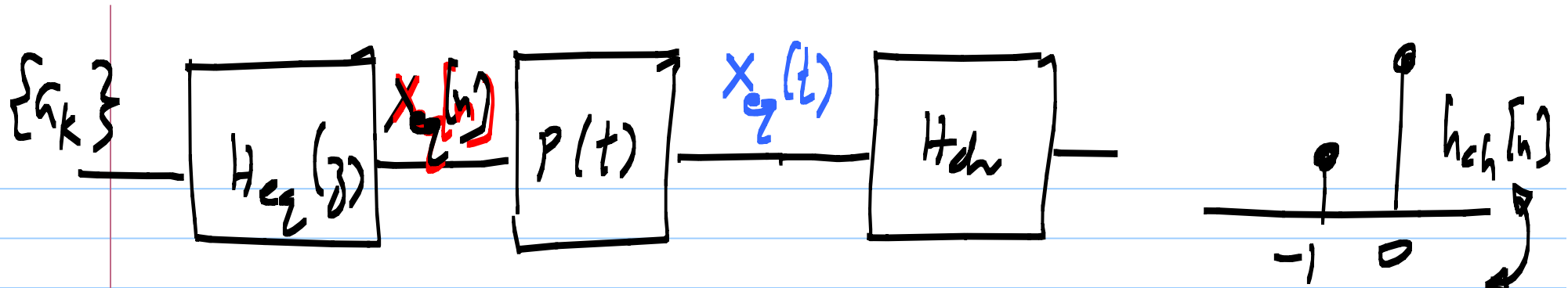

$$H_{ch}(z) = 1 + a_1 z^{-1}$$

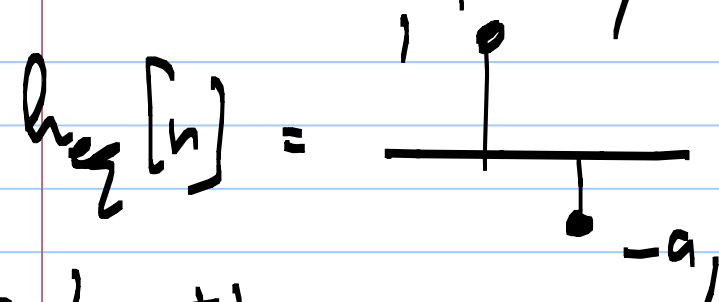

$$H_{eq}(z) = 1 - a_1 z^{-1}$$

