
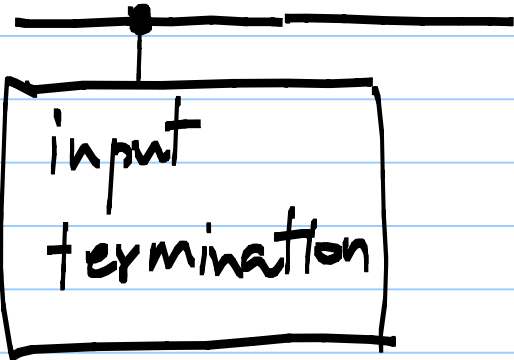


# Receiver circuits:


in

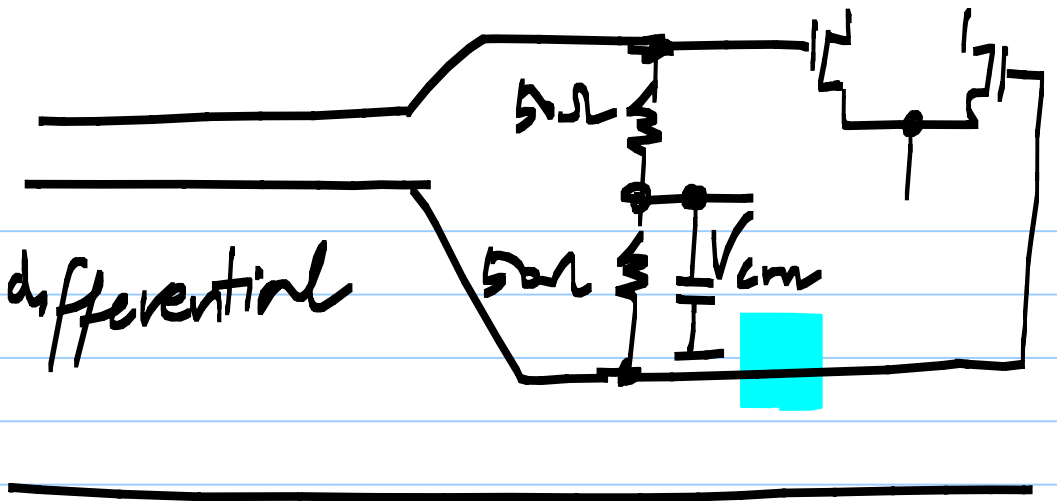

differential




$S_{11}$

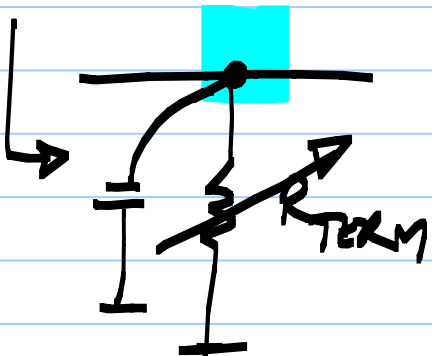


$$|S_{11}| < -10\text{dB}$$

or for broad band termination

Trim for right value

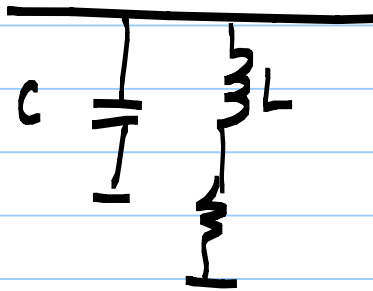

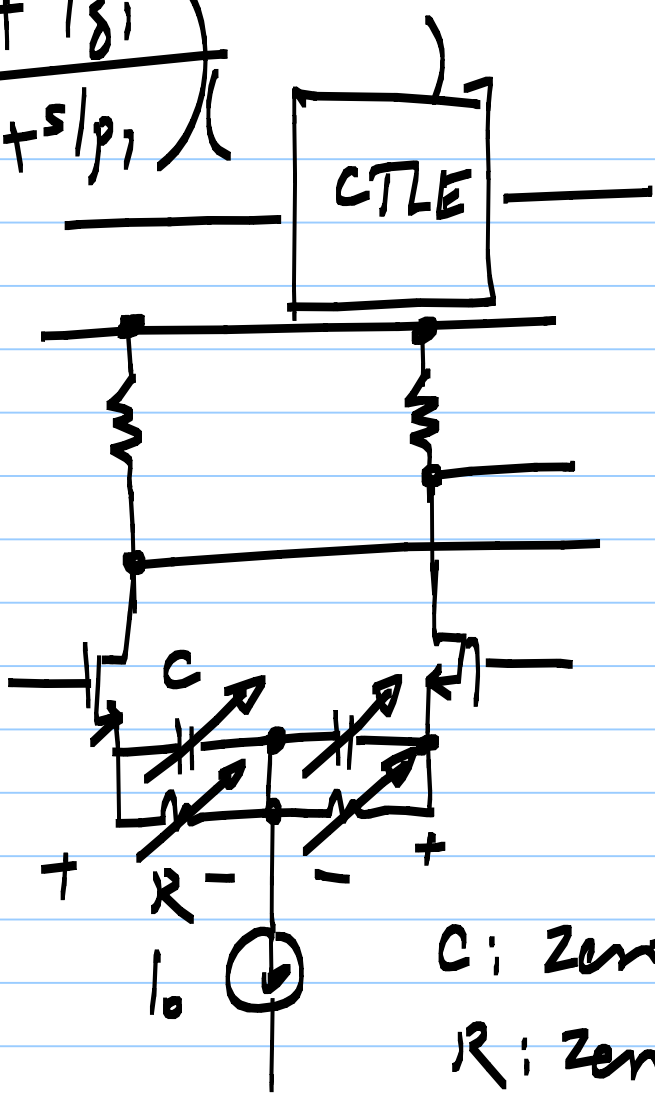
$$\left( \frac{1 + s/z_1}{1 + s/p_1} \right)$$





C: zero  
R: zero, dc gain

Common mode drop across R

No common-mode drop across R

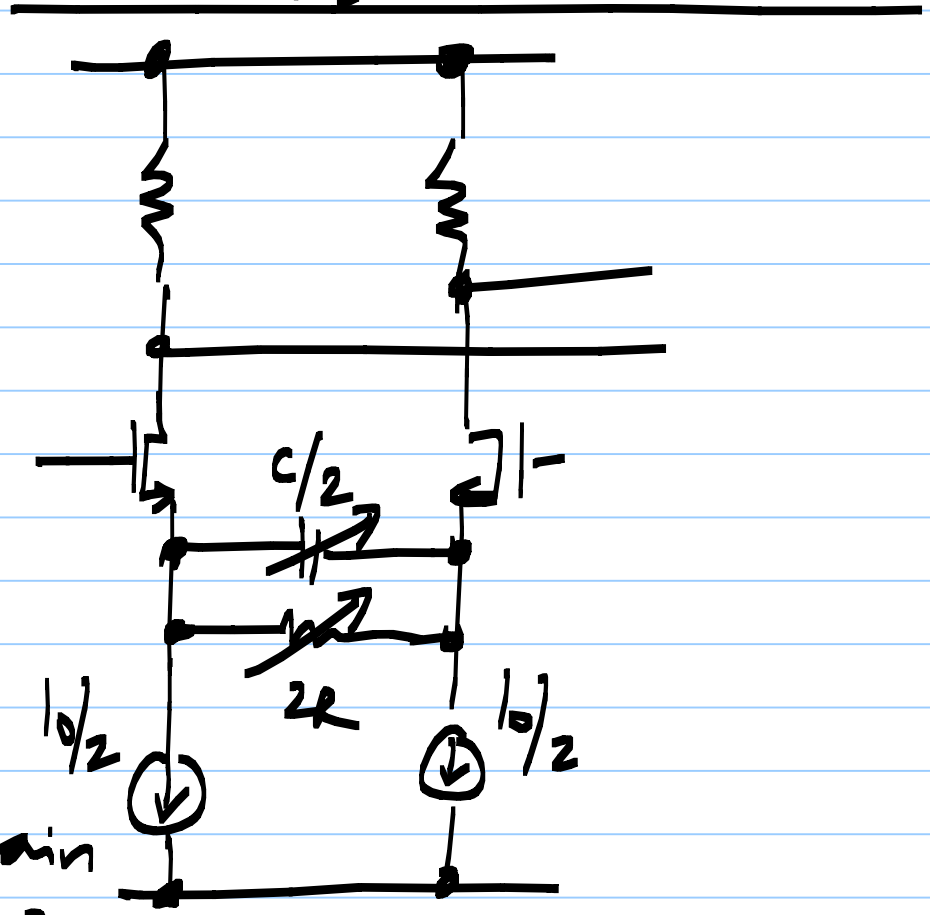


1/2  
2R  
1/2

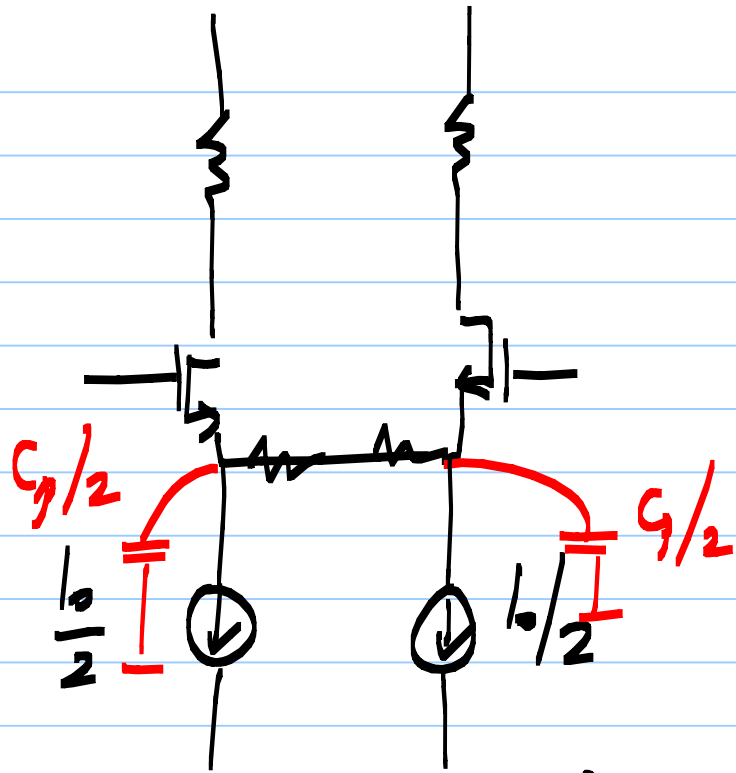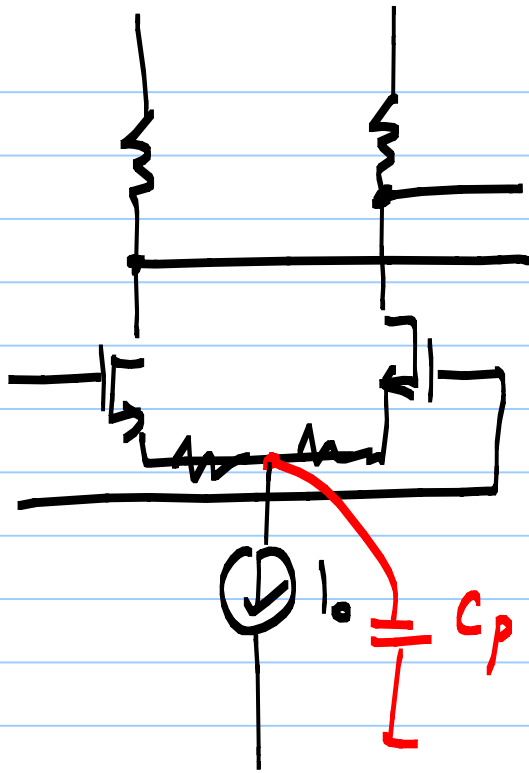


- Noise from  $I_0$  does not appear in the diff. o/p
- $C_p$  does not affect diff. freq. resp.

- Noise from  $I_0$  does appear in the diff. o/p
- $C_p/2$  influences diff. freq. response

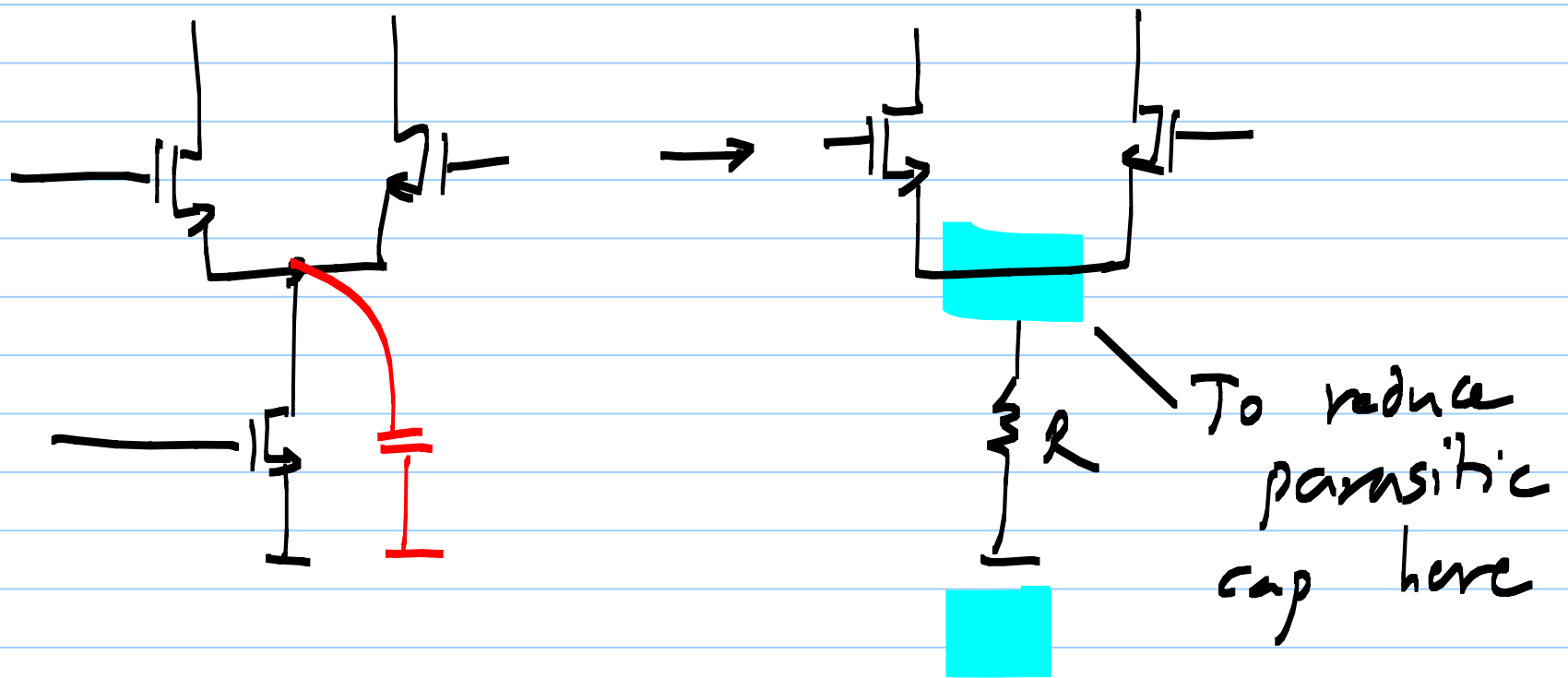poly-Si resistor typically has a smaller parasitic capacitance than a transistor




CTLE:

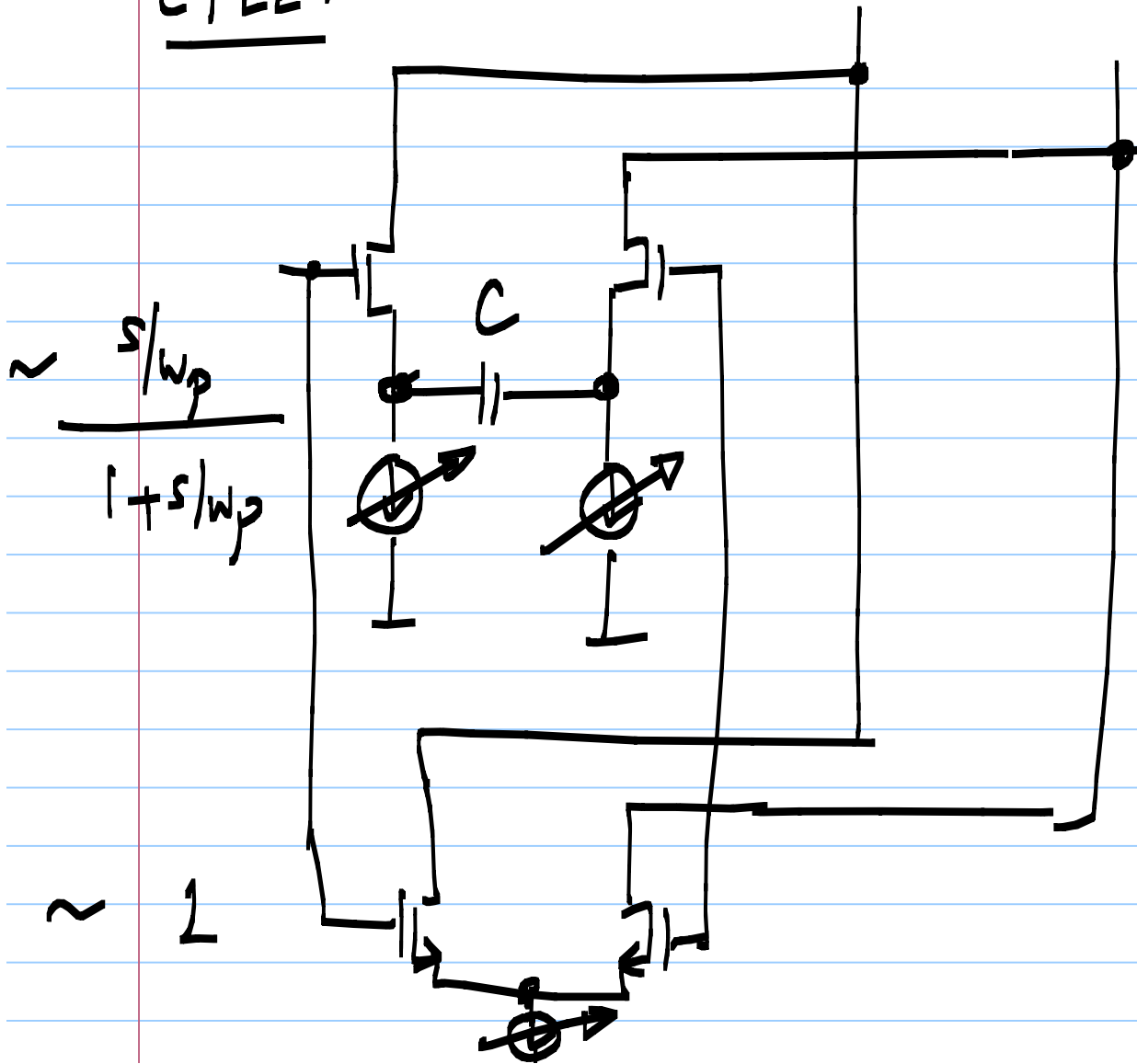

Linear combination

$$\alpha + \beta \cdot \frac{s/w_p}{1 + s/w_p}$$
$$\sim \frac{1 + s/w_z}{1 + s/w_p}$$

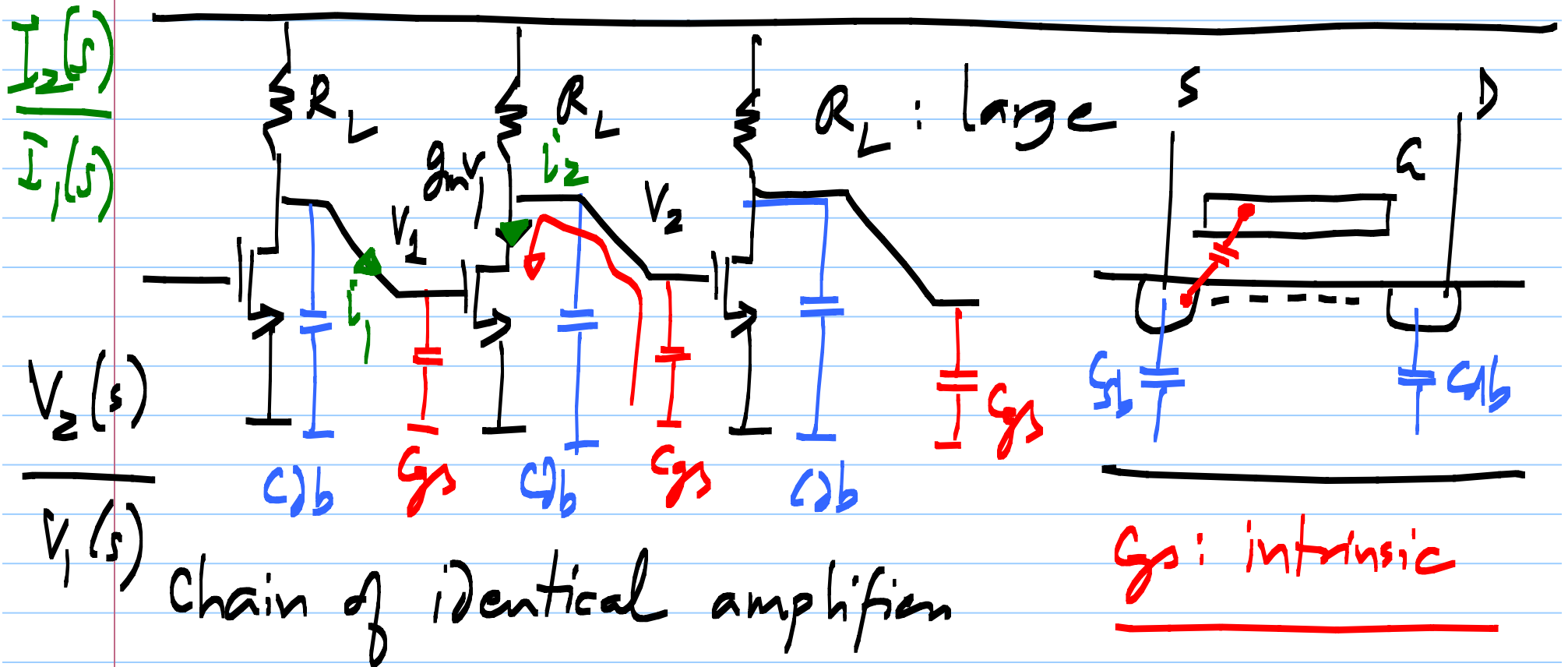Transistors biased at high current densities ( $\frac{I}{W}$ )  
 ~ Min. length transistors



$$\frac{V_2(s)}{V_1(s)} = - \frac{g_m}{s C_{gs}} \quad \left| \frac{V_2}{V_1} \right|_{s=j\omega} = 1 \quad @ \quad \omega = \frac{g_m}{C_{gs}}$$

$$\omega_T = \frac{g_m}{C_{gs}} = \frac{\mu C_{ox} \frac{W}{L} (V_{GS} - V_T)}{\frac{2}{3} C_{ox} W L} = \frac{3}{2} \mu \cdot \frac{V_{GS} - V_T}{L^2}$$

(transit frequency)


$$f_T = \frac{g_m}{2\pi C_{gs}}$$

Measure of inherent speed  
of transistors

$$I_D = \frac{\mu C_{ox}}{2} \frac{W}{L} (V_{GS} - V_T)^2$$

$$(V_{GS} - V_T) = \sqrt{\frac{2I_D}{\mu C_{ox} W/L}}$$

$$\propto \sqrt{\frac{I_D}{W}}$$

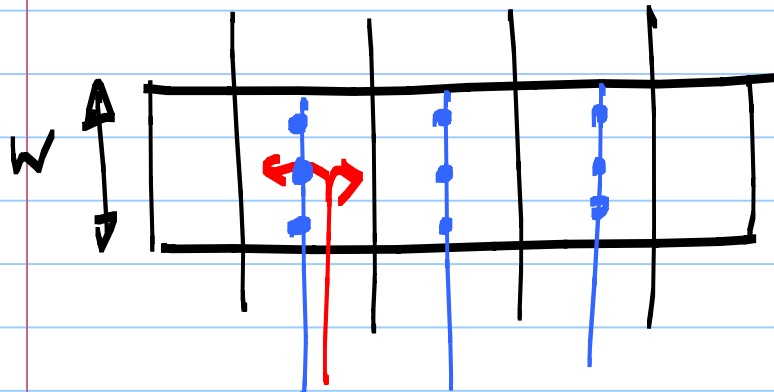

Current density

③  
large current

$$dc \text{ gain} = \frac{g_m}{g_{DS}}$$

$$= \frac{\sqrt{2\mu C_{ox} \frac{W}{L} \cdot I_D}}{I_D} \propto \frac{1}{\sqrt{I_D/W}}$$



$$I_D = \frac{\mu C_{ox}}{2} \frac{W}{L} (V_{GS} - V_T)^2$$

$$= \underbrace{\mu \cdot \frac{V_{GS} - V_T}{L}}_{\text{velocity}} \cdot \underbrace{\frac{C_{ox} W}{2} (V_{GS} - V_T)}_{\text{charge}}$$

$$g_m = \mu C_{ox} \frac{W}{L} (V_{GS} - V_T)$$

$$\omega_T = \frac{3}{2} \mu \cdot \left( \frac{V_{GS} - V_T}{L^2} \right)$$

$$I_D = k \cdot W (V_{GS} - V_T) \cdot v_{sat}$$

$$C_{gs} = k' C_{ox} W L$$

$$g_m = k \cdot W \cdot v_{sat}$$

$$g_m = \frac{k \cdot W v_{sat}}{C_{gs}}$$

$$C_{gs} = k' C_{ox} W L$$

$$= \frac{k}{k' C_{ox}} \left( \frac{v_{sat}}{L} \right)$$

## High-speed circuits:

\* operate at high current densities

— Short  $L$ , large  $V_{GS} - V_T$

→ poor dc gain

→ High current density in wires

— parasitic voltage drops

---