

# EC204: Networks & Systems

## Solutions to Problem Set 9

1. (a) To solve for  $i(t)$ ,  $t \geq 0$  using Thevenin's theorem, we first transform the given network to the Laplace domain, as in figure (1).

We obtain values for the Thevenin impedance  $Z_0(s)$  and voltage source  $V_{oc}(s)$  as

$$Z_0(s) = \frac{1}{\frac{1}{s} + \frac{1}{1+1/(1+s)}}$$

$$= \frac{s(s+2)}{s^2 + 2s + 2}$$

$$V_{oc}(s) = \frac{1}{s} \quad (\text{absence of current})$$

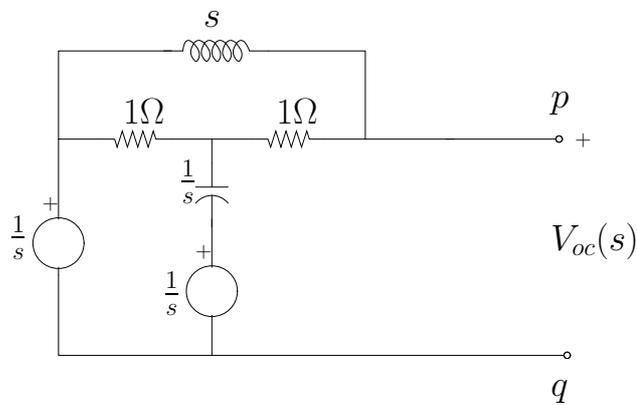


Figure 1: (*Problem 1(a)*) Laplace-transformed network

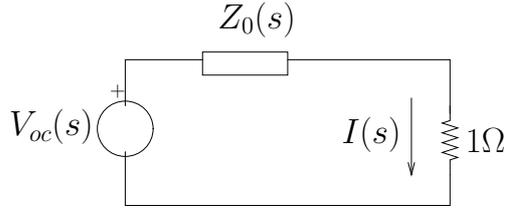


Figure 2: (*Problem 1(a)*) Thevenin equivalent network

From figure (2) we get

$$\begin{aligned}
 I(s) &= \frac{V_{oc}(s)}{Z_0(s) + 1} = \frac{1/s}{\frac{s^2+2s}{s^2+2s+2} + 1} \\
 &= \frac{s^2 + 2s + 2}{s(2s^2 + 4s + 2)} \\
 &= \frac{1}{s} - \frac{1}{2} \left[ \frac{1}{s+1} + \frac{1}{(s+1)^2} \right] \\
 \implies i(t) &= \left\{ 1 - \frac{1}{2} [e^{-t} + te^{-t}] \right\} u(t) \quad \square
 \end{aligned}$$

- (b) By using the substitution theorem, the Laplace-transformed network can be expressed as shown in figures (3) and (4). Then, using superposition, we can treat the network as the sum of two independent networks as shown in figure (5). As a consequence, we obtain

$$I(s) = \frac{V_{oc}(s)}{Z_0(s) + 1} = \frac{s^2 + 2s + 2}{s(2s^2 + 4s + 2)} \quad \square$$

2. The bridge is balanced when  $R_x = 600\Omega$ , i.e.  $I_g = 0$ . The incremental networks for  $R_x = 630\Omega$  and  $R_x = 570\Omega$  are as shown in figures (6) and (7) respectively. These resistive networks can be solved for the galvanometer currents to give

$$I_{g1} = -39.2\mu A, \quad I_{g2} = 40.8\mu A$$

Therefore, by the linearity of the entire network, we can conclude that the range of  $I_g$  is from  $-39.2\mu A$  to  $40.8\mu A$   $\square$ .

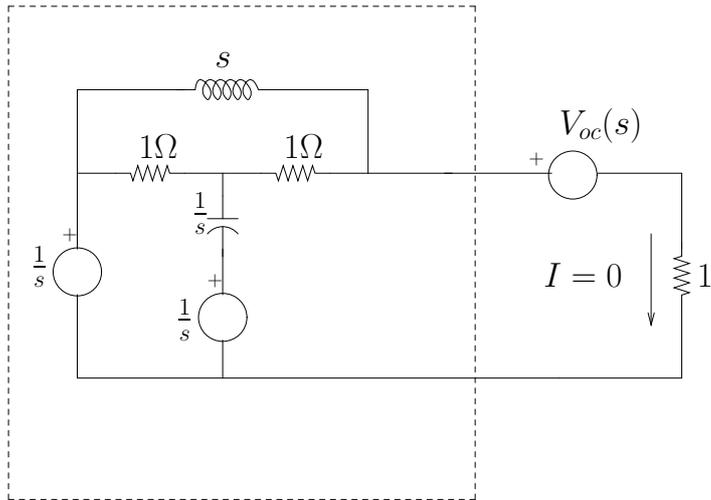


Figure 3: (*Problem 1(b)*) With switch open

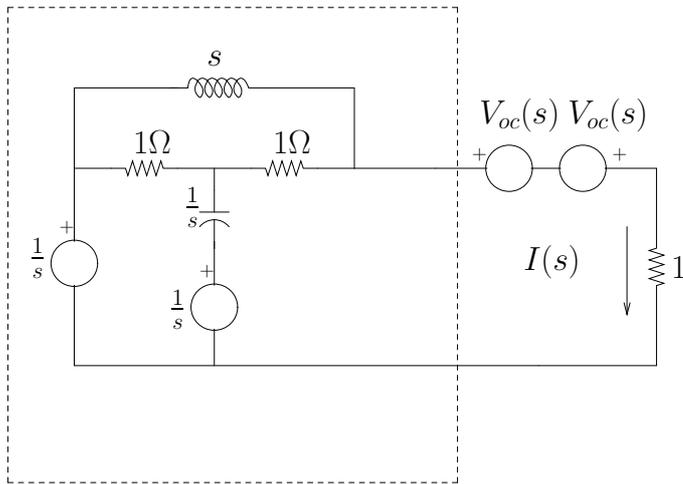


Figure 4: (*Problem 1(b)*) With switch closed

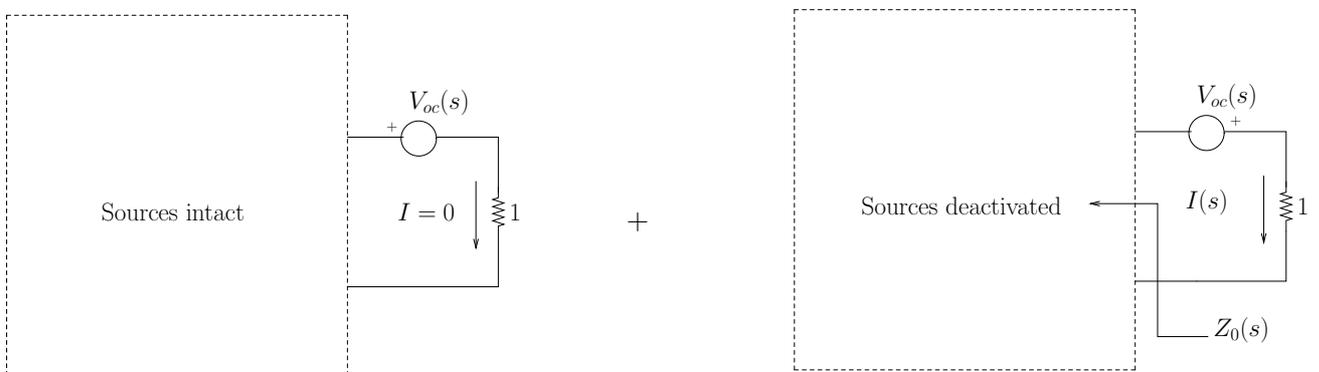


Figure 5: (*Problem 1(b)*) Applying the superposition principle

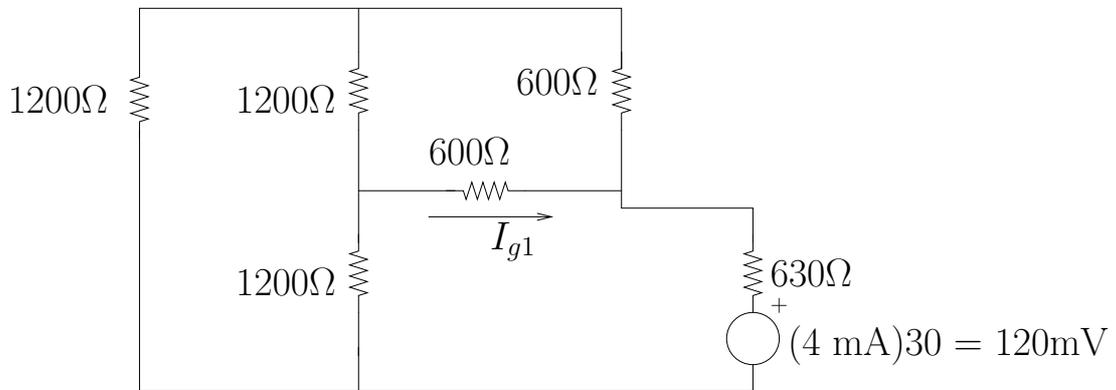


Figure 6: (*Problem 2*) Incremental network for  $R_x = 630\Omega$

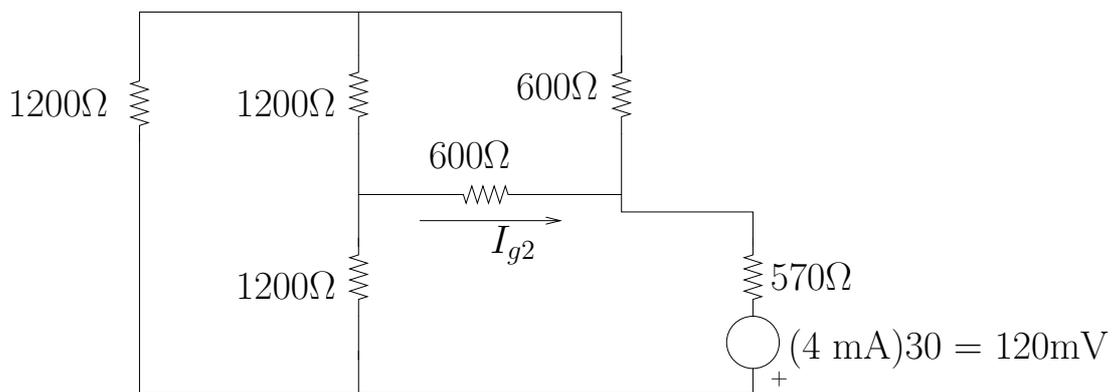


Figure 7: (*Problem 2*) Incremental network for  $R_x = 570\Omega$

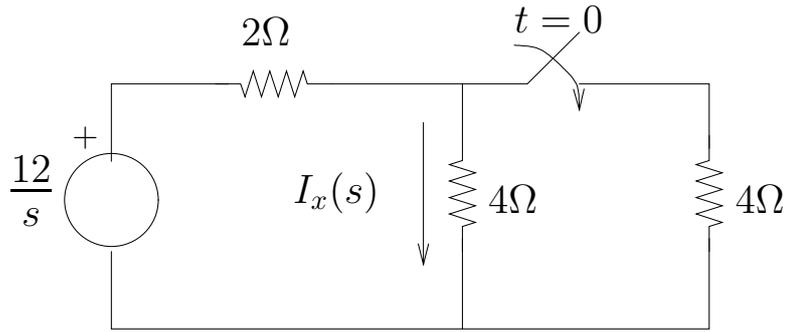


Figure 8: (*Problem 3*) Original network in the Laplace domain

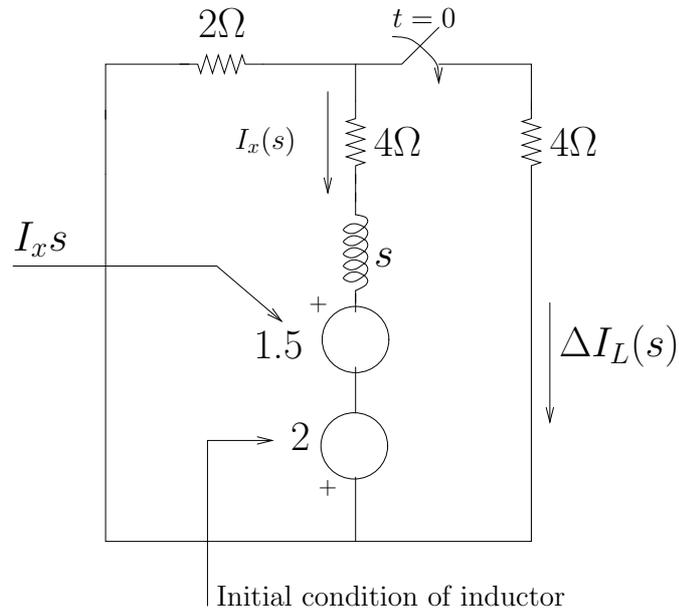


Figure 9: (*Problem 3*) Incremental network in the Laplace domain

3. In the original transformed network (figure (8)), we have

$$I_L(s) = \frac{1.5}{s}, \quad I_x(s) = \frac{1.5}{s}$$

In the incremental network (figure (9)), we account for the inductor's initial current at  $t = 0$  and the compensation voltage  $V_x(s)$  given by

$$V_x(s) = sI_x(s) = 1.5$$

We have,

$$\begin{aligned} \Delta I_L(s) &= \frac{-0.5}{s + 4 + \frac{4}{3}} \times \frac{2}{2 + 4} \\ &= \frac{-0.5}{3s + 16} \\ \implies \Delta i_L(t) &= \frac{-0.5}{3} e^{-16t/3} u(t) \\ \therefore i_L(t) &= \mathcal{L}^{-1}\left(\frac{1.5}{s}\right) + \Delta i_L(t) \\ &= \left[1.5 - \frac{0.5}{3} e^{-16t/3}\right] u(t) \quad \square \end{aligned}$$

4. (a) By substitution theorem, the network in case (ii) is equivalent to network (a) in Figure 10. Now, using superposition theorem, the solution for network (a) is the same as the superposition of the solutions for networks (b) and (c).

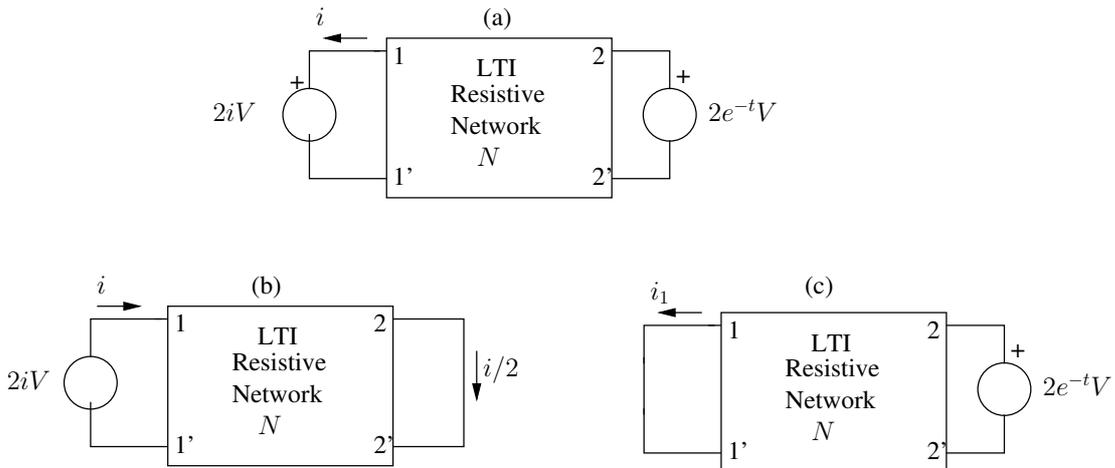


Figure 10: *Problem 4*

By linearity (using case (i)), the current entering terminal 1 in network (b) is  $i$ . Similarly, using reciprocity theorem,  $i_1$  in network (c) is equal to  $e^{-t}/2$  A. Using superposition, we have  $i = i_1 - i$ . Therefore, we have

$$i = i_1/2 = e^{-t}/4 \text{ A.}$$

- (b) Since  $z_{11} = z_{22}$ ,  $y_{11} = y_{22}$ . Also, for this network  $y_{12} = y_{21}$ . Therefore, we can easily write down the y-parameters (from cases (i) and (ii)) as

$$Y = \begin{bmatrix} 0.5 & -0.25 \\ -0.25 & 0.5 \end{bmatrix}.$$

Finally, we have

$$Z = Y^{-1} = \begin{bmatrix} 8/3 & 4/3 \\ 4/3 & 8/3 \end{bmatrix}.$$