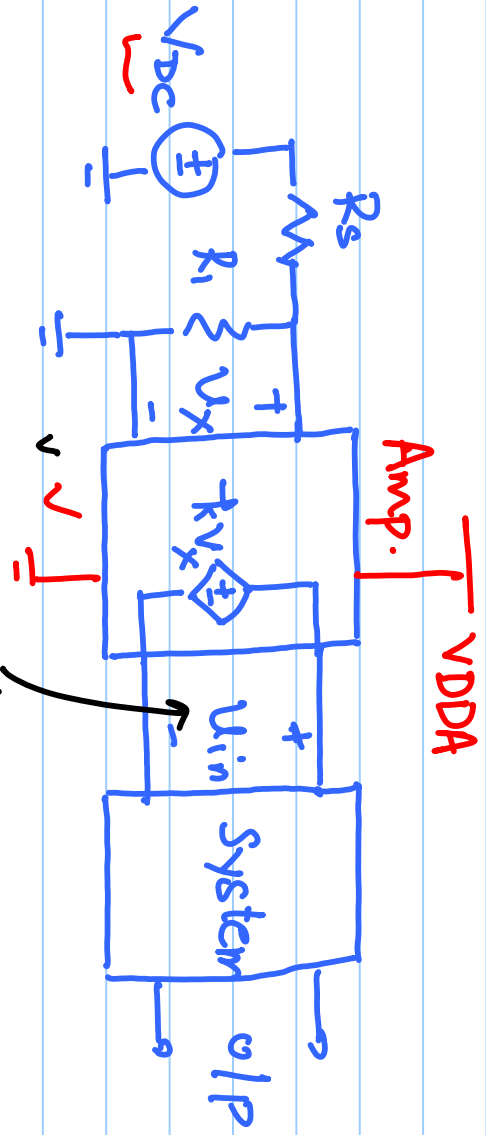


Lecture # 03




as large as required by sys.

$$V_x = \frac{R_2}{R_1 + R_2} V_{dc}$$

$$V_{in} = k V_x < V_{dc}$$


VCVS: Voltage Controlled Voltage Source.

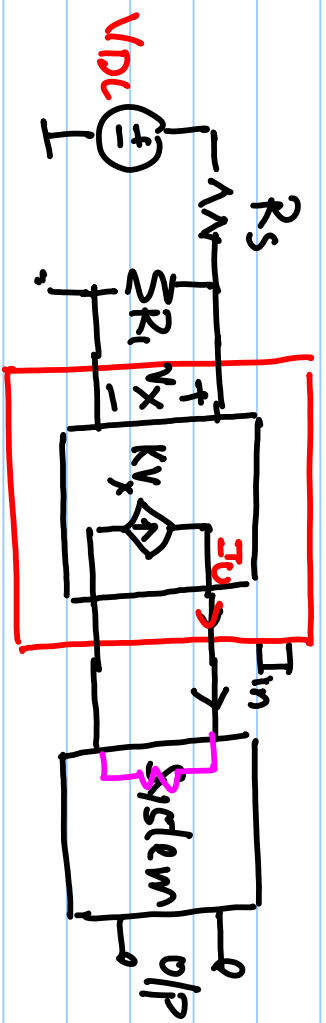


VCCS: Voltage Controlled Current Source

$$I_o = k V_x = k \cdot \frac{R_2}{R_1 + R_2} V_{dc}$$

Current Controlled Current Source (CCCS)

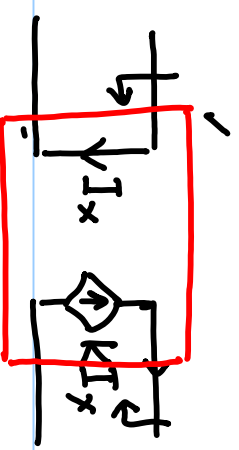

Current Controlled Voltage Source (CCVS)

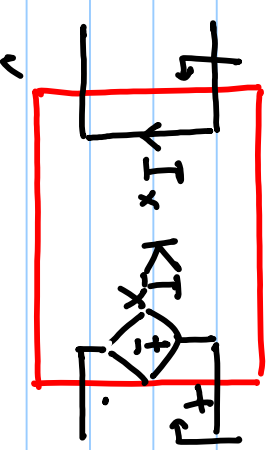





Voltage source @ o/p $\Rightarrow Z_{out} = 0$


Current source @ o/p $\Rightarrow Z_{out} = \infty$

Voltage sensing @ i/p $\Rightarrow Z_{in} = \infty$




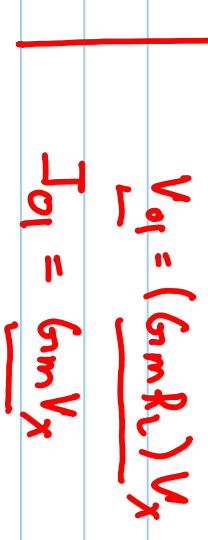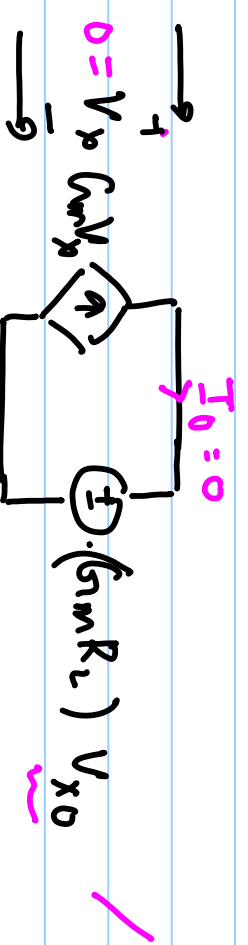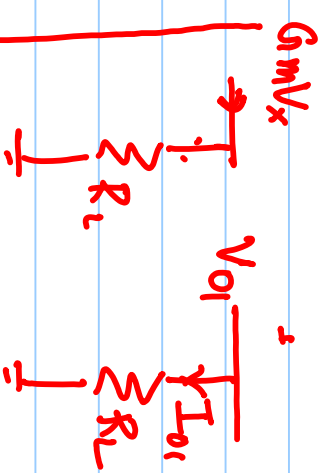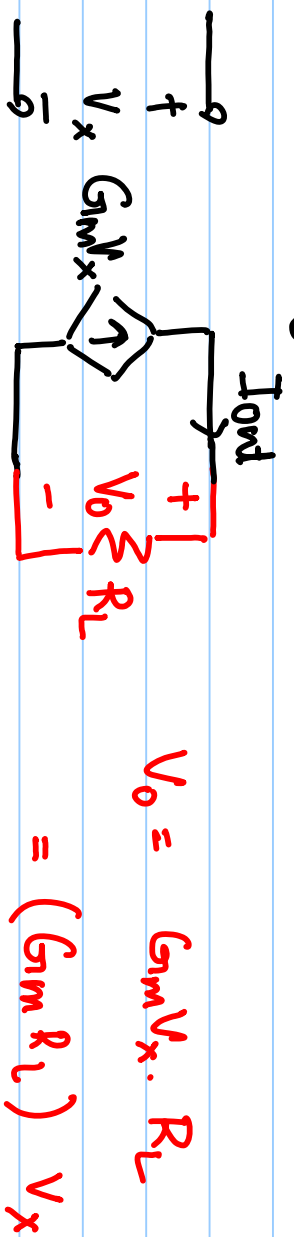Current sensing @ i/p $\Rightarrow Z_{in} = 0$



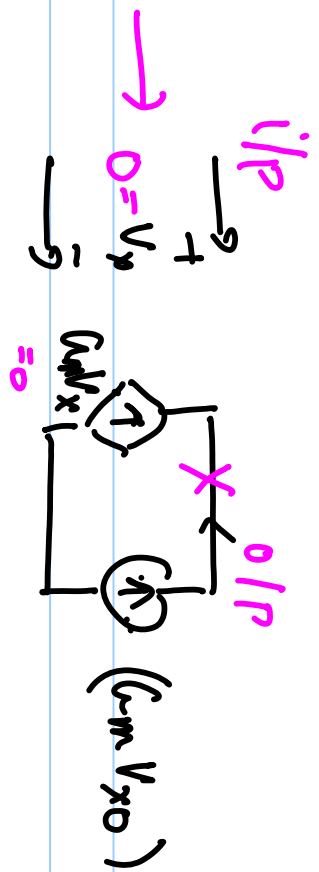



Unilateral controlled sources.

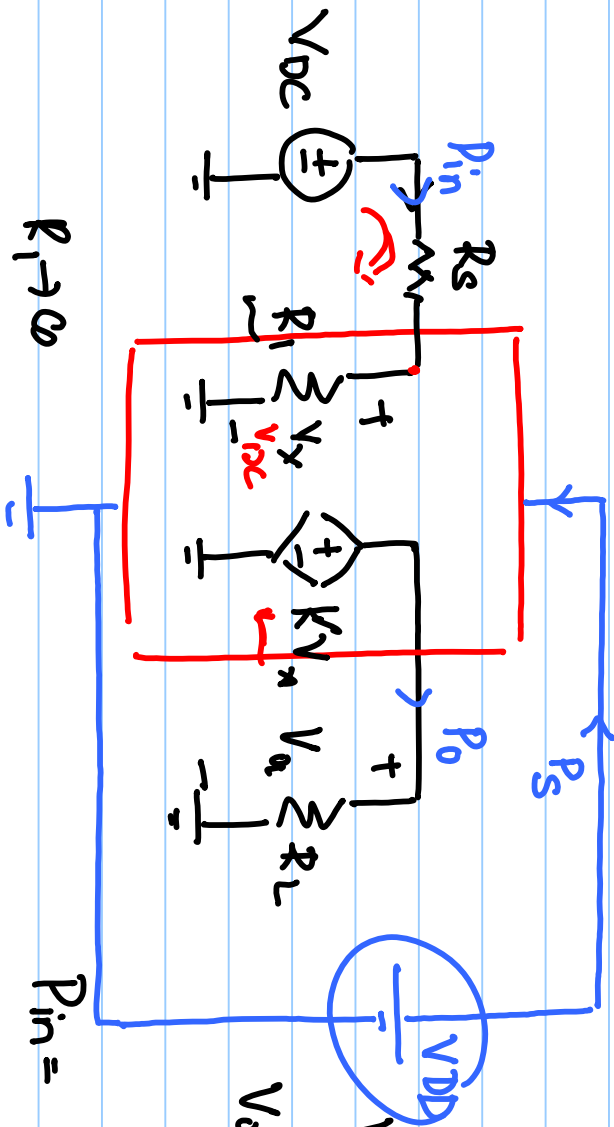

$$P_{in} = \frac{V_{dc}^2}{R_1 + R_s}$$

$$V_o = K \frac{R_1}{R_1 + R_s} V_{dc}$$

$$V_o = K V_x$$

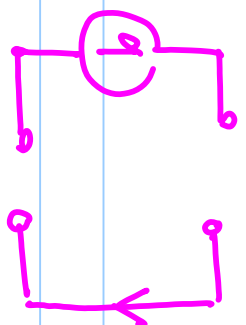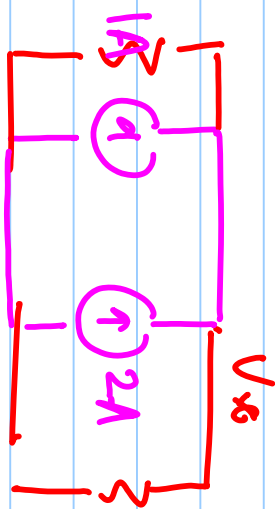

$$P_{out} = \frac{K^2 V_x^2}{R_L} =$$

$$\frac{K^2 V_{dc}^2}{R_L} \left(\frac{R_1}{R_1 + R_s} \right)^2$$

$$\frac{P_{out}}{P_{in}} = \frac{K^2 R_1^2 / R_L (R_1 + R_s)^2}{1 / (R_1 + R_s)}$$

$$= \frac{K^2 R_1^2}{R_L (R_1 + R_s)}$$


$$\frac{P_{out}}{P_{in}} = \frac{K^2}{\frac{R_L}{R_1} \left(1 + \frac{R_S}{R_1}\right)}$$

> 1

$$P_S + P_{in} > P_{out}$$

VDDA, (AVDD, GYVDD)

Analog ↓ Digital

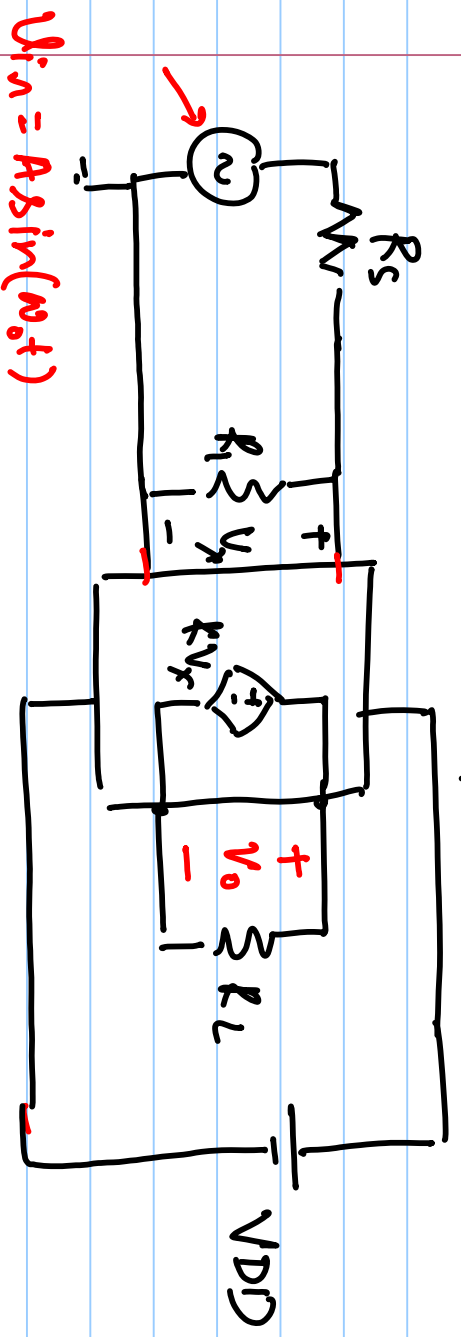


$$V_o = k V_x = k \frac{R_1}{R_1 + R_S} (A \sin(\omega t))$$

$$V_o = k \frac{R_1}{R_1 + R_S} A \sin(\omega t)$$


— Power gain from i/p to o/p irrespective of i/p ang. & frequency

— Power is drawn from supply VDD and delivered to o/p.

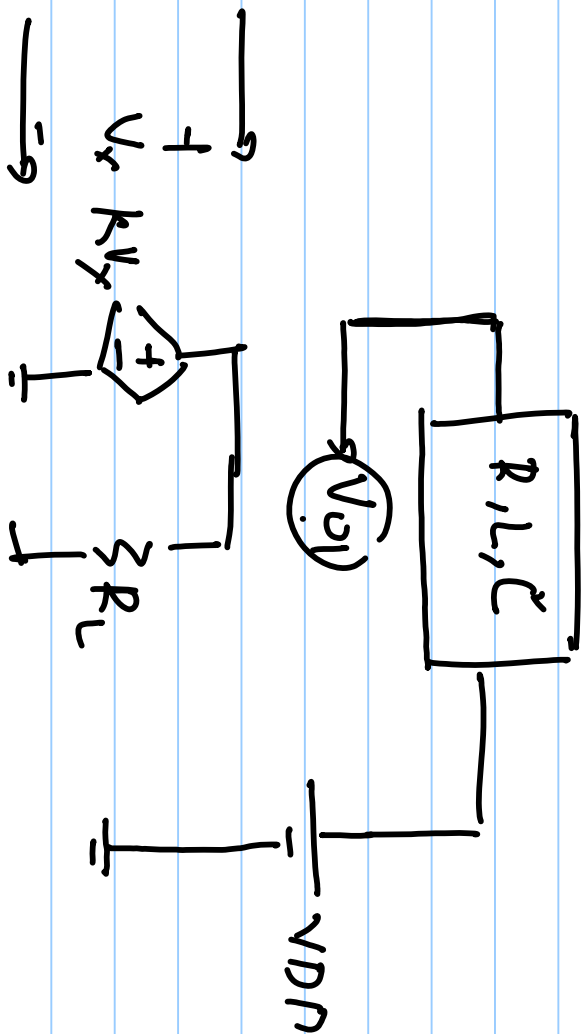$A \sin(\omega_i t)$ → Linear → $\alpha \cdot A \sin(\omega_i t + \phi)$



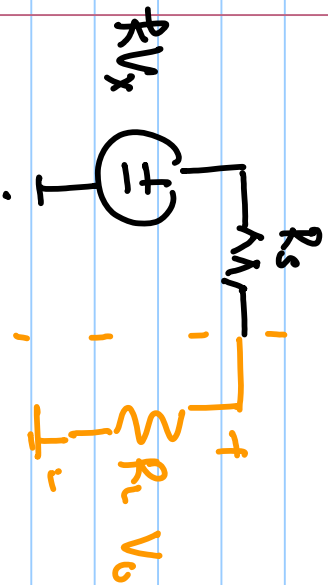\Rightarrow Non-linear system to deliver power at o/p with $\frac{P_{out}}{P_{in}} > 1$



$$V_o = \frac{R_L}{R_L + R_s} (kV_x)$$