
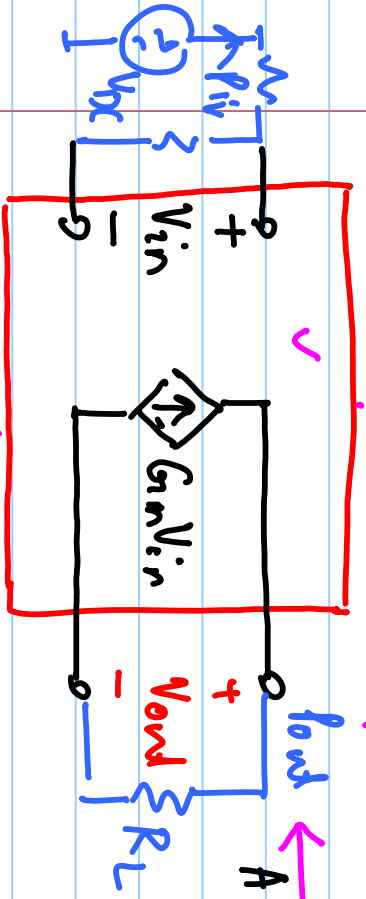
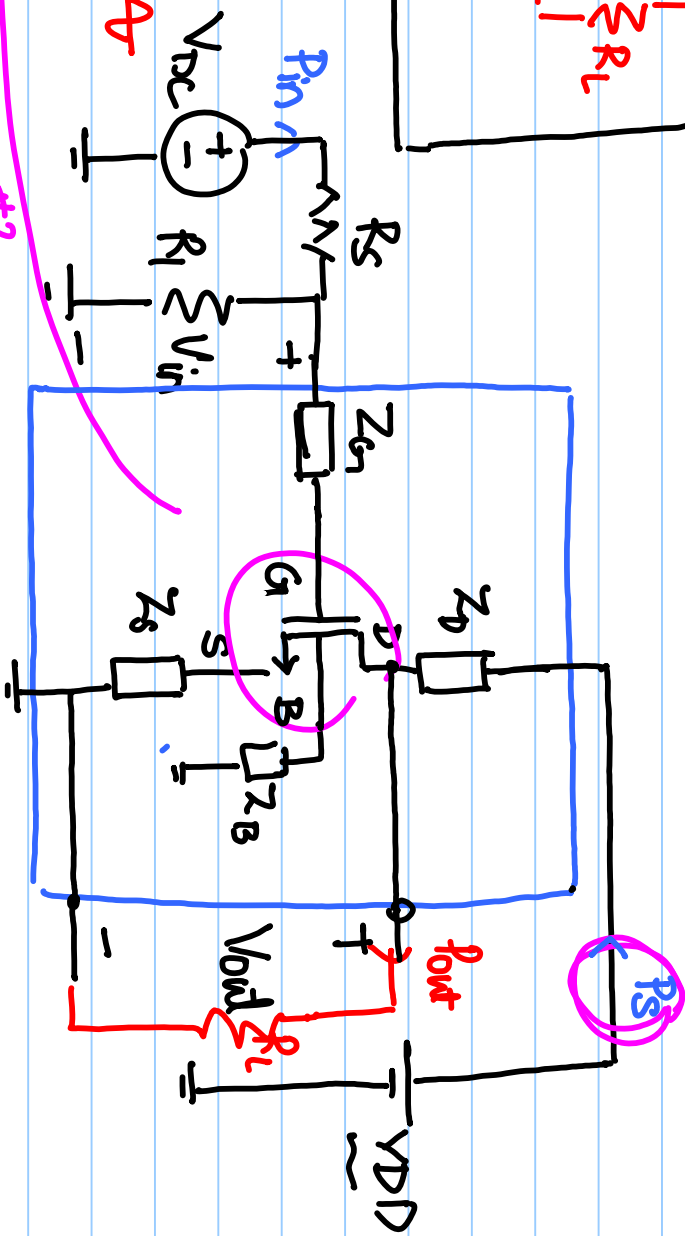

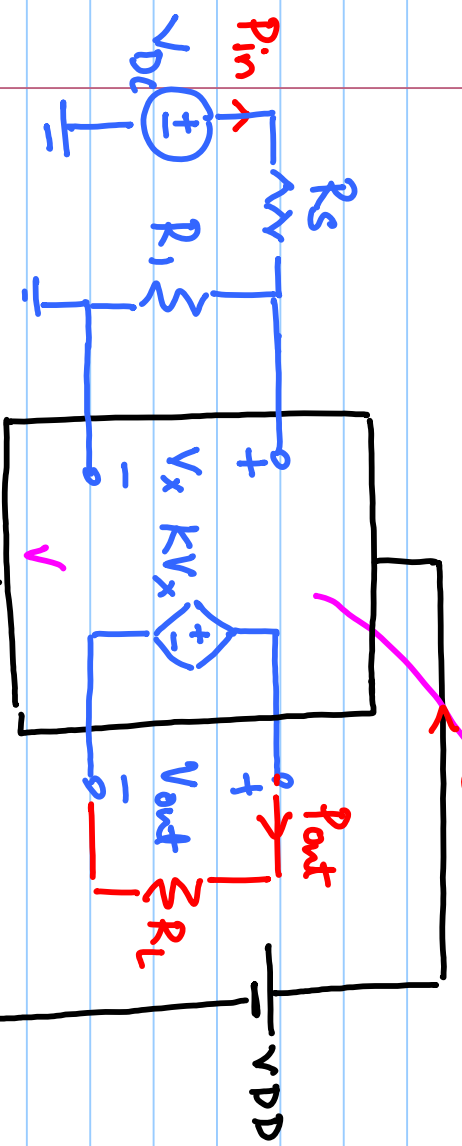
# Lecture # 04



MOSFET: Metal-Oxide-Semiconductor Field Effect Transistor





Approx.  $P_{out} > P_{in}$

$P_{out} < P_{in} + P_s$

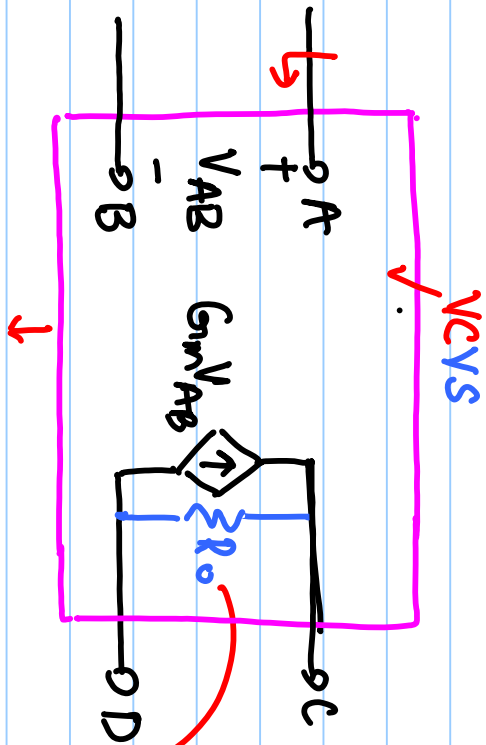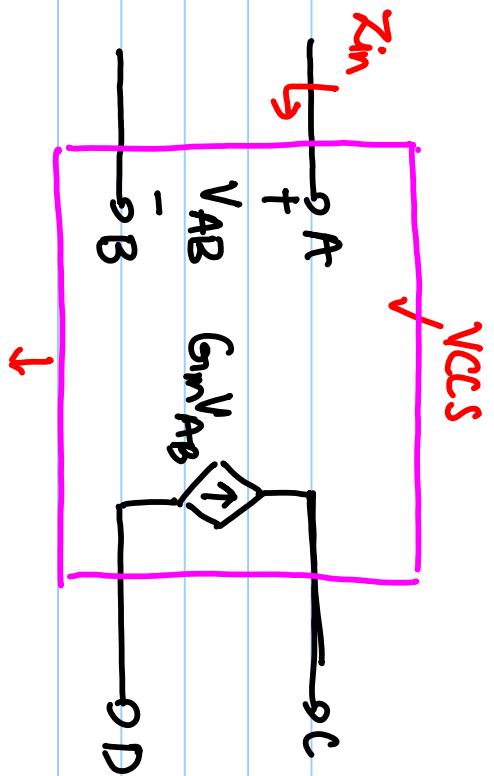
$V_{out} = G_m V_{in} \cdot R_L = (G_m R_L) V_{in}$  ;  $P_{out} > P_{in}$



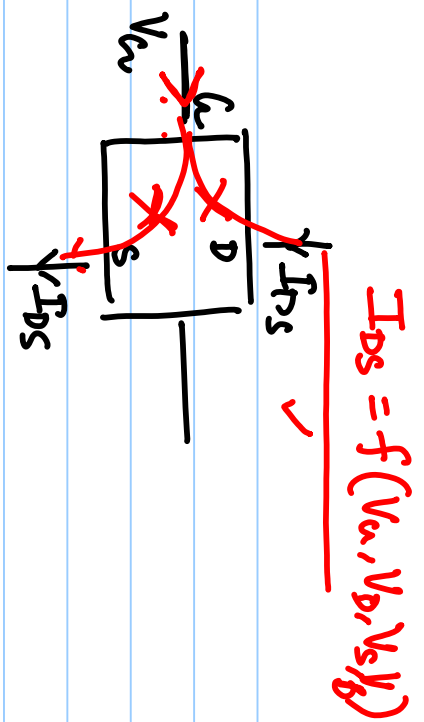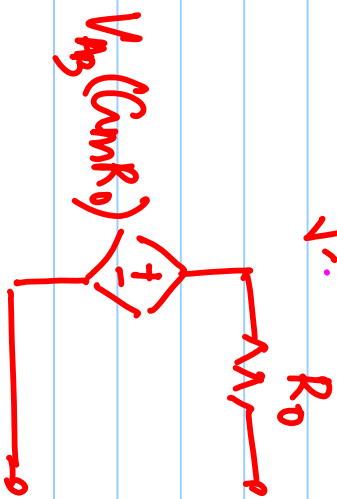
$$\frac{V_{CD}}{V_{AB}} = (G_m R_o) = K$$


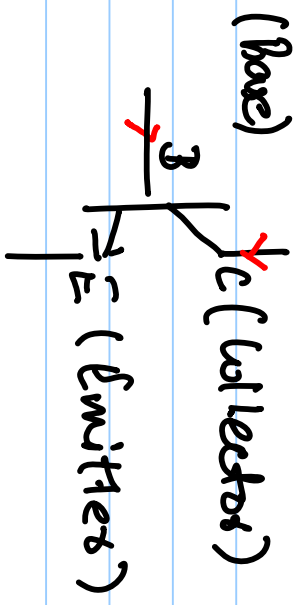
$$I_{D_S} = f(V_{g_s}, V_{d_s}, V_{s_s}, V_{b_s})$$



$$I_{C_C} = f(V_B, V_C, V_E)$$

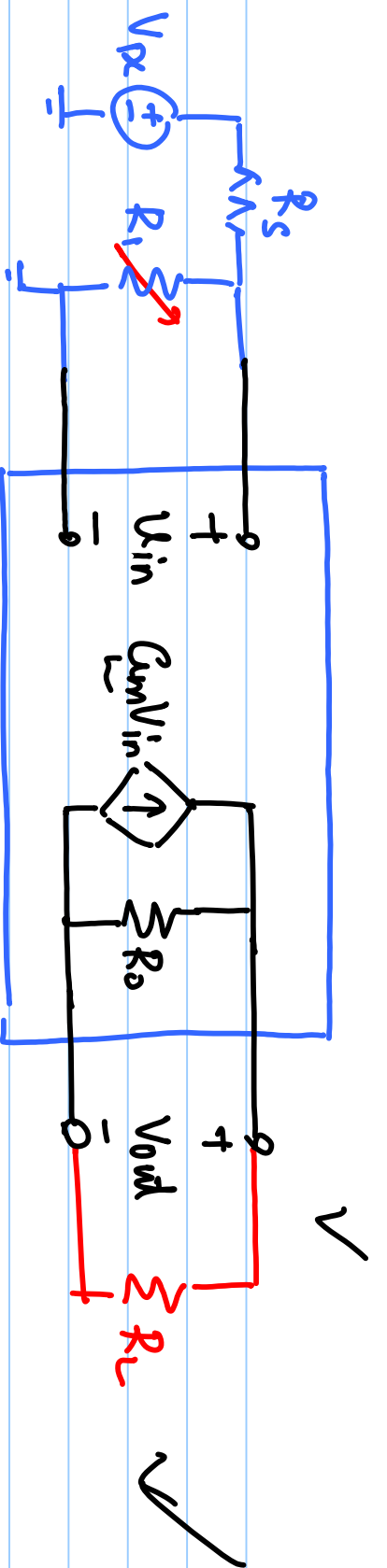


$$V_{out} = \frac{R_1}{R_1 + R_S} V_{dc} \times (G_m) (R_0 \parallel R_L)$$

-  $G_m$ ,  $R_0$  process, voltage, temperature (NVT) dependent parameters

$$\frac{V_{out}}{V_{in}} \approx 10$$

Ex:


Acceleration / Decelerate

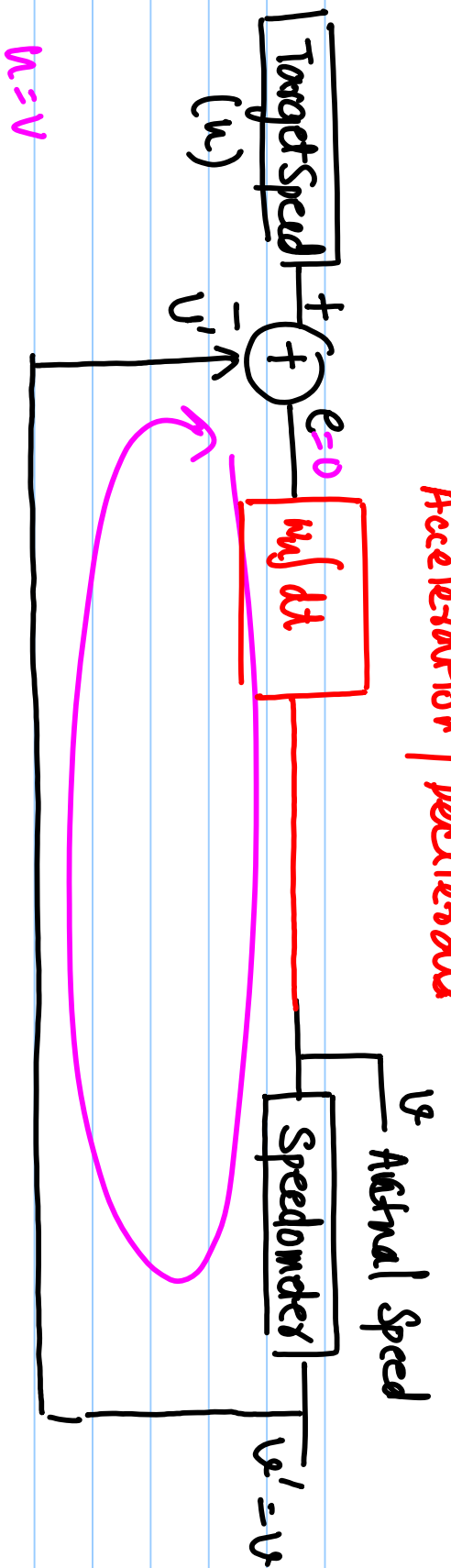


$$v = \alpha t$$

$$e \rightarrow \int dt \rightarrow v$$


Tesla

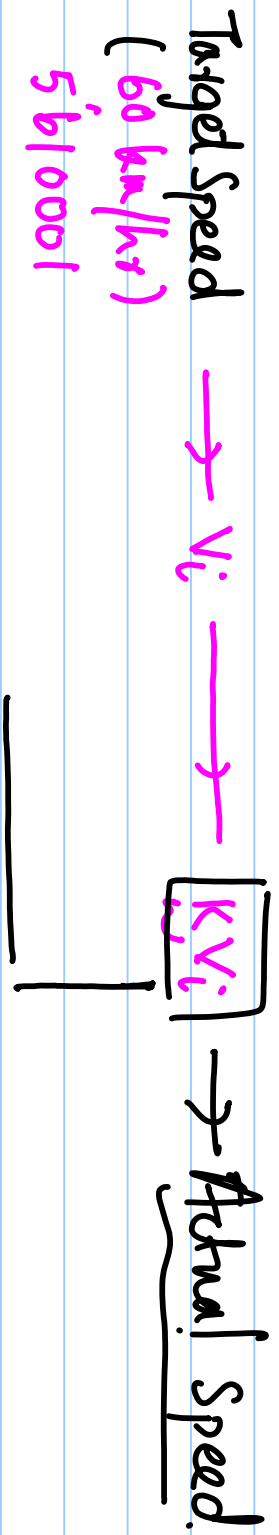

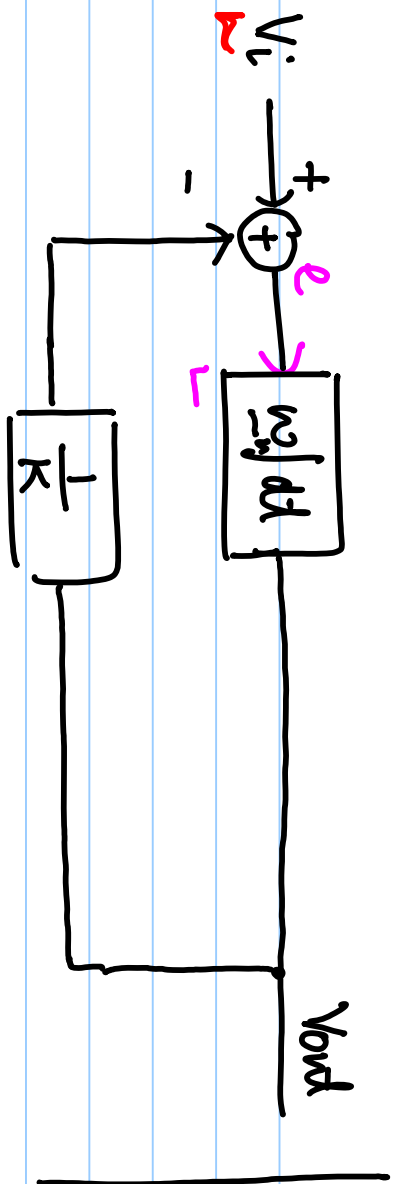

$$V_{out} = K V_i v$$

$$\frac{V_{out}}{K} = \underline{V_i}$$

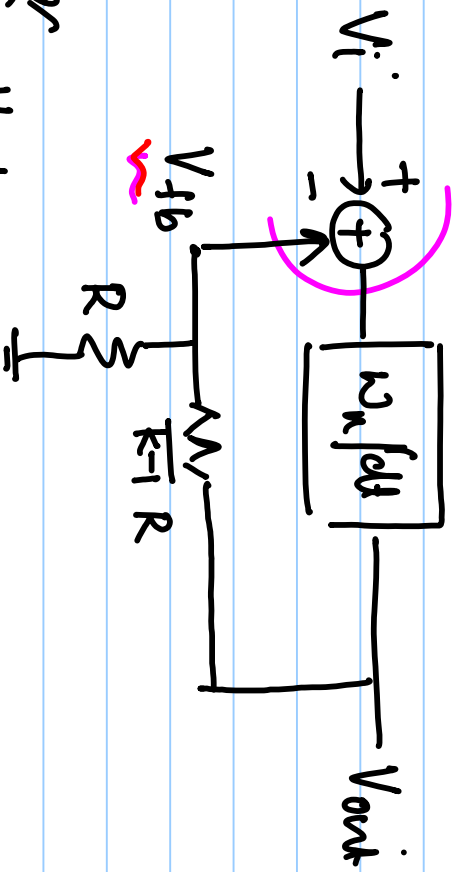



$$V_{fb} = \frac{K}{K-1} V_{out}$$

$$x \rightarrow \left[ \int dt \right] \rightarrow y$$

$$y = \int x \cdot dt$$

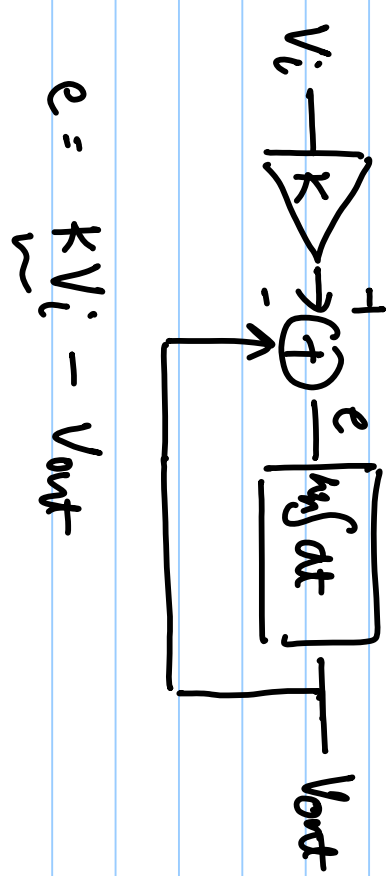
$$V_{out} = \omega_n \int_0^t e \cdot dt + V_{out}(0)$$



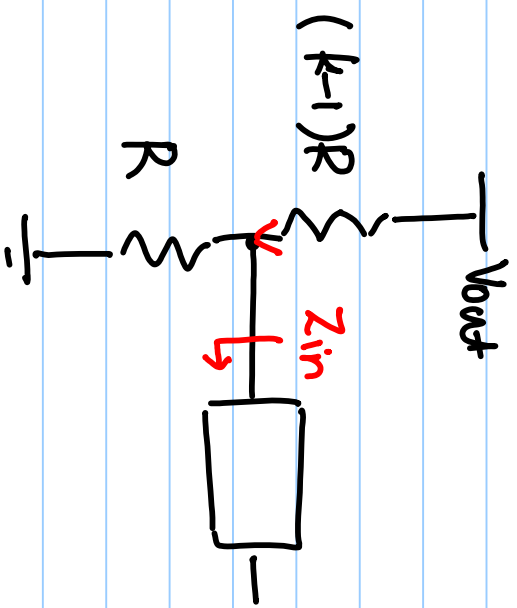

#1  $Z_{in} = \infty$
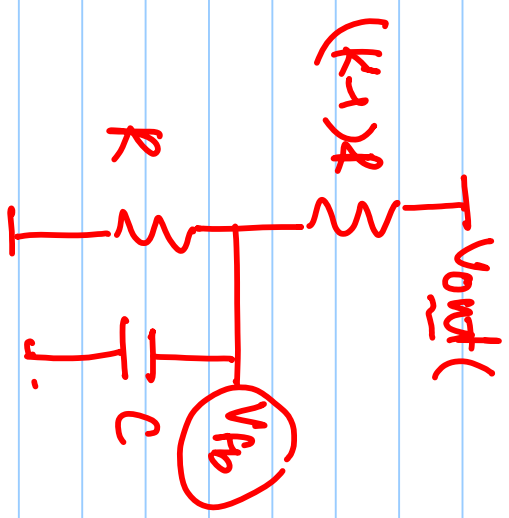
#2  $Z_{in}(0) = \infty$ ,  $Z_{in}(\infty)$  is finite



$$V_{R0} = \frac{R \parallel \frac{1}{sC}}{(k-1)R + (R \parallel \frac{1}{sC})} V_{out}$$