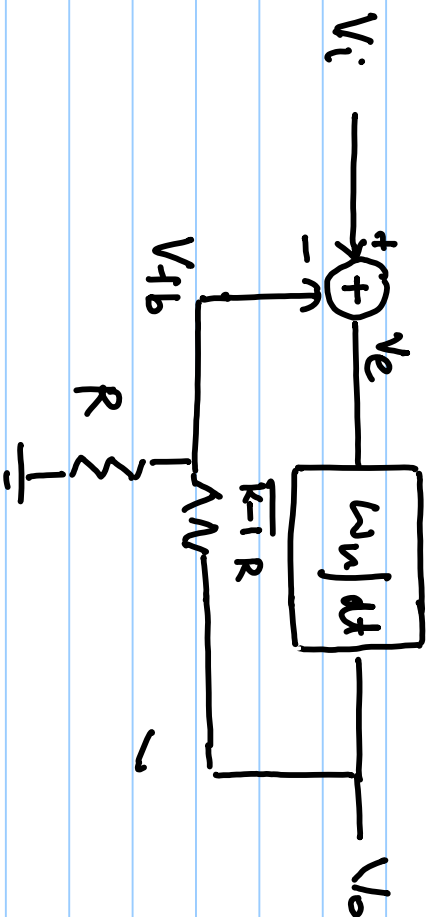



# Lecture # 05



$$V_e = V_i - V_{fb}$$

$$V_{fb} = \frac{1}{k} V_o$$

$$V_o = k \int V_e \cdot dt$$

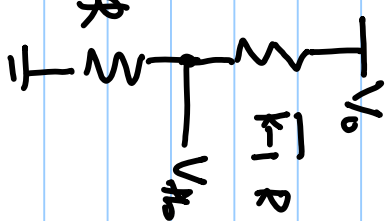

$$V_o = k \int \left( V_i - \frac{V_o}{k} \right) dt \quad (1)$$

$$\frac{dV_o}{dt} = k \left( V_i - \frac{V_o}{k} \right)$$

$$\frac{dV_o}{dt} + k \frac{V_o}{k} = k V_i$$

$$V_o = e^{-\omega t/k} \int k V_i e^{\omega t/k} dt + Q e^{-\omega t/k}$$

$$V_o = e^{-\omega t/k} \int k V_i(0) e^{\omega t/k} dt + Q e^{-\omega t/k}$$

$$V_o = V_i(0) \cdot \frac{k}{k/k} + Q e^{-\omega t/k}$$

$$V_{fb} = \frac{R}{k+R} V_o = \frac{1}{k} V_o$$


$$V_i = 0; t < 0$$

$$= V_i(0); t \geq 0$$

$$V_o(t) = K V_i(0) + Q e^{-\omega_n t / k}$$

at  $t=0$ ,  $V_o(t) = 0 \Rightarrow 0 = K V_i(0) + Q \Rightarrow Q = -K V_i(0)$


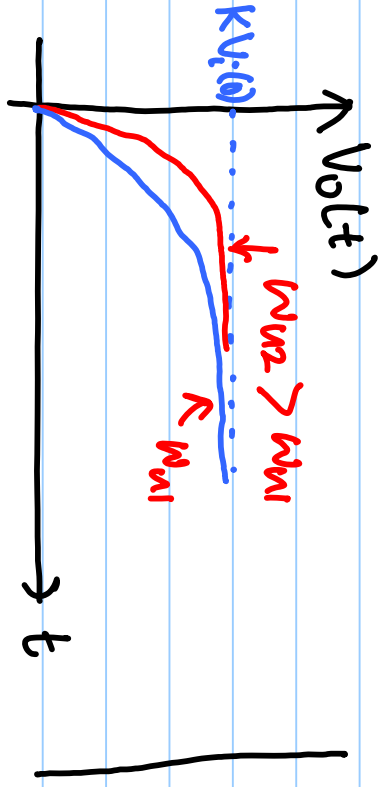
$$V_o(t) = K V_i(0) \left( 1 - e^{-\omega_n t / k} \right) \checkmark$$



$$\frac{dV_o(t)}{dt} = K V_i(0) \frac{\omega_n}{k} \cdot e^{-\omega_n t / k}$$

$$= \omega_n M_i(0) e^{-\omega_n t / k}$$

$$(V_e = V_i - V_{th})$$

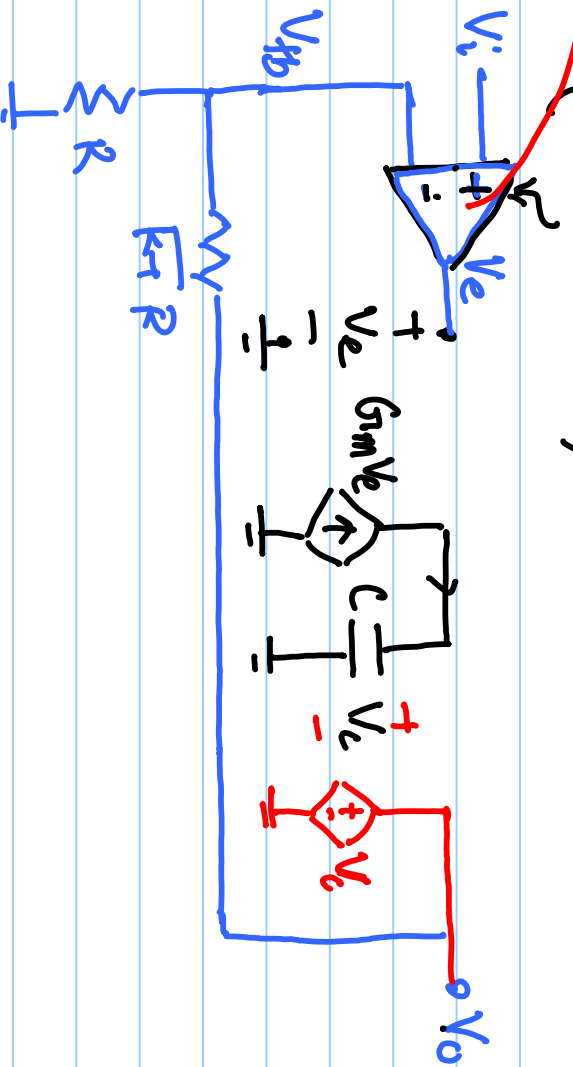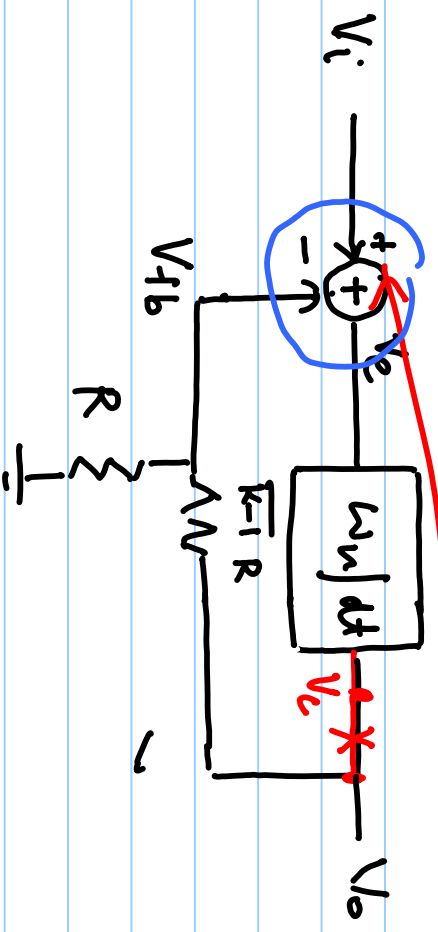

$$V_o = \omega_n \int V_e dt \checkmark$$

$$i_c = C \frac{dV_c}{dt}$$

$$i_c = l_m \frac{dV_c}{dt}$$

$$V_c = \frac{1}{C} \int i_c dt$$

$$V_c = \frac{l_m}{C} \int V_o dt$$

$$V_c = \frac{1}{C} \int i_c dt$$

$$V_c(t) = \frac{1}{C} \int G_m V_e dt$$



$$V_c(t) = \frac{G_m}{C} \int V_e dt$$

$$V_o(t) = V_c(t)$$


$$V_o(t) = \frac{G_m}{C} \int V_e dt$$

$i_c \propto V_e$


Ideal OpAmp.

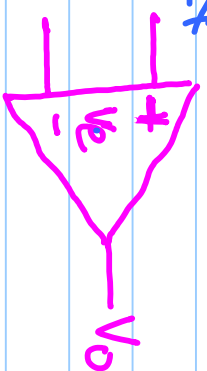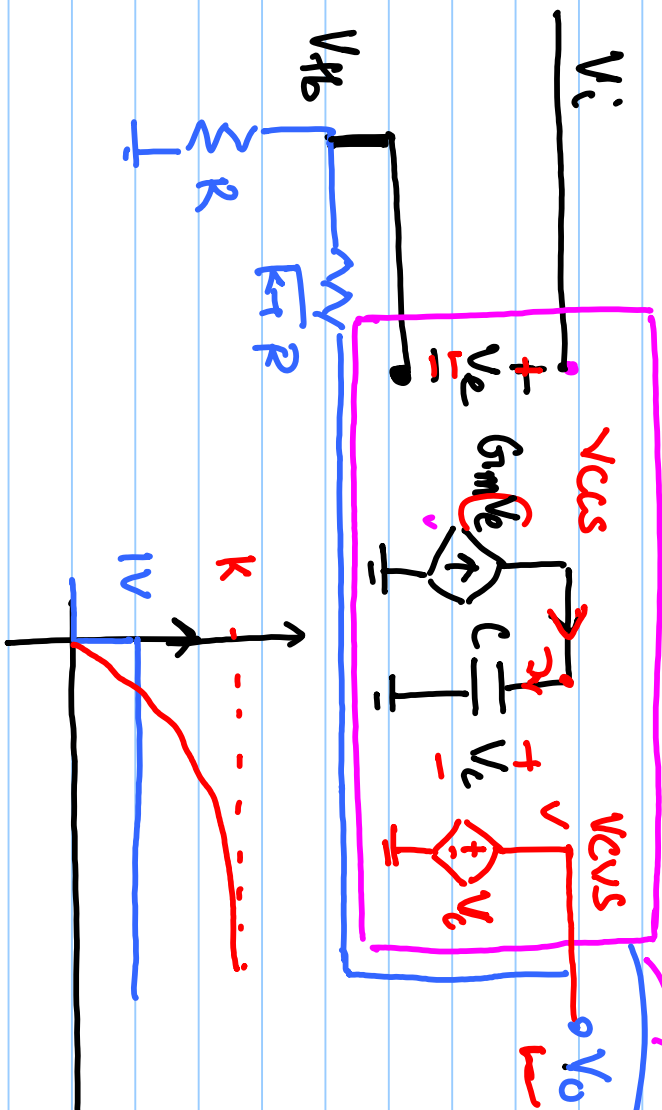

$$V_o(t) = \int \frac{G_m}{C} V_e dt$$

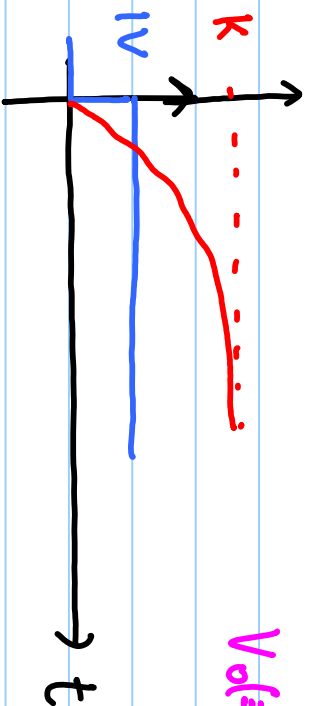


✓

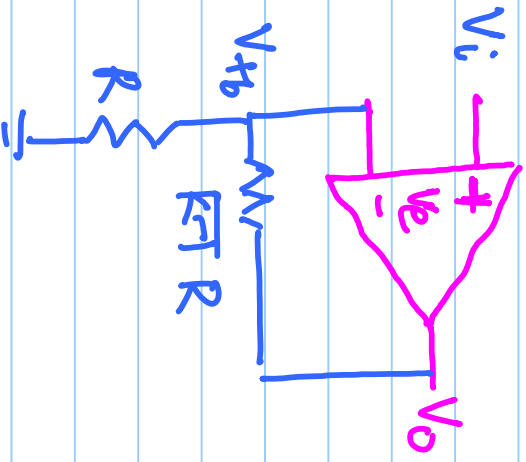

$$V_o(t) = \frac{G_m}{C} \int v_e dt$$


$$V_o(t) = \frac{G_m}{C} \int \left( V_i - \frac{V_o}{K} \right) dt$$

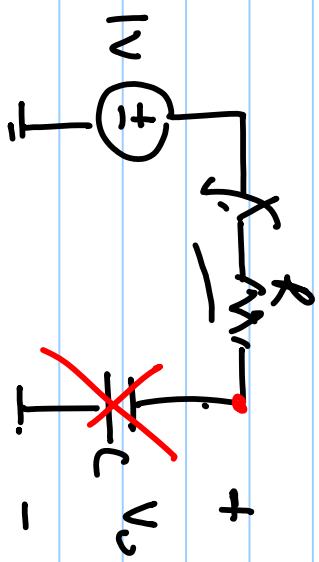at  $t \rightarrow \infty$ ,  $C \rightarrow$  open circuit



Voltage in steady state

At  $t \rightarrow \infty$   $V_o(t) :$

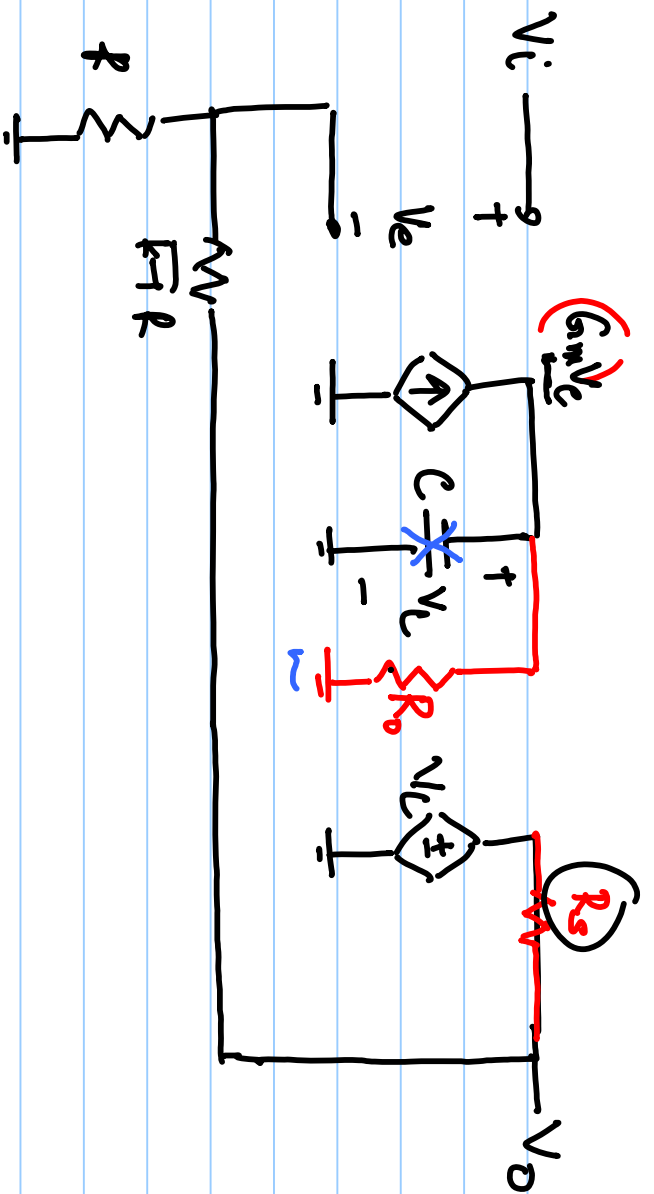

Ideally,

$$R_S \rightarrow 0$$

$$R_L \rightarrow \infty$$

1) What is  $V_o$  in steady state ✓

$$V_o = V_i - \frac{V_o}{k}$$

2) What is  $V_e$  in steady state.

$$V_o = V_i - \frac{V_i}{1 + \frac{k}{g_m R_o}}$$

#1  $R_o$  is finite,  $R_S = 0$


$$V_e = g_m V_e \cdot R_o = g_m R_o \left( V_i - \frac{V_o}{k} \right) = V_o$$

$$V_e = V_i \cdot \frac{1}{1 + \frac{k}{g_m R_o}} \rightarrow 0$$

$$V_o = \frac{V_i}{\left( \frac{1}{g_m R_o} + \frac{1}{k} \right)} = \frac{(k V_i)}{1 + \frac{k}{g_m R_o}} \rightarrow 0$$

$$V_o < k V_i$$
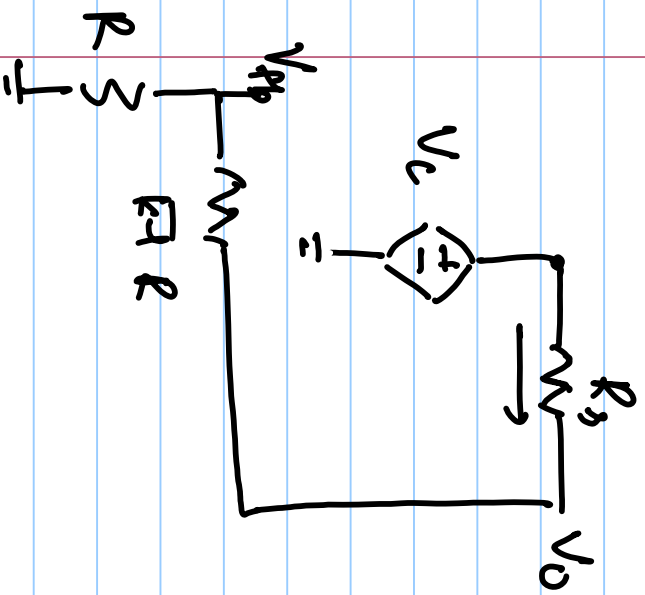
#2  $R_L \rightarrow \infty$ ,  $R_S$  is finite



$$V_i = V_{th}$$

$$V_i = V_c \cdot \frac{R}{R + (1 + \beta)R_S} = \frac{R}{\cancel{KR + R_S}} \cdot \frac{\cancel{KR} \cancel{R_S}}{KR} V_o$$

$$V_o = \frac{KR}{KR + R_S} \cdot V_c \quad \left. \vphantom{V_o} \right\} V_i = \frac{V_o}{\beta}$$