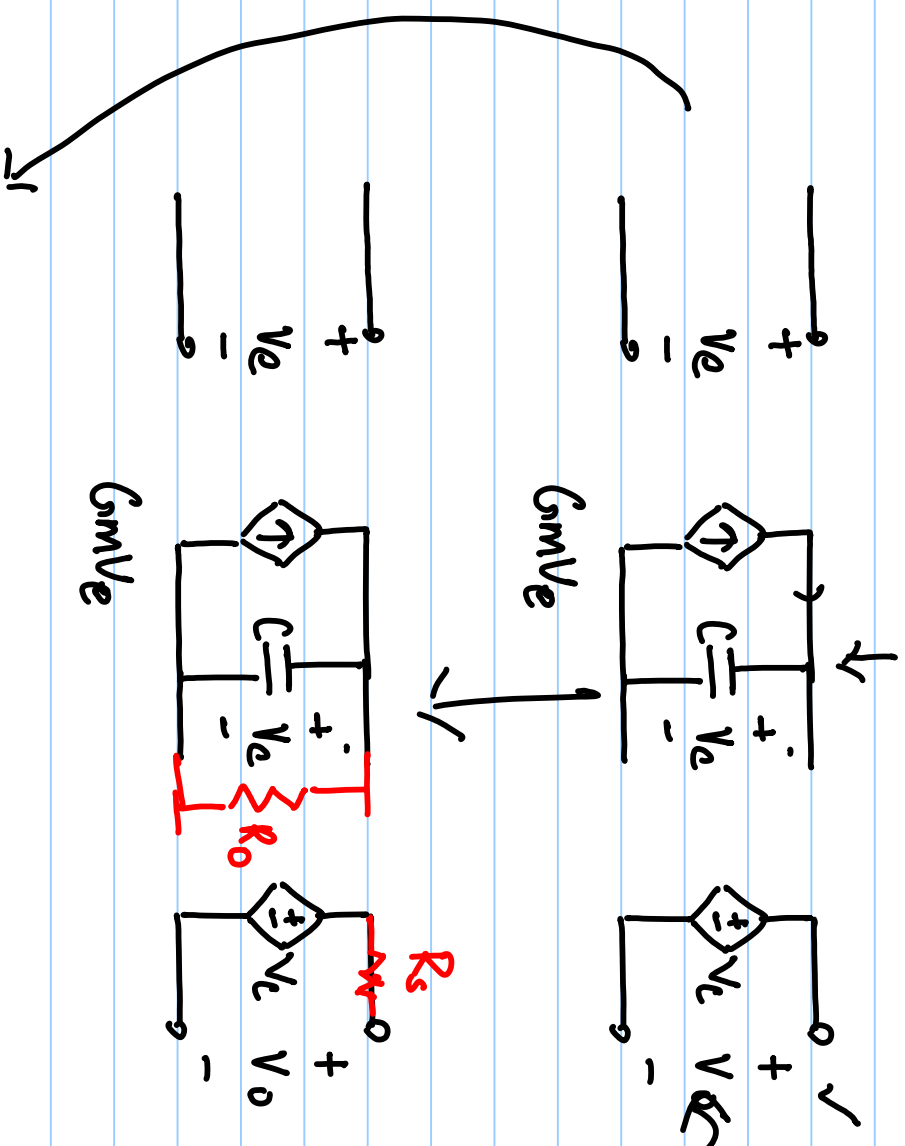



Lecture # 06

Ideal Operational Amp. (Opamp)




$$V_e(s) = G_m \cdot V_e(s) \times \frac{1}{sC}$$
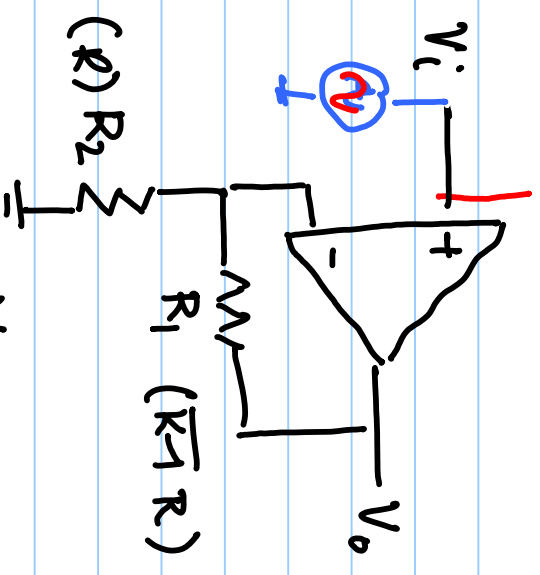
$$V_o(s) = \frac{G_m / C}{s} \cdot V_e(s)$$




$$\frac{V_o}{V_i} = R$$

$$V_e = \frac{1}{C} \int G_m V_e dt$$

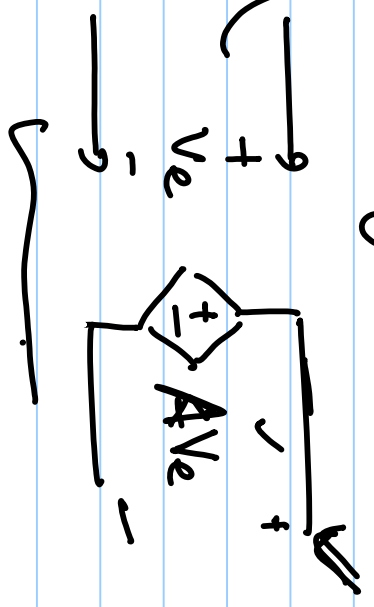


$$H(s) = \frac{V_o(s)}{V_e(s)} = \frac{(C_{in}/C)}{s}$$

$$20 \log_{10} |H(\omega)|$$

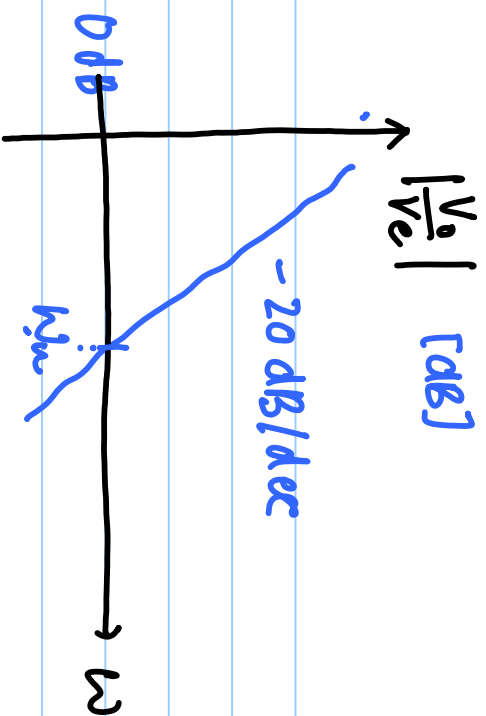

$$\omega_c = \frac{C_{in}}{C}$$

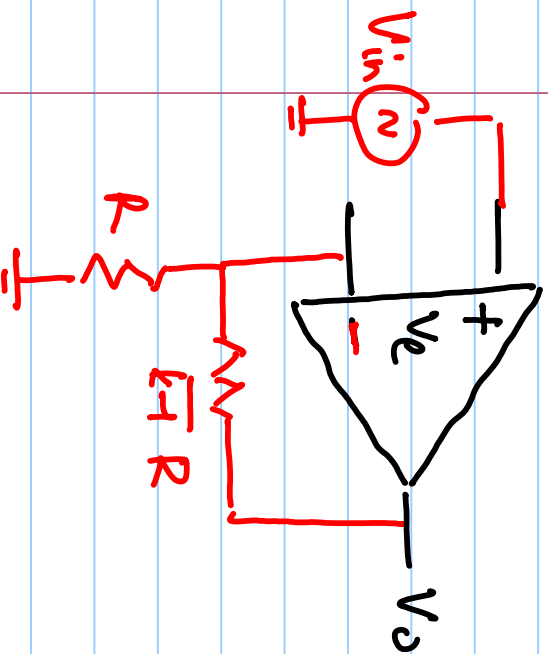

$$\frac{V_o(s)}{V_e(s)} = \frac{\omega_c}{s} \quad ; \quad \omega_c = \frac{C_{in}}{C}$$

$$V_e(s) = V_{in}(s) - \frac{1}{K} V_o(s)$$


$$V_o(s) = \frac{\omega_c}{s} V_e(s) = \frac{\omega_c}{s} \left(V_{in}(s) - \frac{V_o(s)}{K} \right)$$

$$V_o(s) \left(\frac{s}{\omega_c} + \frac{1}{K} \right) = V_{in}(s)$$

$$H(s) = \frac{V_o(s)}{V_{in}(s)} = \frac{1}{\frac{s}{\omega_n} + \frac{1}{k}} = \frac{k}{1 + \frac{s}{(\omega_n/k)}}$$

$$v_{in}(t) = a \sin(\omega_{in} t) \longrightarrow v_o(t)$$

$$v_o(t) = |H(\omega_{in})| a \sin(\omega_{in} t + \phi) = a |H(\omega_{in})| \sin(\omega_{in} t + \phi)$$

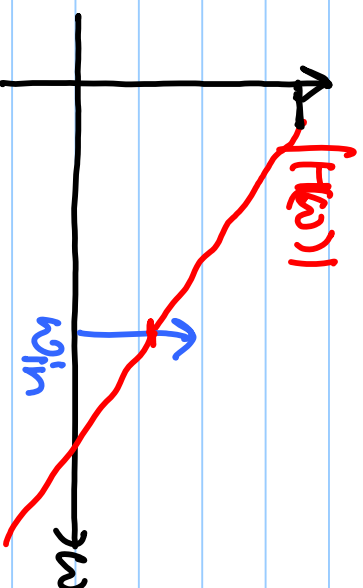


$$|H(j\omega_{in})| = \frac{k}{\left| 1 + j \frac{\omega_{in}}{\omega_n/k} \right|} = \frac{k^v}{\sqrt{1 + \left(\frac{\omega_{in}}{\omega_n/k} \right)^2}}$$

$$\angle H(j\omega_{in}) = -\tan^{-1} \left(\frac{\omega_{in}}{\omega_n/k} \right)$$

$$\omega_{in} \ll \frac{\omega_n}{k} \Rightarrow |H(j\omega_{in})| \approx k$$


$$\angle H(j\omega_{in}) \approx 0$$
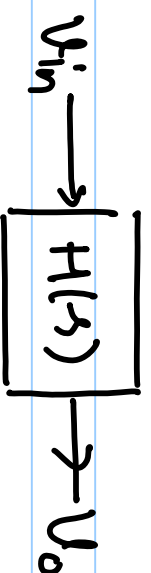
$$\phi = -\tan^{-1} \left(\frac{\omega_{in}}{\omega_n/k} \right)$$



$$V_o(s) = H(s) \cdot V_{in}(s)$$

$20 \log_{10} |H|$

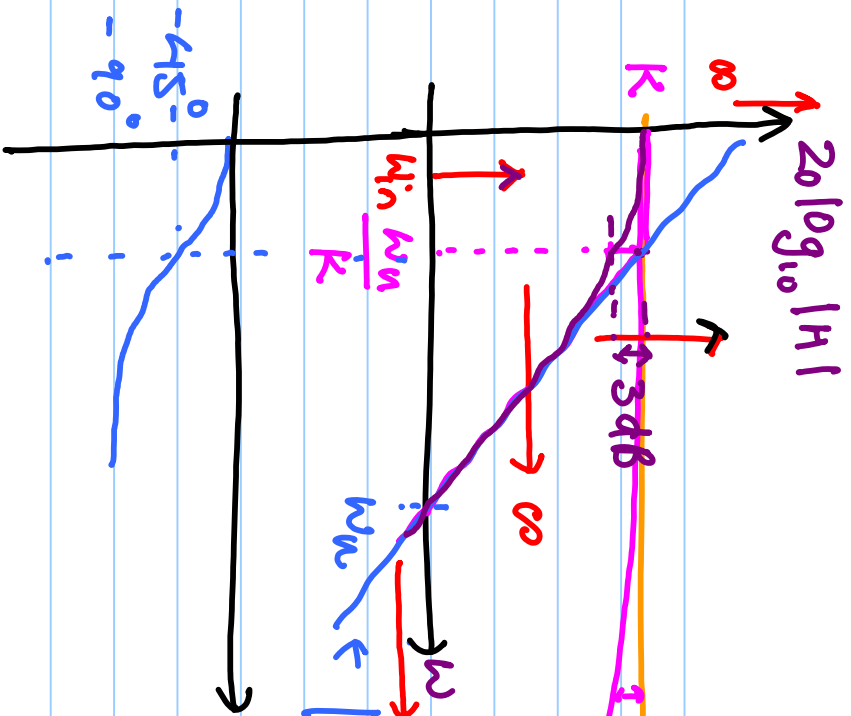


$$H(s) = \frac{K}{1 + \frac{s}{\omega_n/k}} \quad \checkmark \rightarrow \frac{K}{\omega_n' s} = \phi$$


$$\frac{\omega_n'}{\omega_n/k} \Rightarrow \omega_n' = \omega_n$$

$$\frac{V_o(s)}{V_e(s)} = \frac{\omega_n}{s}$$
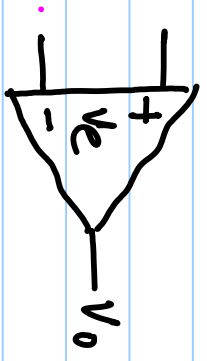
$$\frac{V_o}{V_e} = \frac{\omega_n'}{s} \rightarrow \infty$$




#1

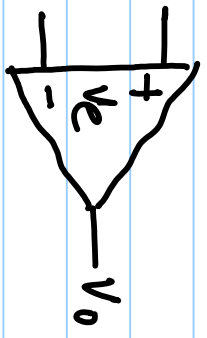


$$\frac{V_o}{V_e} = G_c \rightarrow \infty$$

#2

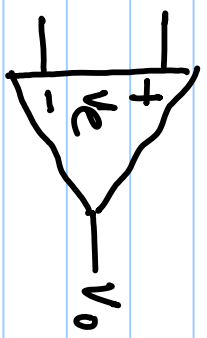

$$\frac{V_o}{V_e} = G_c \text{ (large)}$$

#3

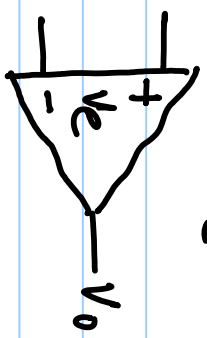


$$\frac{V_o}{V_e} = \frac{\omega_n}{s}$$


#3

$$\frac{V_o}{V_e} = G_c ; G_c \rightarrow \infty$$

#n

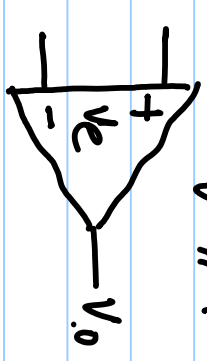
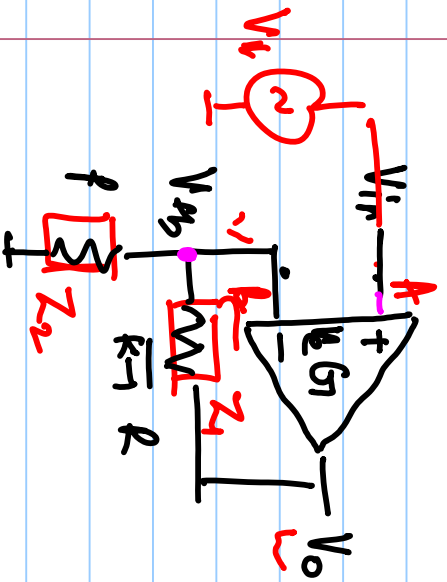
$$\frac{V_o}{V_e} = \frac{A_{dc}}{1+s/\omega_p}$$



$$a \left(V_{in} - \frac{V_o}{k} \right) = V_o$$

$$V_{in} = V_o \left(\frac{1}{k} + \frac{1}{a} \right)$$

$$V_e: V_{in} - \frac{V_o}{k} = \frac{V_o}{a}$$

$$\frac{V_o}{V_{in}} = \frac{k}{1 + \frac{k}{a}} = \frac{V_{in} (k/a)}{1 + k/a}$$

#1: $a \rightarrow \infty$

$$\frac{V_o}{V_{in}} = k, \quad V_e = 0 = V_{in} - V_{th}$$

$\Rightarrow V_{th} = V_{in} \rightarrow$ Virtually Short.

$$V_{th} = \frac{V_{z2}}{Z_1 + Z_2} \quad V_o = V_{in} \quad \checkmark$$

\checkmark

#3: $a = \frac{M_n}{S}$; $\frac{V_o}{V_{in}} = \frac{k}{1 + \frac{S}{M_n/k}} \xrightarrow{\beta=0} k \quad V_e = \frac{V_{in}}{1 + \frac{M_n}{k \cdot S}} \rightarrow 0$