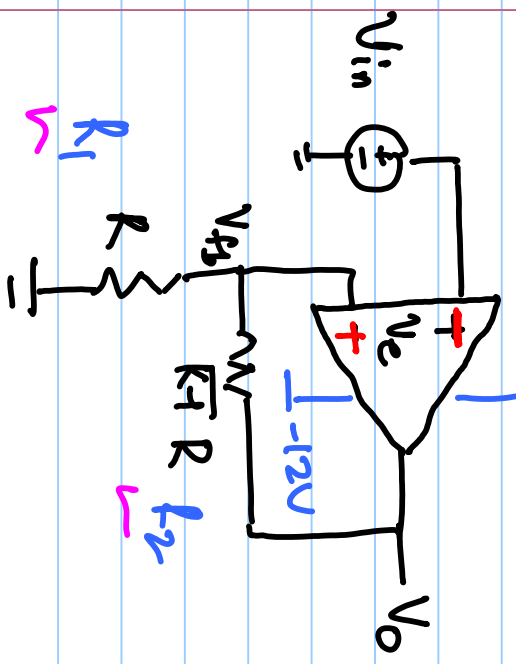


lecture # 08

'Schmitt Trigger'



$K=4,$

$V_{th} = \frac{V_o}{4}$

$V_e = V_{th} - V_{in}$

$V_e = \frac{V_o}{4} - V_{in}$

$V_o = A_0 V_e$

$V_e = \frac{-12 - V_{in}}{4}$

$V_e > 0$

$\rightarrow -3 - V_{in} > 0$

$\Rightarrow V_{in} < -3V$

$V_e = \frac{12 - V_{in}}{4}$

$V_e < 0$

$\rightarrow 3 - V_{in} < 0$



$V_{in} > 3$

$V_{th} = \frac{R_1}{R_1 + R_2} V_o$

\Rightarrow

$V_e = V_{th} - V_{in} =$

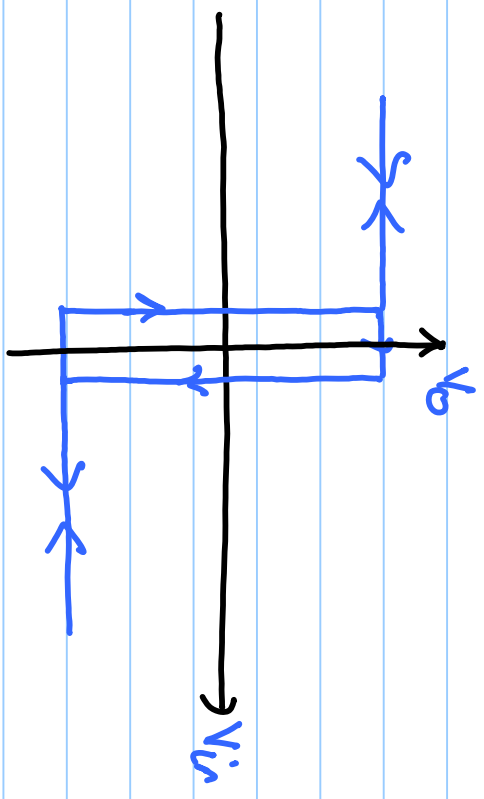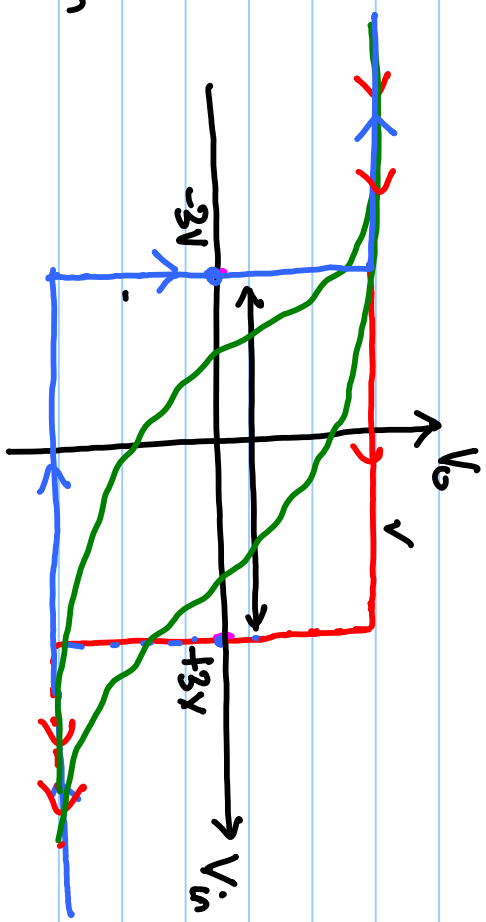$\frac{R_1}{R_1 + R_2} (12 - V_{in}) < 0$





$$\Rightarrow V_{in} > 12 \cdot \frac{R_1}{R_1 + R_2}$$

$V_{in} > 12$


$$1 + \left(\frac{R_2}{R_1}\right)$$

$$V_o = -12V, \quad V_i \geq 0$$


$$+12V, \quad V_i < 0$$

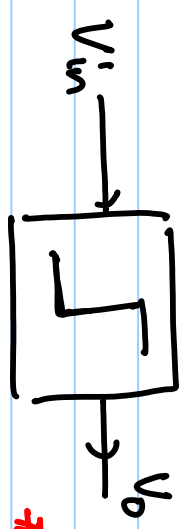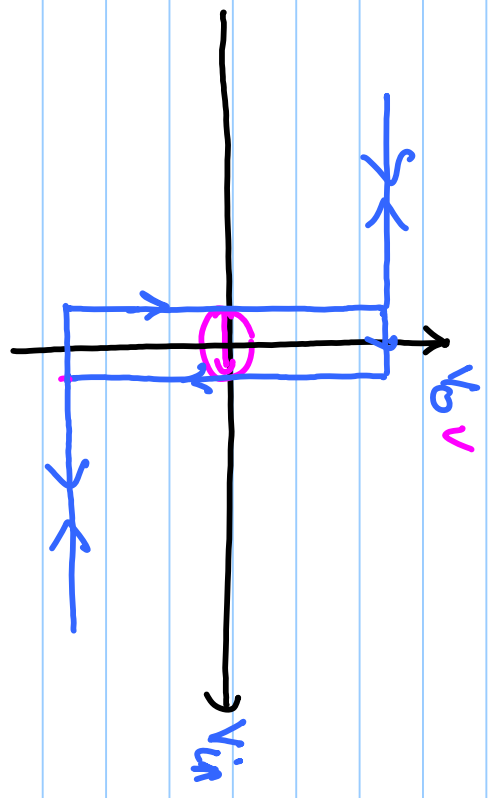


#2

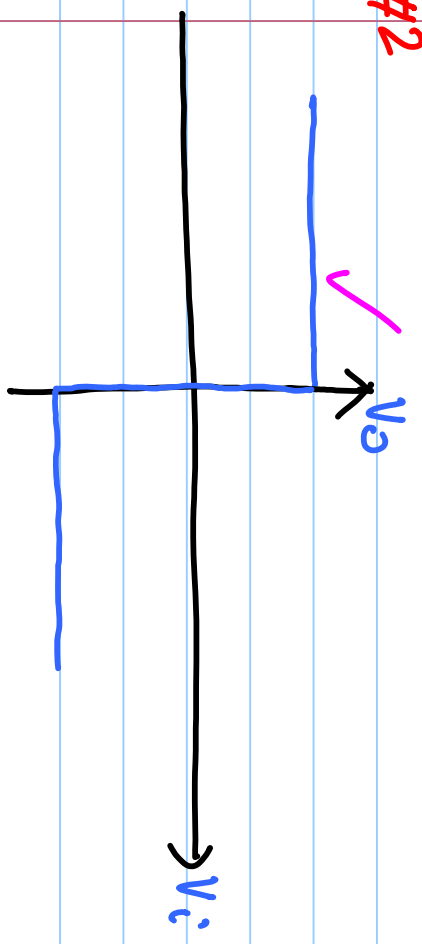




#1

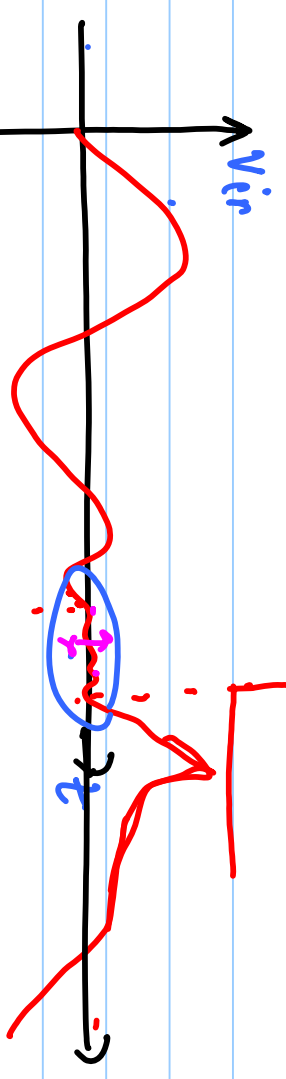

#2

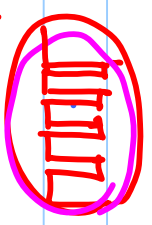
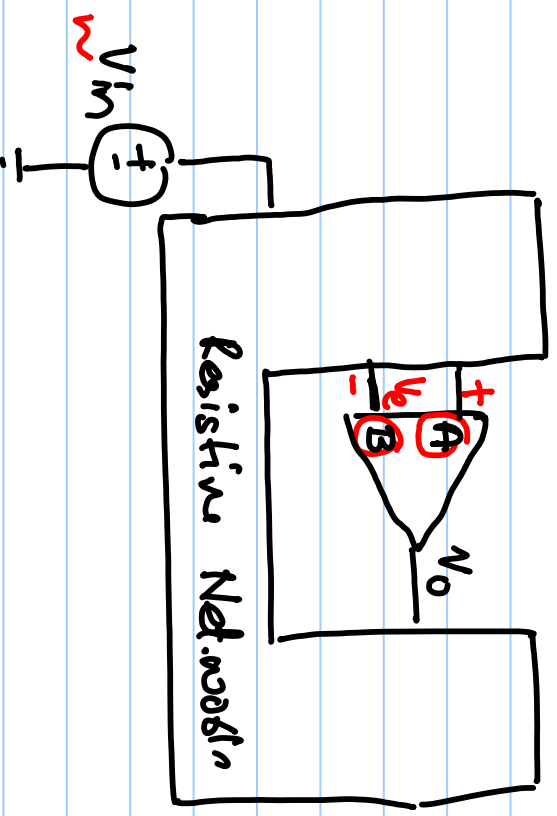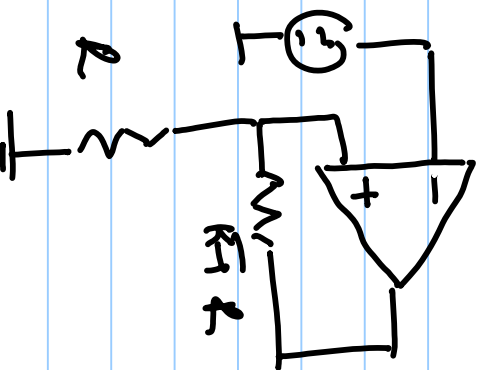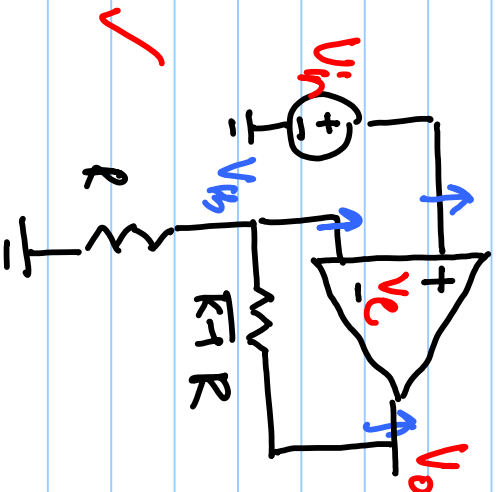
$$V_o = G_v V_e ; G_v \rightarrow \infty$$



$$V_e = \frac{V_o}{k} + V_{in}$$

$$V_e = \beta V_o + \alpha V_{in}$$

$$V_o = G_v V_e$$

where $G_v \rightarrow \infty$


$$V_e = \beta V_o$$

$$= V_A - V_B$$

$$= \frac{R_3}{R_3 + R_u} V_o - \frac{R_1}{R_1 + R_2} V_o$$

$\beta < 0$ \rightarrow neg. feedback
 $\beta > 0$ \rightarrow positive feedback

$$\Rightarrow V_e = 0.2 V_o$$

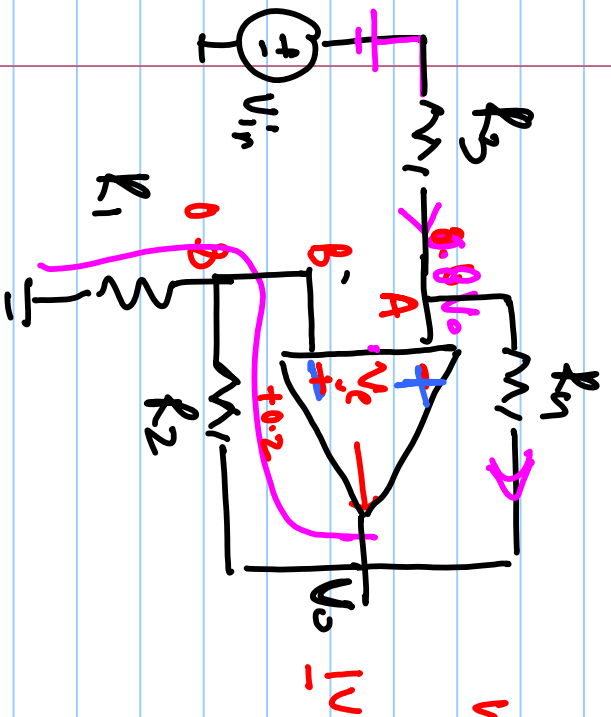

$$V_B = 0.8V_0$$

$$\frac{V_{in} - 0.8V_0}{R_3} = \frac{0.8V_0 - V_0}{R_4}$$

$$\Rightarrow \frac{R_3}{R_3 + R_4} < \frac{R_1}{R_1 + R_2} \quad \text{Neg. feedback.}$$

$$V_e = V_0 \left(\frac{R_3}{R_3 + R_4} - \frac{R_1}{R_1 + R_2} \right)$$

$$0.6 \quad 0.8$$

