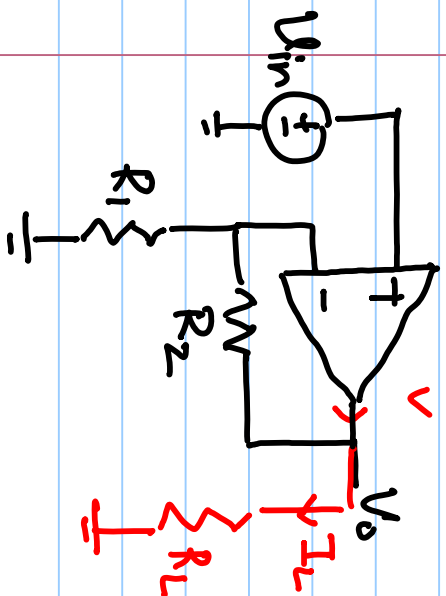


Lecture # 09




Non-inverting

$$\frac{V_0}{V_{in}} = \left(1 + \frac{R_2}{R_1}\right)$$

$$I_L = \frac{V_0}{R_L}$$

$$= \frac{(1 + R_2/R_1) V_{in}}{R_L}$$

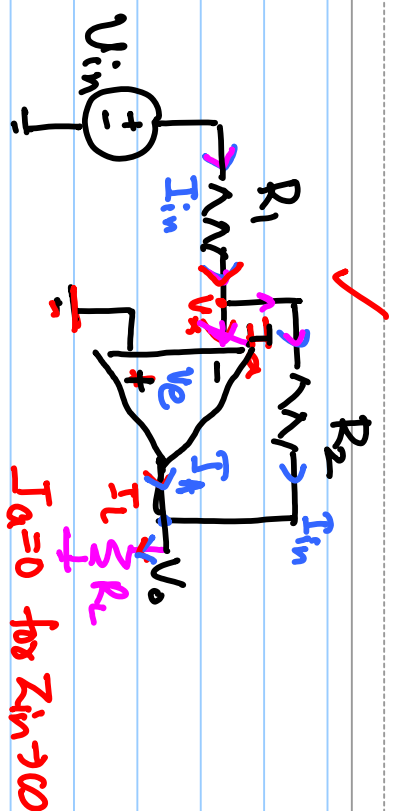

$$V_0 = A V_e$$

if $A \rightarrow \infty \xrightarrow{I_n - V_e \rightarrow 0} V_e = 0$


$\Rightarrow V_x = 0$, $V_e = 0 - V_x = 0$

$$\frac{V_{in} - V_x}{R_1} = -\frac{(V_0 - V_x)}{R_2}$$

$$\frac{V_0}{V_{in}} = -\frac{R_2}{R_1}$$

"Inverting"

$$V_x = \frac{R_1}{R_1 + R_2} V_0$$

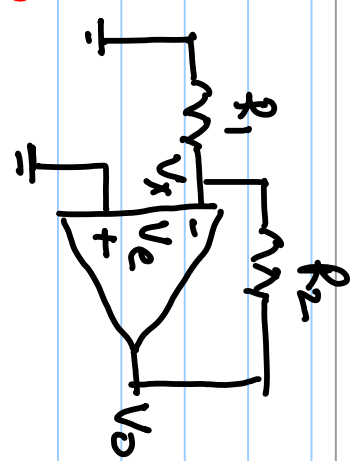


$$V_e = 0 - V_x = -\frac{R_1}{R_1 + R_2} V_0$$

$\underbrace{\hspace{10em}}_{B < 0}$

$$I_L = \frac{-R_2/R_1 V_{in}}{R_L}$$


"Buffer" "Unity Gain Config."

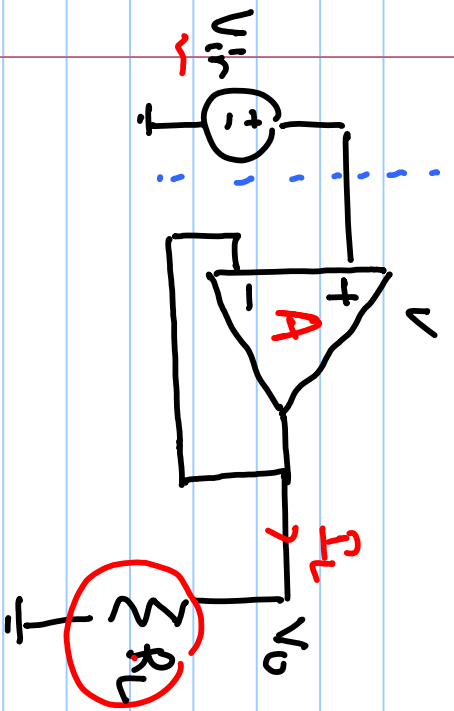

$$\frac{V_o}{V_{in}} = 1$$



$$(V_{in} - V_o) A = V_o$$

$$V_o = \frac{V_{in}}{1 + \frac{1}{A}}$$

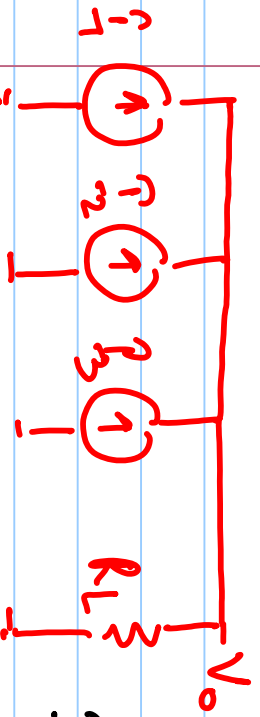


$$I_1 = \frac{V_1}{R_1} \Rightarrow$$

$$0 - V_o = \frac{V_o}{R_2} = I_1$$

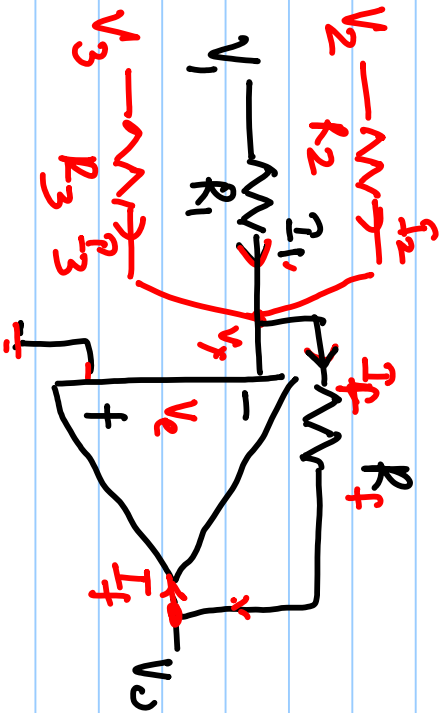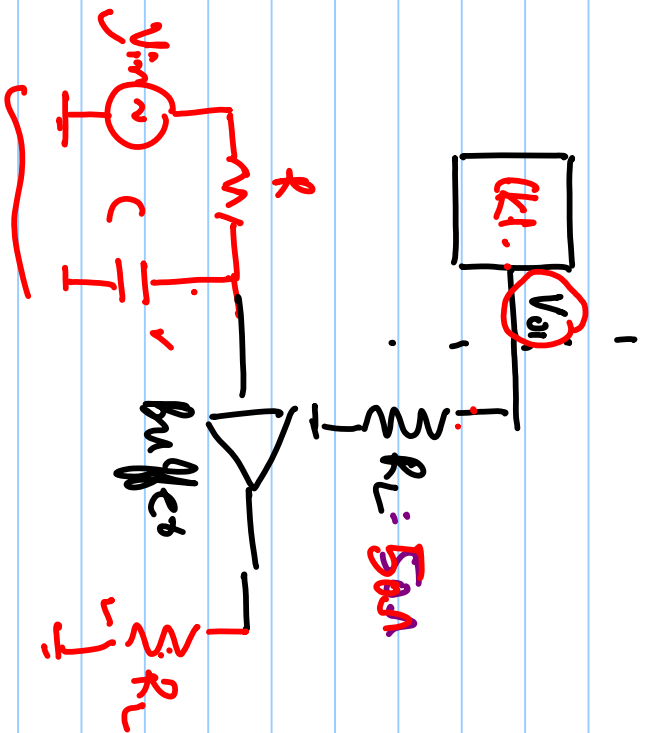

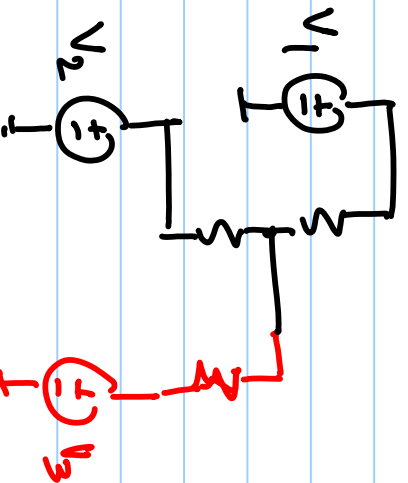
$$V_o = \alpha V_1 + \beta V_2 + \gamma V_3$$



$$I_L = I_1 + I_2 + I_3 = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}$$

$$I_L \times R_f = \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right) R_f = -V_o$$

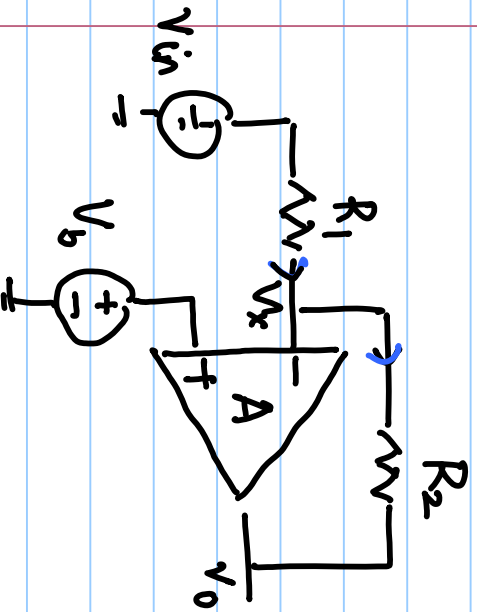
$$V_o = - \left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right)$$



$$\frac{V_{in} - V_x}{R_1} = \frac{V_x - V_o}{R_2}$$

$$A(V_b - V_x) = V_o$$
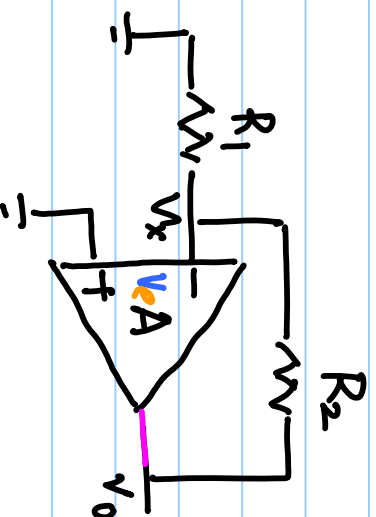
$$\frac{V_{in} - V_x}{R_1} = \frac{V_x - A(V_b - V_x)}{R_2}$$



$$V_c = V_f - V_- = 0 - \frac{R_1}{R_1 + R_2} V_o = \beta V_o$$




$\beta < 0$

$$V_{in} \cdot \frac{R_2}{R_1} = V_x \left(1 + \frac{R_2}{R_1} + A \right) - A \cdot V_b$$

$$V_x = \frac{V_{in} \cdot \frac{R_2}{R_1} + A V_b}{1 + \frac{R_2}{R_1} + A}$$

$$V_x = \frac{V_{in} \cdot R_2/R_1}{(1 + R_2/R_1 + A)} + \frac{V_b}{1 + (1 + R_2/R_1)/A}$$

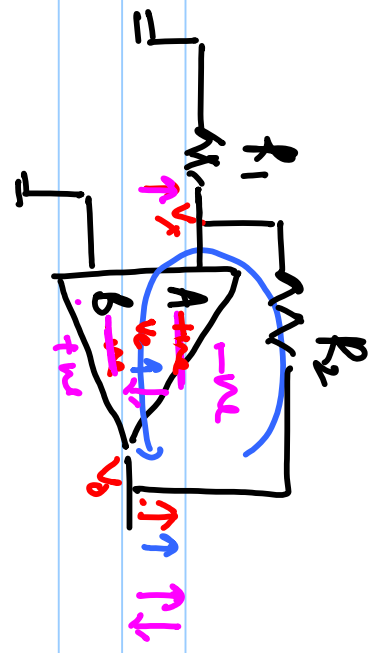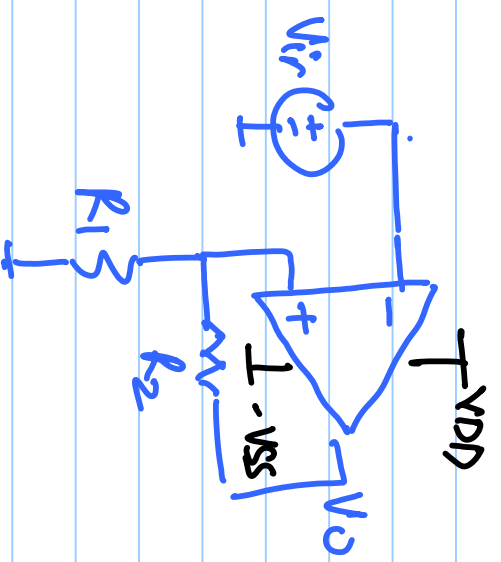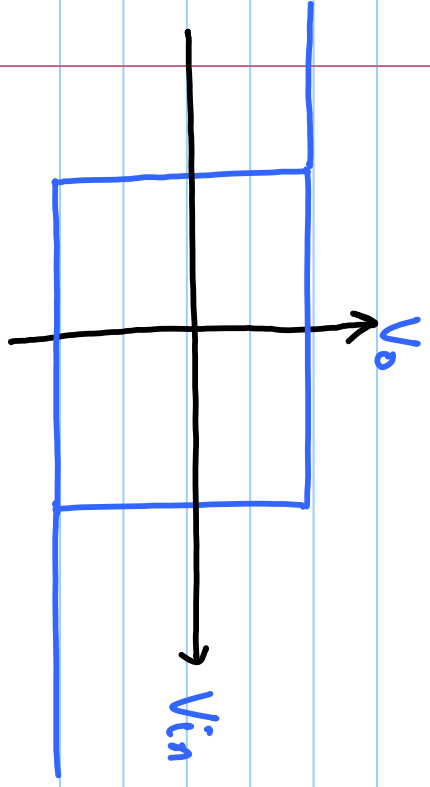if $A \rightarrow \infty$, $\left[V_x = V_b \right] \Rightarrow V_e = V_b - V_x = 0V$




A is +ve, B is -ve ✓


$$V_e = \beta \cdot V_o$$

A is +ve, B is +ve

$$V_e = \beta \cdot V_o$$

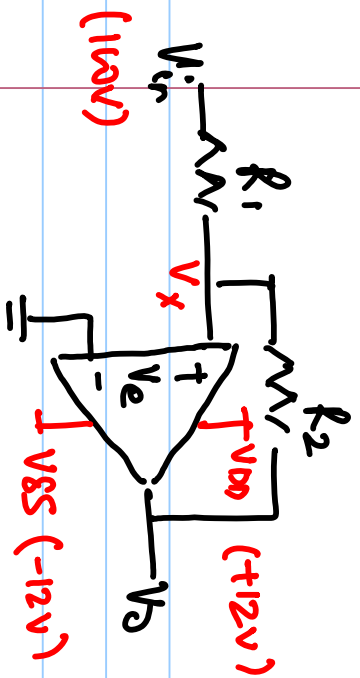

$$V_e = V_x$$

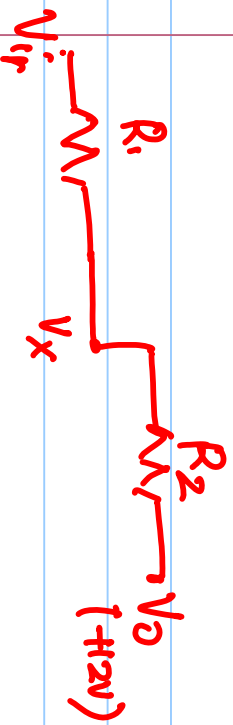


$$V_e = V_o = \frac{R_2}{R_1 + R_2} V_{in} + \frac{R_1}{R_1 + R_2} V_o$$

$$V_e = \frac{1}{R_1 + R_2} (R_2 V_{in} + R_1 V_o)$$

$$V_e < 0 \Rightarrow V_{in} < -\frac{R_1}{R_2} \times 12V$$

Non-inverting Hysteresis

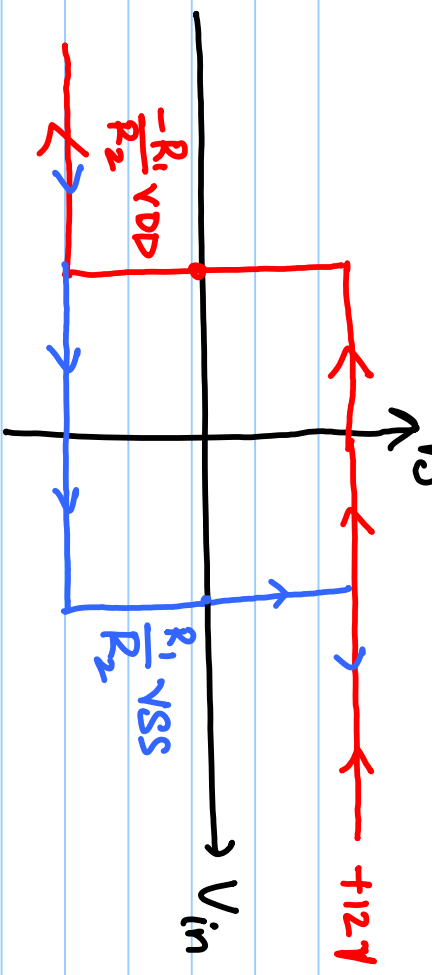

$$|V_{DD}| = |V_{SS}| = 12$$