

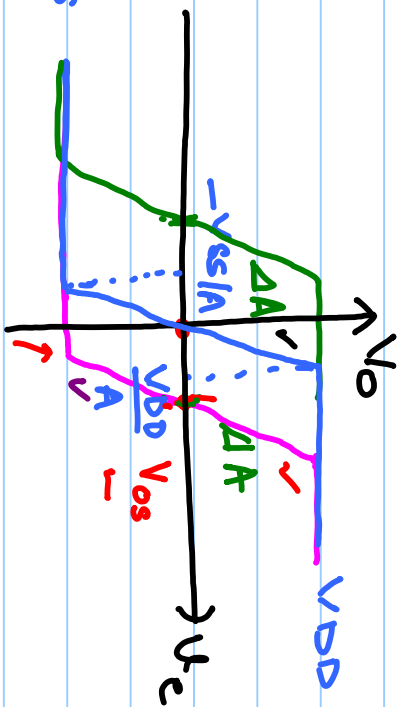


Lecture # 10

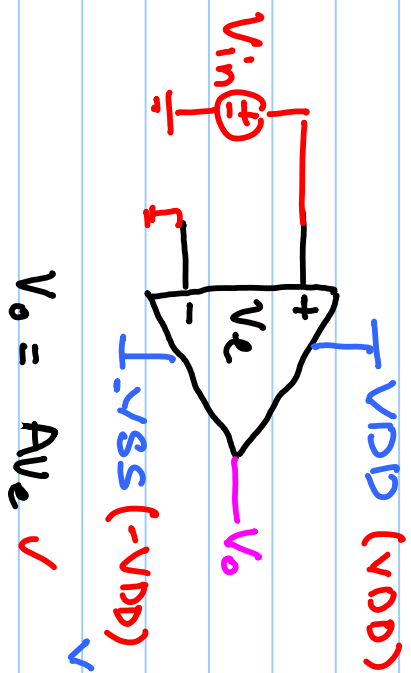


$V_e = V_{in}$



V_{os} : Input Offset Voltage.

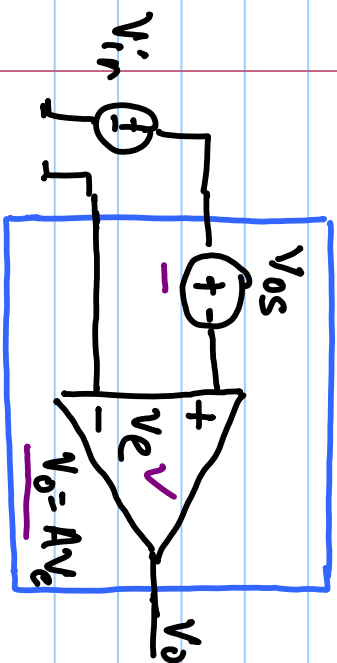

$V_e = V_{in} - V_{os}$

$V_o = A (V_{in} - V_{os}) = A V_e$

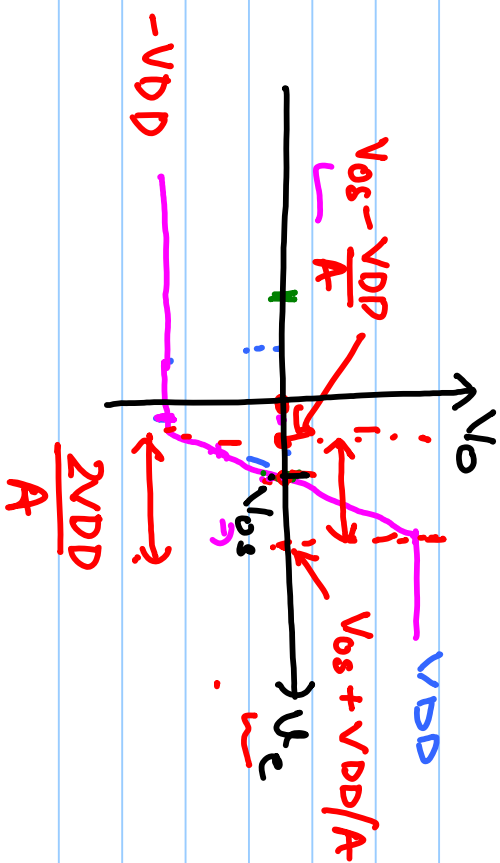

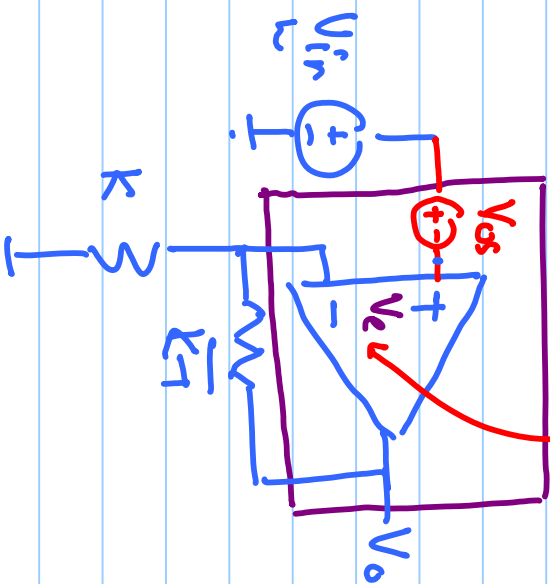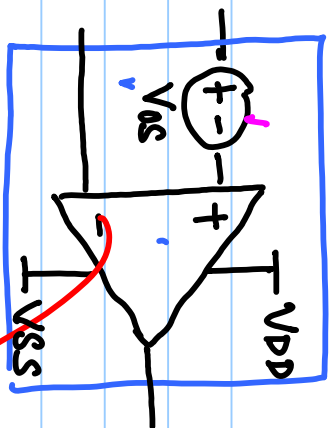


$$\frac{V_o}{V_{in}} = k$$

$$V_o = k V_{in}$$


$$(V_{in} - V_{os} - \frac{V_o}{k}) A = V_o$$

V_e

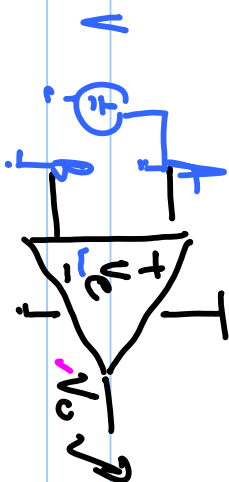
$$V_o = \frac{V_{in}}{\frac{1}{A} + \frac{1}{k}} - \frac{V_{os}}{\frac{1}{k} + \frac{1}{A}} = \frac{k V_{in}}{1 + k/A} - \frac{k V_{os}}{1 + k/A}$$




$$V_o = A V_e$$

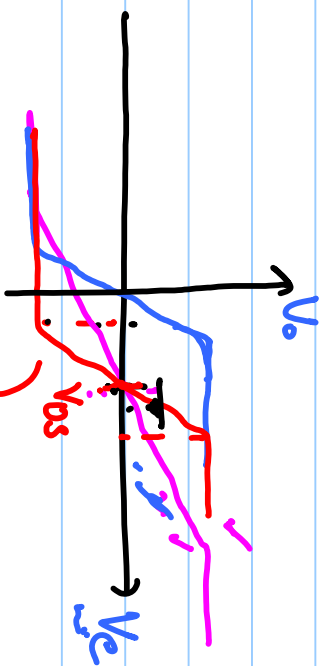

$$V_{os} = 0.5 V$$

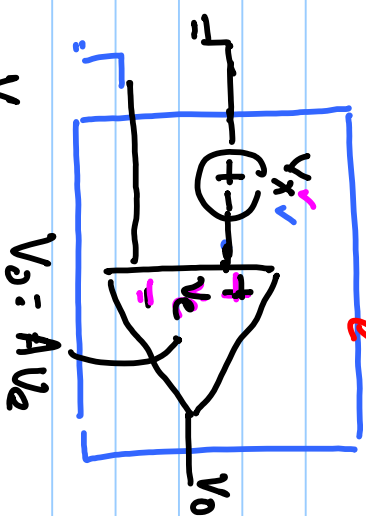

$$V_o = A V_e$$



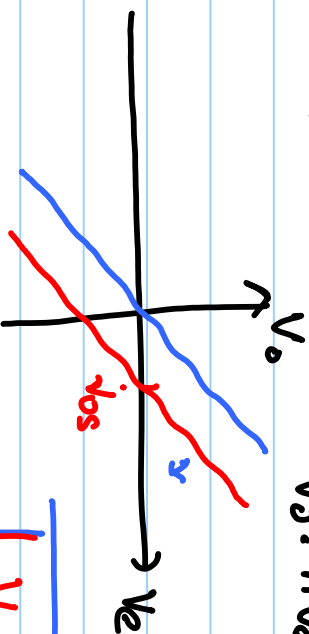


$$V_o = A V_e$$

$$V_o = A(V_e - V_{os})$$

$$V_o = A V_e - A V_{os}$$
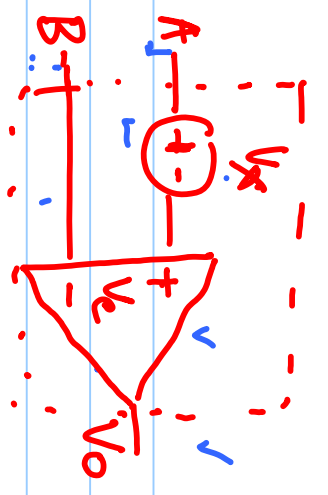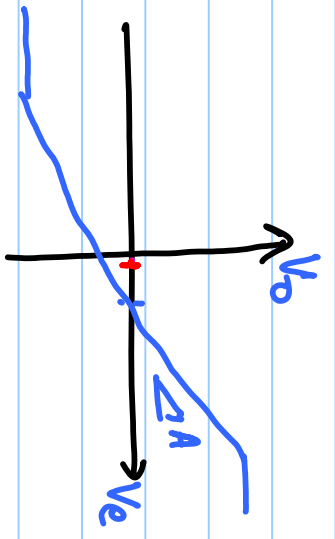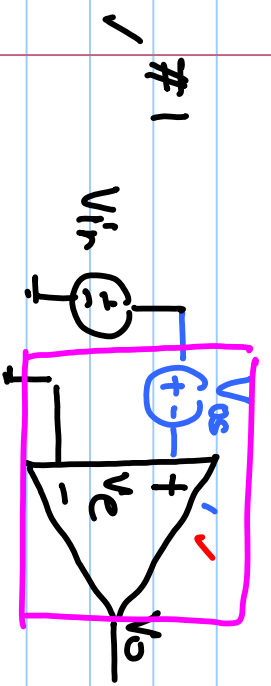
$$V_o = \frac{K V_{in}}{1+K/A} - \frac{K V_{os}}{1+K/A}$$




$$V_e = V_{AB} - V_A$$


$$V_o = A (V_{AB} - V_A)$$

$$V_o = A (V_{AB} - V_{os})$$

#2

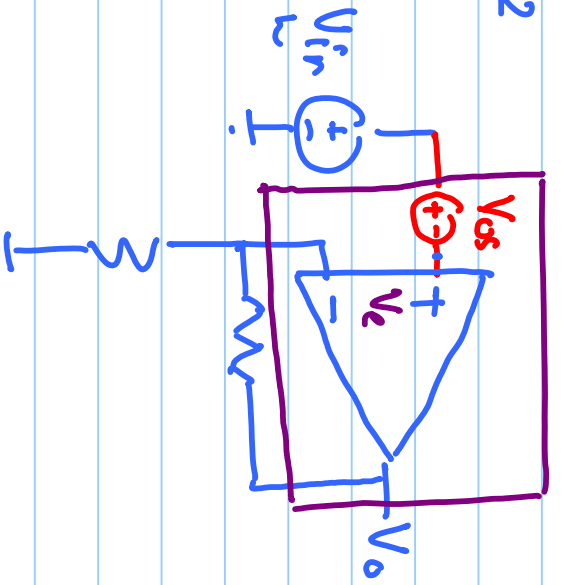

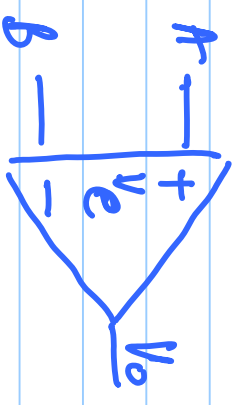
$$V_o = \frac{K V_{in}}{1+K/A} - \frac{K V_{os}}{1+K/A}$$




$$V_e = V_{AB}$$

"Offset Cancellation"

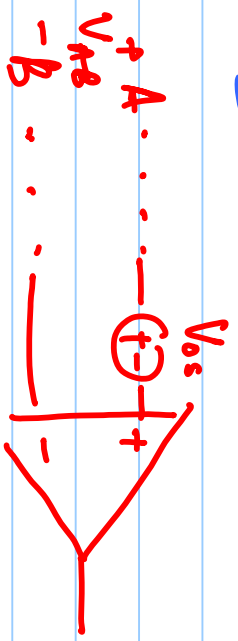

- Two supply voltages.

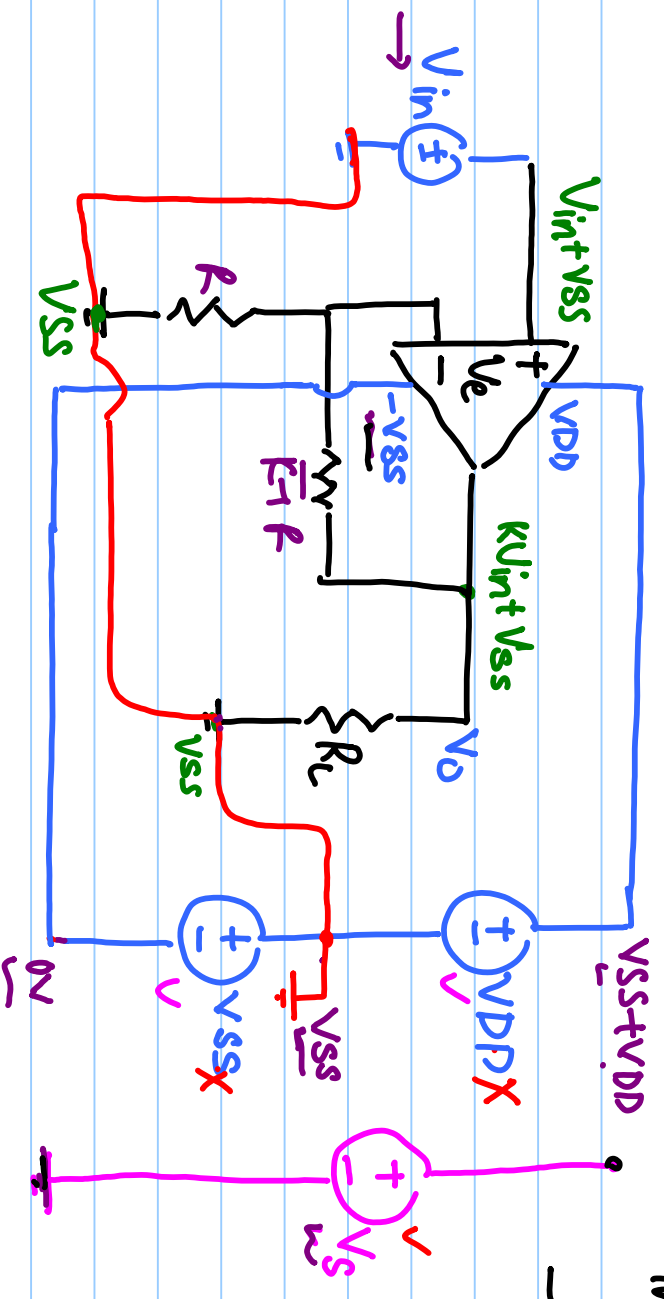

$$V_s = V_{SS} + V_{DD} \quad V$$

