
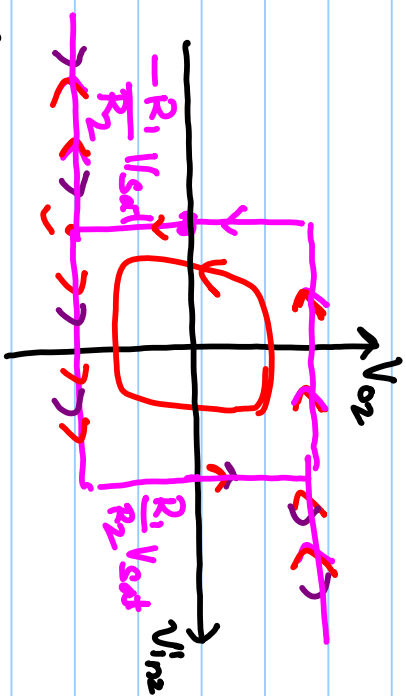


Lecture #14

"Oscillators"

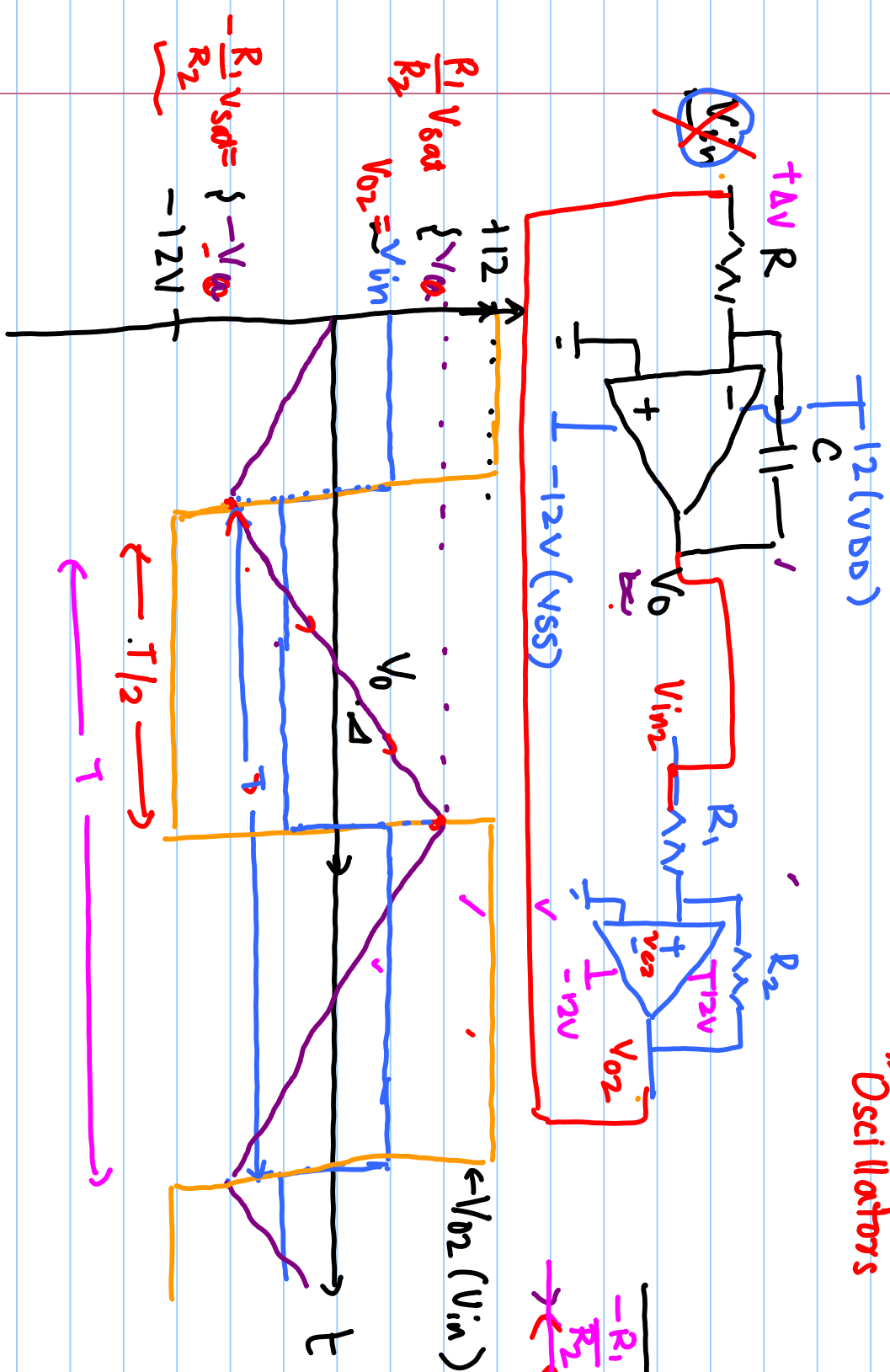

$$V_{o2} = -\frac{R_2}{R_1 + R_2} V_{in}$$

$$V_{o2} = 0$$

$$R_2 V_{in2} + R_1 V_{o2} = 0$$

$$\frac{V_{o2}}{V_{in2}} = -\frac{R_2}{R_1}$$

$$V_{in2} = -\frac{R_1}{R_2} V_{o2}$$

$$\frac{dV_o}{dt} = -\frac{1}{RC} V_{in}$$

$$-\frac{R_1}{R_2} V_{sat} = -\frac{V_o}{R}$$


$$V_{o2} = V_{in}$$

$$\frac{2R_1 V_{sat}}{R_2} \frac{V_{DD}/RC}{} = \frac{I}{2} \Rightarrow T = \frac{4R_1 RC}{R_2} \frac{V_{sat}}{V_{DD}}$$

$$T = \frac{4R_1 RC}{R_2} \quad \text{if } V_{sat} = V_{DD}$$

$$f = \frac{1}{T} = \frac{R_2}{4R_1 RC}$$

$$\frac{R_1}{R_2} V_{sat} < V_{DD}$$

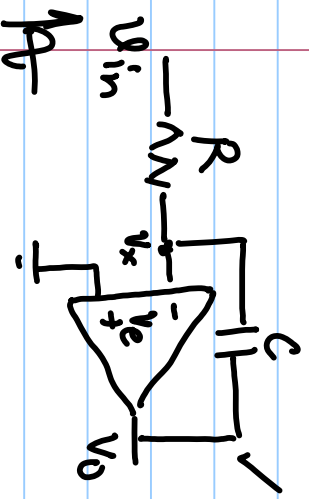

$$V_0 = A V_e, \quad \text{at } t=0, \quad V_0(t) = 0$$

$$V_{in} = a \sin(\omega_0 t)$$

$$\frac{V_{in} - (-V_e)}{R} = C \frac{d(-V_e - V_0)}{dt} \Rightarrow \frac{V_{in} + \frac{V_0}{A}}{R} = -C \frac{d(V_0 + \frac{V_0}{A})}{dt}$$

$$\frac{dV_0}{dt} + \frac{V_0}{(1+A)RC} = \frac{-V_{in}}{RC(1+\frac{1}{A})}$$

$$V_o(t) = e^{-t/RC(1+A)} \int \frac{-a \sin(\omega_0 t)}{RC(1+A)} e^{t/RC(1+A)} dt + K e^{-t/RC(1+A)}$$

"Integration by parts"

$$V_o(t) = \frac{-aA}{RC(1+A)} \left[\frac{RC(1+A)}{1+(\omega_0 RC(1+A))^2} \sin(\omega_0 t) - \frac{\omega_0 (RC(1+A))^2}{1+(\omega_0 RC(1+A))^2} \cos(\omega_0 t) \right] + K e^{-t/RC(1+A)}$$

$$V_o(t) = \frac{-aA \sin(\omega_0 t)}{1+(\omega_0 RC(1+A))^2} + \frac{aA \omega_0 (RC(1+A))^2}{1+(\omega_0 RC(1+A))^2} \frac{1}{RC} \left\{ \cos(\omega_0 t) - e^{-t/RC(1+A)} \right\}$$

A → ∞

$$V_o(t) = 0$$

$$H(s) = \frac{V_o}{V_{in}} = \frac{-1}{sRC} = -\frac{1}{j\omega RC}$$

$$V_{in} \xrightarrow{[H(s)]} V_o \checkmark$$

$$\angle H(j\omega_0) = \angle \left(\frac{-1}{j\omega_0 RC} \right)$$

$$V_o = V_{in} \underline{H(s)}$$

$$v_{in}(t) = a \sin(\omega_0 t)$$


$$= +180^\circ - 90^\circ = 90^\circ$$

$$v_o(t) = a |H(j\omega_0)| \sin(\omega_0 t + \angle H(j\omega_0))$$

$$\angle \left(\frac{-1}{j^2 \omega_0 RC} \right) = \angle \left(\frac{-j}{\omega_0 RC} \right)$$

$$= \frac{a}{\omega_0 RC} \sin(\omega_0 t + 90^\circ)$$
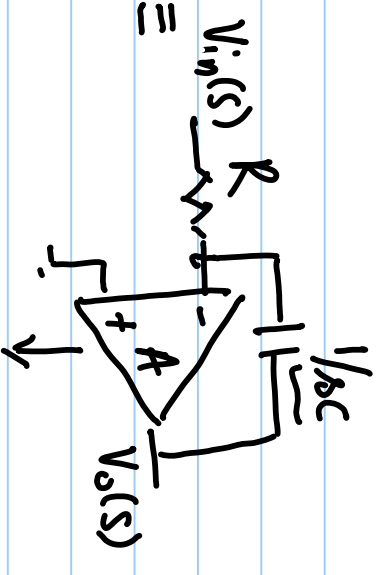
$$= \frac{a}{\omega_0 RC} (\sin(\omega_0 t) \cdot \cos 90^\circ + \sin 90^\circ \cdot \cos(\omega_0 t))$$



$$\frac{v_{in}(t)}{R} = -C \frac{dv_o}{dt}$$

$$\frac{V_{in}(s)}{R} = -\frac{V_o(s)}{1/sC}$$

$$\frac{V_o}{V_{in}} = \frac{-1}{sRC}$$

$$\int_{-\infty}^t i(t) \frac{C}{RC} dt = \int_{-\infty}^t i(t) dt + V_0(s) \quad I(s) = \int i(t) e^{-st} dt$$

$$i(t) = C \frac{dV_0}{dt}$$

$$I(s) = C (sV_0(s))$$

$$V_0(s) = \frac{1}{sC} \cdot I(s)$$

$$\frac{V_{in}(s) + V_0(s)}{R} = \frac{-V_C(s) - V_0(s)}{1/sC}$$

$$\frac{V_{in}(s) + \frac{V_0(s)}{A}}{R} = -V_0(s) \left(1 + \frac{1}{A}\right)$$

$$\frac{1}{1/sC}$$

$$V_{in}(s) = -V_o(s) \left\{ sRC \left(1 + \frac{1}{A} \right) + \frac{1}{A} \right\}$$

$$\frac{V_o(s)}{V_{in}(s)} = \frac{-1}{sRC \left(1 + \frac{1}{A} \right) + \frac{1}{A}} \quad \xrightarrow{A \rightarrow \infty} \quad \frac{-1}{sRC}$$

