
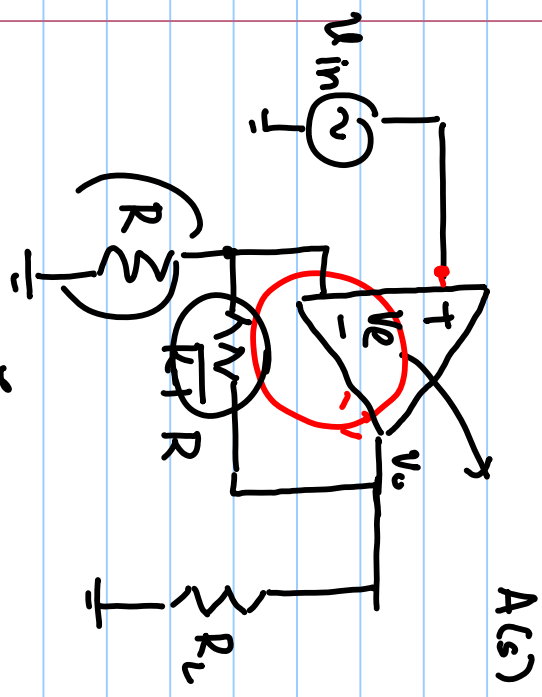


Lecture # 15

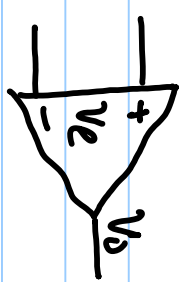


AC(s)

'standalone Amp'


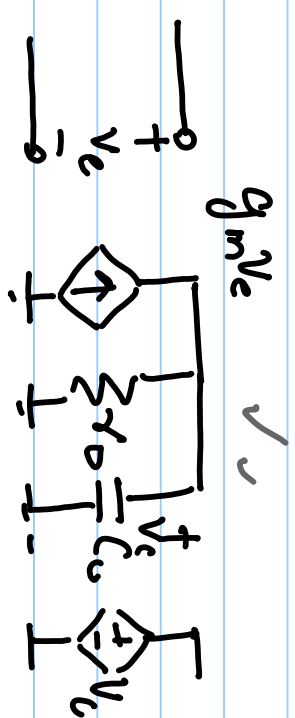
$$AC(s) = \frac{V_o}{V_e} = \frac{A_o}{1 + s/p_1}$$



$g_m v_e$ ✓

$$A_o = g_m r_o$$

$$p_1 = \frac{1}{r_o C_o}$$

$$\frac{V_o}{V_e} = g_m (r_o || r_{\omega s})$$

$$= \frac{g_m r_o}{1 + s C_o r_o}$$

$$\left[V_{in}(s) = \frac{V_o(s)}{k} \right] A(s) = V_o(s)$$

$$v_{in}(t) \xrightarrow{k} v_{in}(s)$$

$$v_o(t) \xrightarrow{k} v_o(s)$$

$$\frac{V_o(s)}{V_{in}(s)} = \frac{k}{1 + \frac{k}{A(s)}} = \frac{k}{1 + \frac{k}{A_o}} = \frac{1 + \frac{k}{A_o}}{1 + \frac{k}{A_o}} = \frac{1}{1 + \frac{k}{A_o}}$$


$$H(s) = \frac{V_o(s)}{V_{in}(s)} = \frac{k}{1 + \frac{k}{A_o}} \frac{1}{p_1 \left(1 + \frac{A_o}{k}\right)}$$

$$= A_{dc} \frac{1}{1 + s/\omega_p}$$

$$|H(j\omega)| = \frac{k}{1 + \frac{k}{A_o}} \approx k$$

$$\omega_u = A_{dc} \cdot \omega_p = k \cdot \frac{A_o p_1}{k} = A_o p_1$$

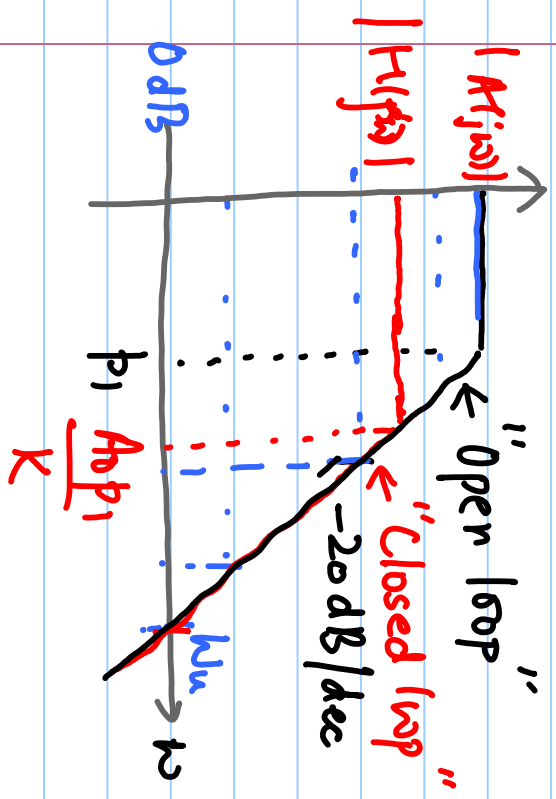Where $A_{dc} = \frac{k}{1 + k/A_o}$, $\omega_p = p_1 \left(1 + \frac{A_o}{k}\right) \approx \frac{A_o p_1}{k}$
 $s_1 = -\omega_p$ (L.N.P)



$$A(s) \approx \frac{A_o}{1 + s/p_1}$$

$\omega_u \approx A_o p_1$

$$20 \log_{10} |A(j\omega)| : @ \omega = 0 \quad 20 \log_{10} |A_o|$$

$$@ \omega = j p_1 \Rightarrow 20 \log_{10} \left(\left| \frac{A_o}{1+j} \right| \right)$$

Gain x bandwidth = Constant.

$$|A(j\omega_u)| = 1 = \left| \frac{A_o}{1 + j \frac{\omega_u}{p_1}} \right| \approx \left| \frac{A_o}{j \frac{\omega_u}{p_1}} \right|$$


$A_o \times p_1 = A_o p_1 \approx \omega_u$ open loop $\Rightarrow \omega_u = A_o p_1$

$$K \times \frac{A_{0p}}{K} = A_{0p} \quad \text{closed loop}$$

$$H(s) = \frac{A_0}{1 + s/p_1} \quad \checkmark$$

-3 dB bandwidth (BW) is frequency at which $|H(j\omega)| = \frac{1}{\sqrt{2}} |H(0)|$


$$\omega_{-3dB} = p_1$$

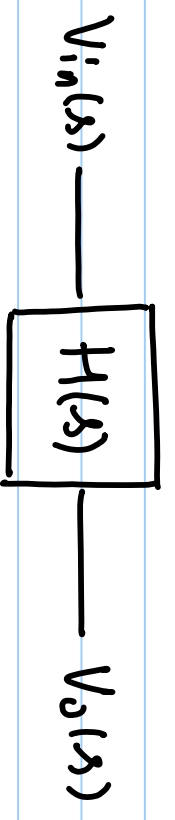

$$V_o(s) = V_{in}(s) H(s)$$

$$V_o(t) = \mathcal{L}^{-1} \{ V_o(s) \}$$
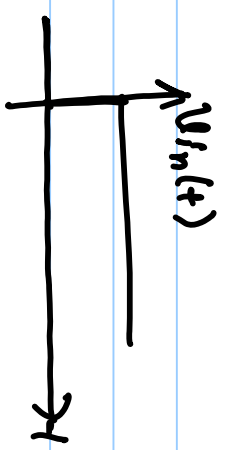
$$= \mathcal{L}^{-1} \{ V_{in}(s) H(s) \}$$



$$V_{in}(t) = \frac{V_{in}(0)}{s} u(t)$$

$$V_{in}(s) = \frac{V_{in}(0)}{s}$$

$$V_o(s) = \frac{V_{in}(0)}{s} \times \frac{A_{DC}}{1 + s/\omega_p}$$

$$V_o(t) = \mathcal{L}^{-1} \left\{ \dots \right\}$$

$$\frac{V_{in}(0)}{s} \times \frac{A_{DC}}{1 + s/\omega_p} = \frac{P}{s} + \frac{Q}{s + \omega_p}$$

$$u_o(t) = \mathcal{L}^{-1} \left\{ \underbrace{\frac{A_{DC}}{s}} + \frac{-A_{DC}}{s + \omega_p} \right\}$$


$$= [A_{DC} u(t) - A_{DC} e^{-\omega_p t} u(t)] u_{in}(0)$$

$$\omega_p = \frac{A_0 p_1}{T}$$

$$\frac{dV_o}{dt} = \frac{k}{1+K} u_{in}(0) e^{-\omega_p t}$$

$$= A_{DC} (1 - e^{-\omega_p t}) u_{in}(0) u(t)$$
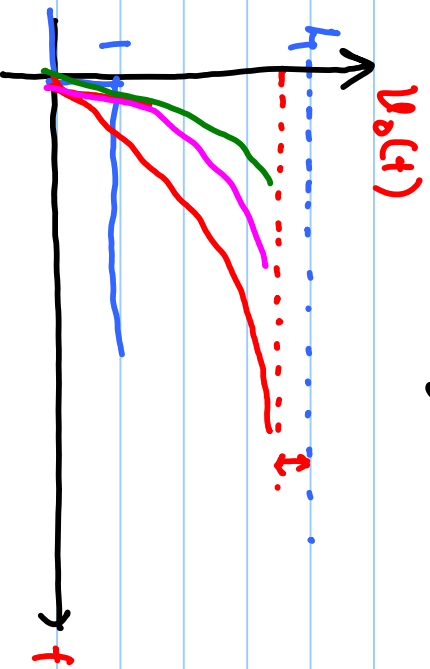
$$\approx \frac{k}{1+K} u_{in}(0) (1 - e^{-\omega_p t}) u(t)$$



$$E_S = \frac{V_o^{ideal}(t \rightarrow \infty) - V_o(t \rightarrow \infty)}{V_o^{ideal}(t \rightarrow \infty)}$$

$$= \frac{k - k/(1+K/A_0)}{k} = 1 - \frac{1}{1+K/A_0}$$

$$= \frac{(A_0/K)^{-1}}{1+(A_0/K)^{-1}} = \frac{1+K/A_0}{1+K/A_0} \checkmark$$