
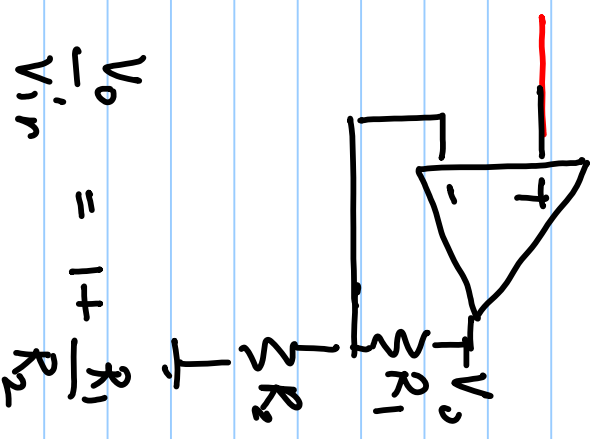

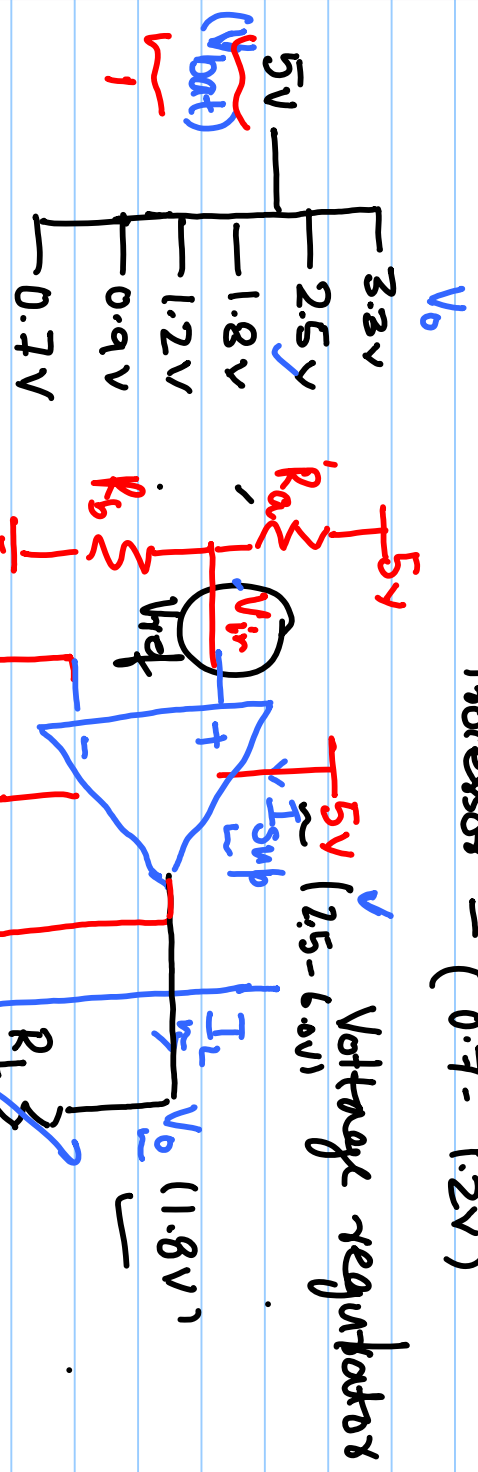
# Lecture # 23


cell phone : (5V)   
 Transmitter / Receiver (3.3V, 1.8V, 0.9V)   
 Audio / Video   
 GPS   
 Processor - (0.7 - 1.2V)




$$\frac{V_0}{V_{in}} = 1 + \frac{R_1}{R_2}$$



$$\frac{V_0}{V_{in}} = 1 \Rightarrow V_0 = \frac{R_b}{R_b + R_a} V_{bat}$$
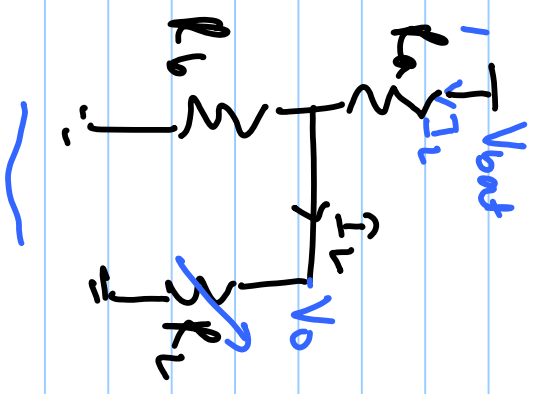
$$\text{Power Efficiency} = \frac{\text{Power delivered to load}}{\text{Power drawn from supply}}$$




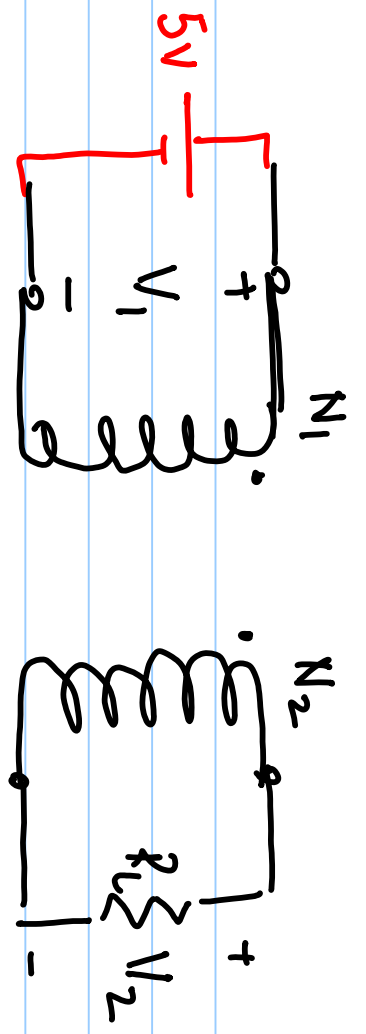


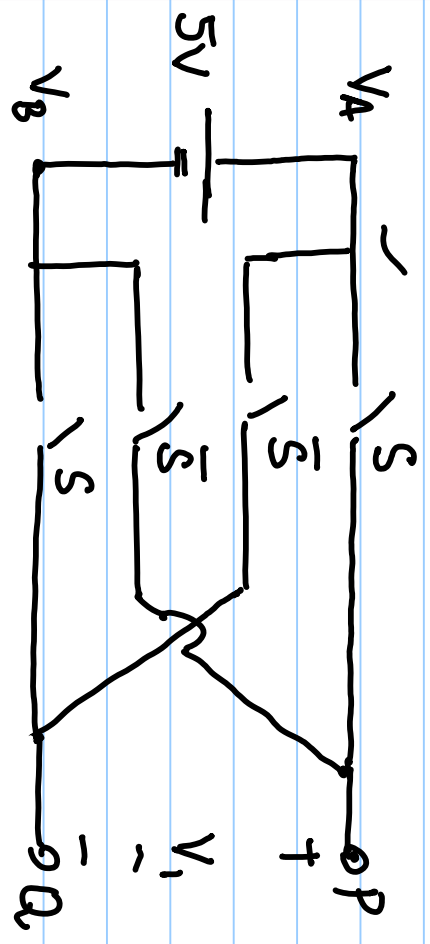
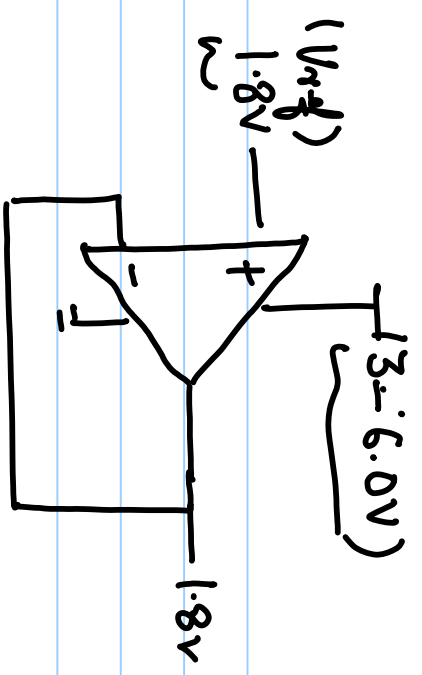
$$\frac{V_1}{N_1} = \frac{V_2}{N_2} \Rightarrow V_2 = \frac{N_2}{N_1} \cdot V_1$$



$$V_1 = V_P - V_Q$$



$$5V = V_A - V_B$$

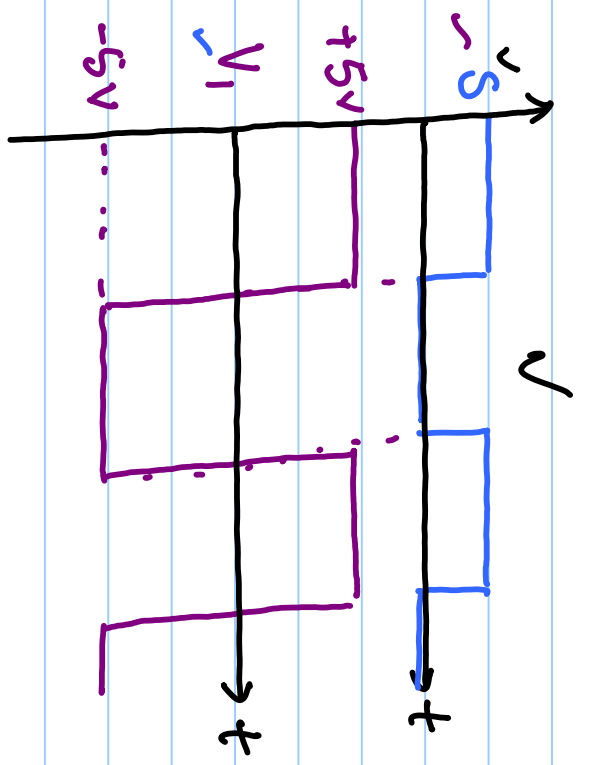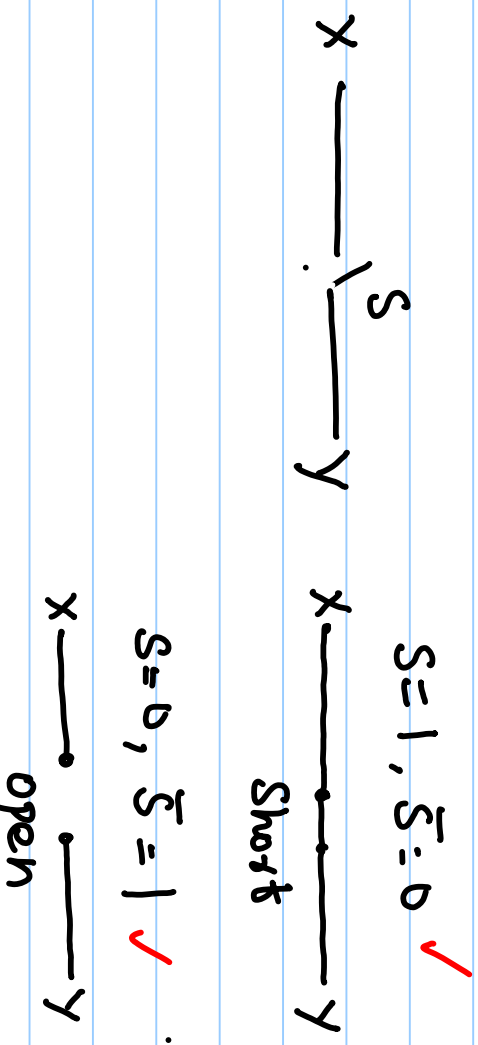


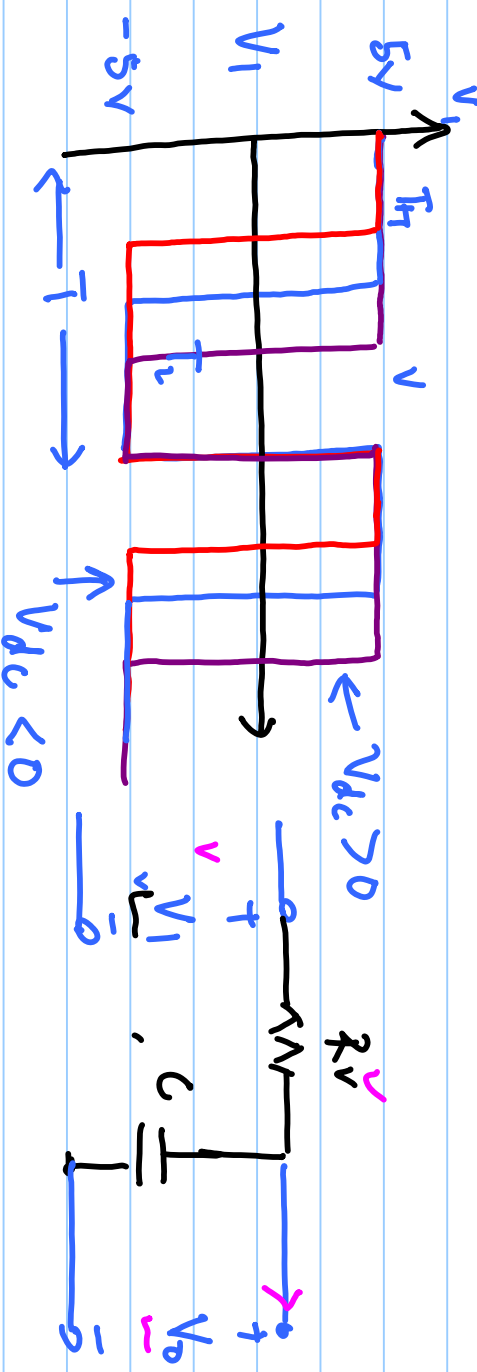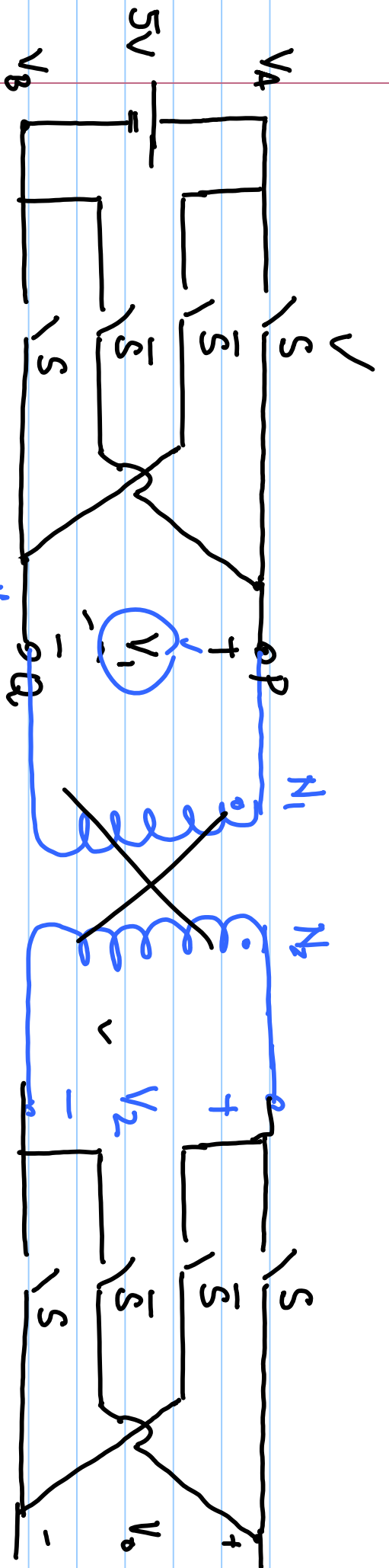


$$\frac{I}{2} = T_H = T_L$$
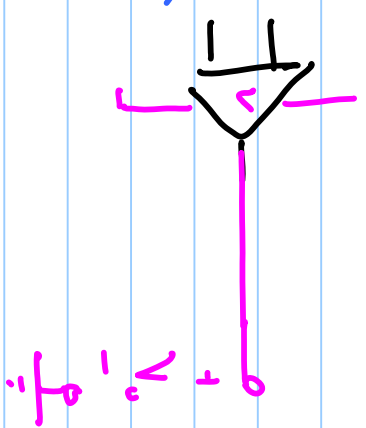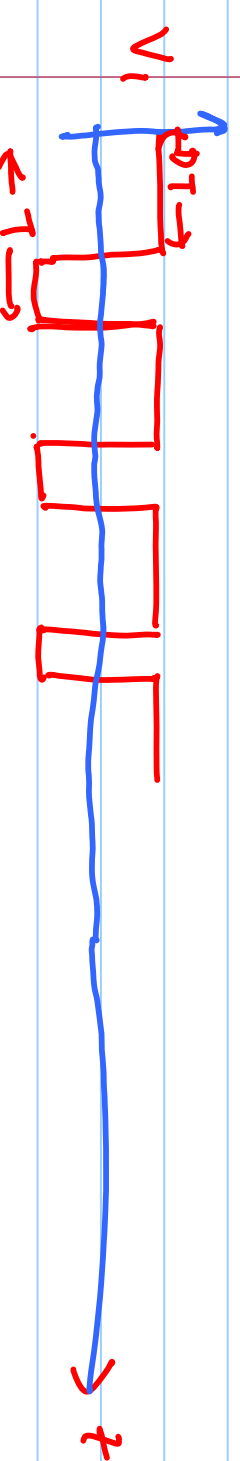
$$\text{Duty Cycle (D)} = \frac{T_H}{T_H + T_L} = \frac{T_H}{T}$$




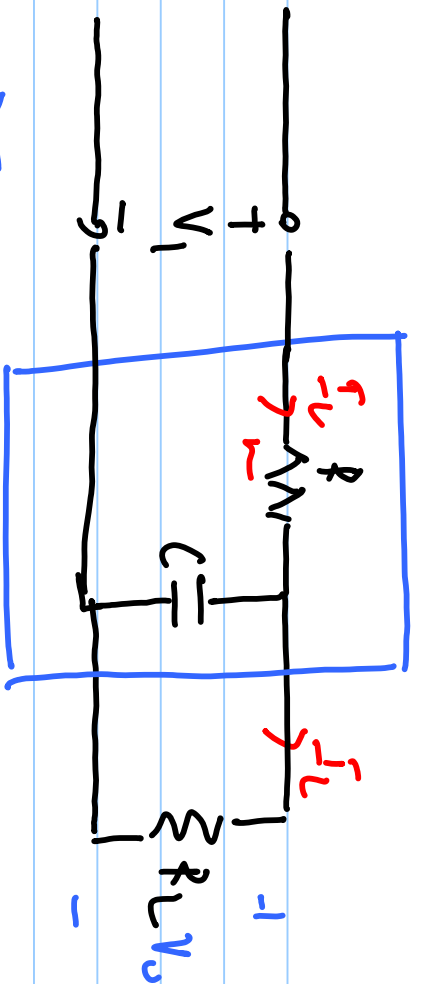
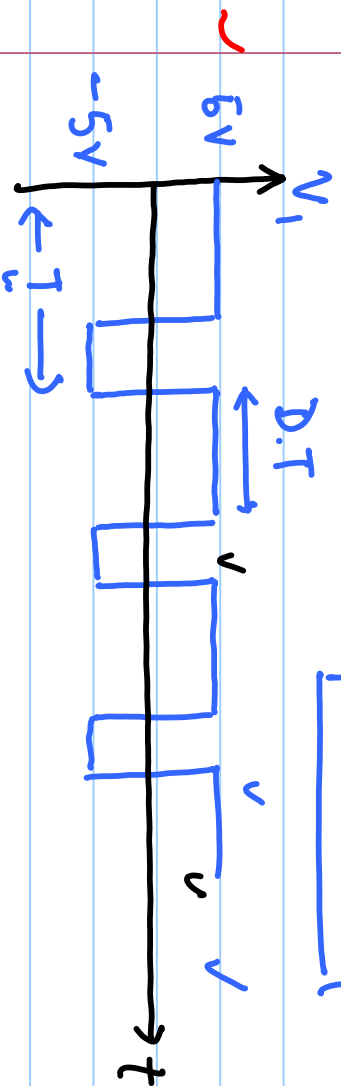
$$\frac{V_0}{V_1} = \frac{(R_L \parallel \frac{1}{sC})}{R + (R_L \parallel \frac{1}{sC})}$$


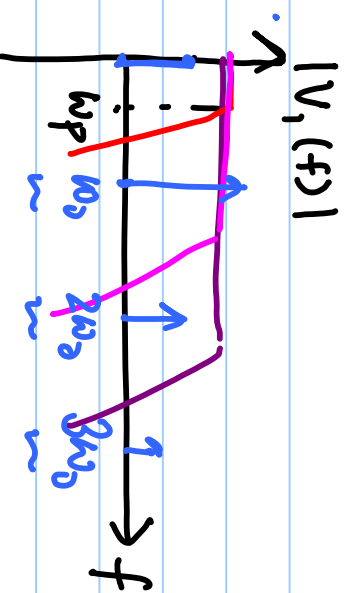
$$V_1(t) = \sum a_n \cos(n\omega_0 t) + b_n \sin(n\omega_0 t)$$




DC:  $a_0$

$$n\omega_0 = n\left(\frac{2\pi}{T}\right)$$

$$\frac{V_0}{V_1} = \frac{R_L / (1 + sR_L C)}{R + \frac{R_L}{1 + sR_L C}}$$

$$= \frac{R_L}{R + R_L + sR_L R C}$$

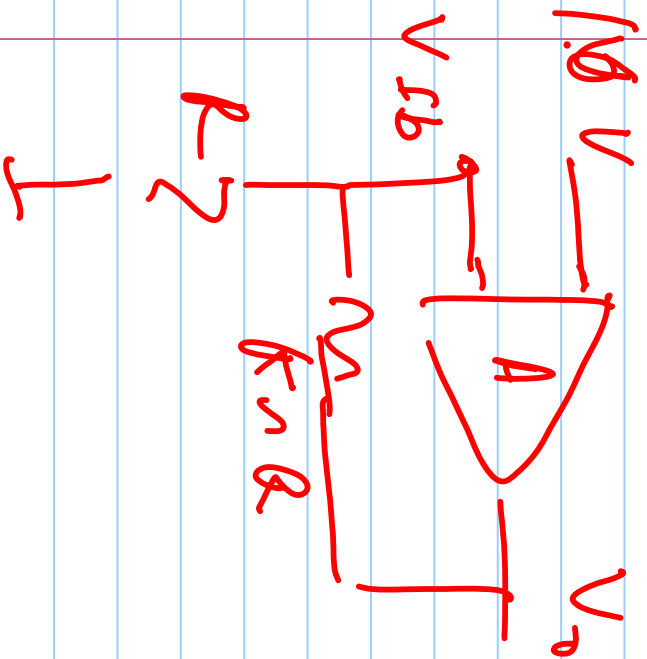

$$\frac{V_o}{V_i} = \frac{R_L / (R + R_L)}{1 + s R_L R / (R_L + R)}$$

DC gain:  $\frac{R_L}{R_L + R} \approx 1$

$$\omega_p = \frac{1}{\frac{R_L R}{R_L + R}} \ll \omega_0$$

$V_o = f(V_{in})$   
 $V_{in}$  sets up the operating point of non-linear blocks.

$$= a_0 + a_1 V_{in} + a_2 V_{in}^2 + a_3 V_{in}^3 + \dots$$

$$\cdot V_o' = f(V_{in} + \Delta V_{in})$$

$$\cancel{V_o} + \Delta V_o = a_0 + a_1 (V_{in} + \Delta V_{in}) + a_2 (V_{in} + \Delta V_{in})^2 + \dots$$
$$= (a_0 + a_1 V_{in} + a_2 V_{in}^2 + \dots) + a_1 \Delta V_{in} + a_2 \Delta V_{in}^2 + \dots$$

$$\Delta V_o = a_1 \Delta V_{in} + \underbrace{a_2 \Delta V_{in}^2 + \dots}_{\text{neg.}}$$

$$\Delta V_o = a_1 \Delta V_{in}$$

"In Simulation"

