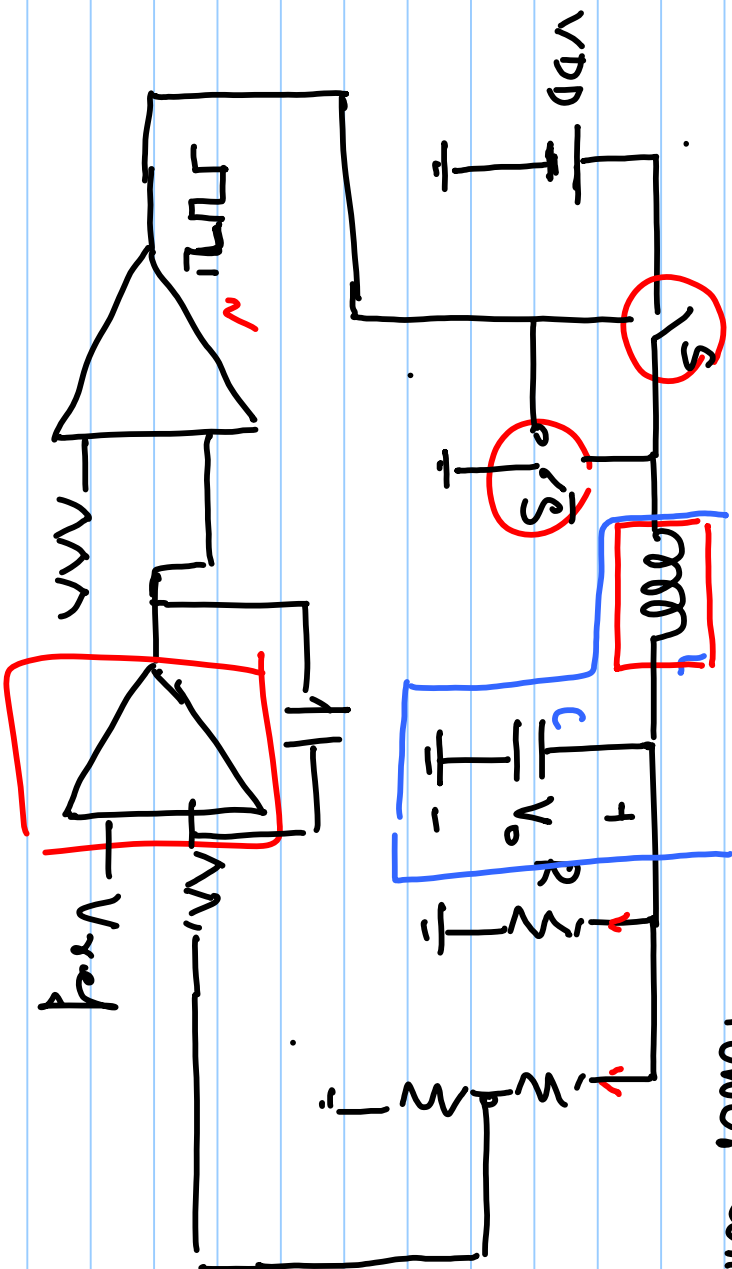



Lecture # 29

"Power Converter" (95%)




$$\eta = \frac{\text{Power delivered to load}}{\text{Total power drawn from supply}} \times 100$$

"Large area"

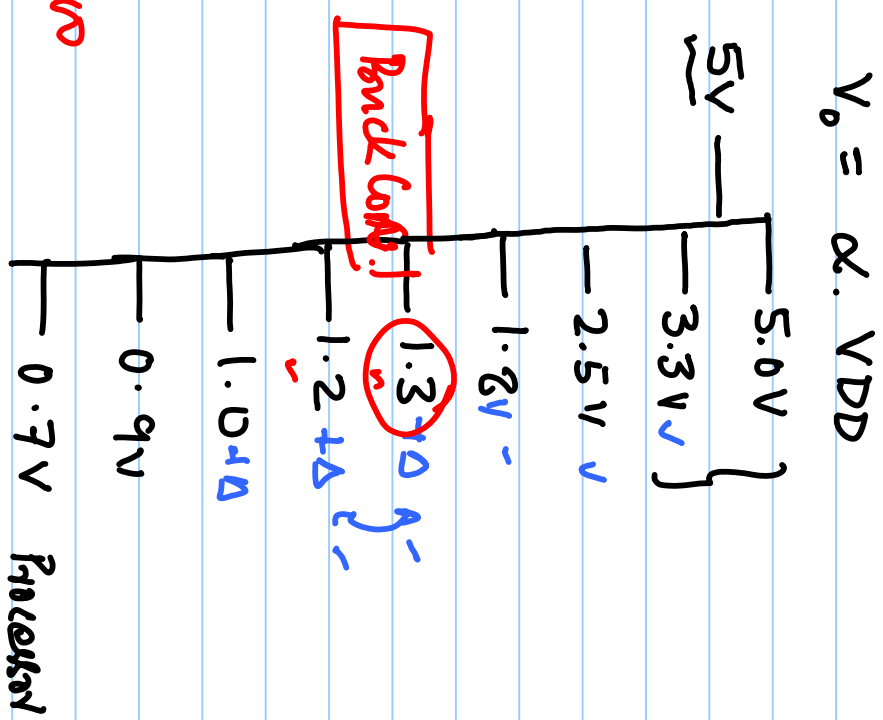

"Linear Regulator"

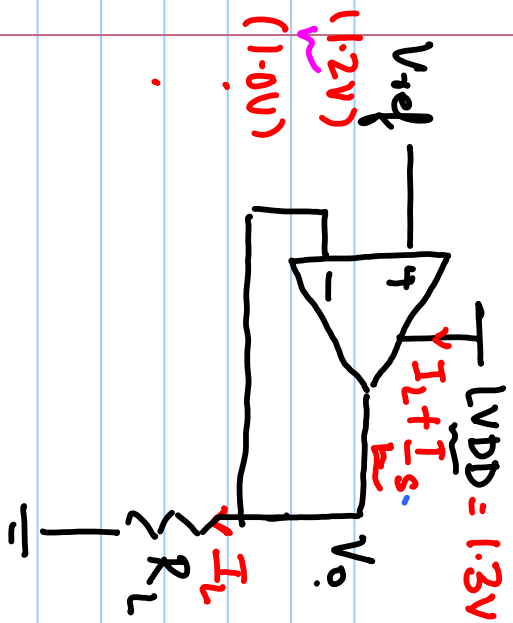

$V_{DD} = 1.3V$

$$V_o = V_{in}$$

$$I_s = 0.1 I_L$$

Best

$$\eta = \frac{1.2}{1.3} \times \frac{I_L}{I_L}$$

$$\eta = \frac{1.2}{1.3} \times \frac{I_L}{I_L + I_s} \times 100$$

$$V_o = V_{req}$$

$$\text{Power delivered to load} = V_o \times I_L$$



$$= V_{req} \times I_L$$


$$\text{Power drawn from supply} = (I_L + I_s) V_{DD}$$

$$V_o = V_{req} \text{ with require } I_s + I_L \gg I_L$$



$$I_s \gg 0$$
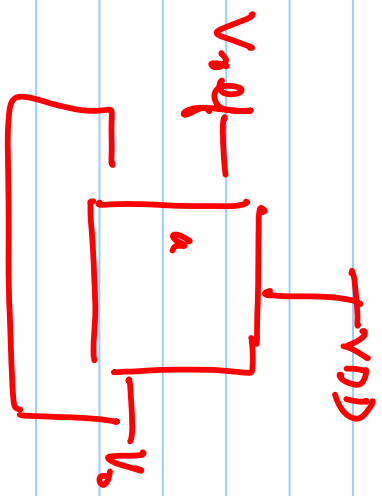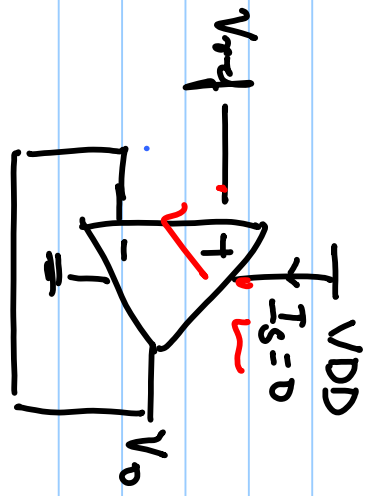
$$\eta = \frac{V_o \times I_L}{(I_s + I_L) V_{DD}} \times 100\%$$






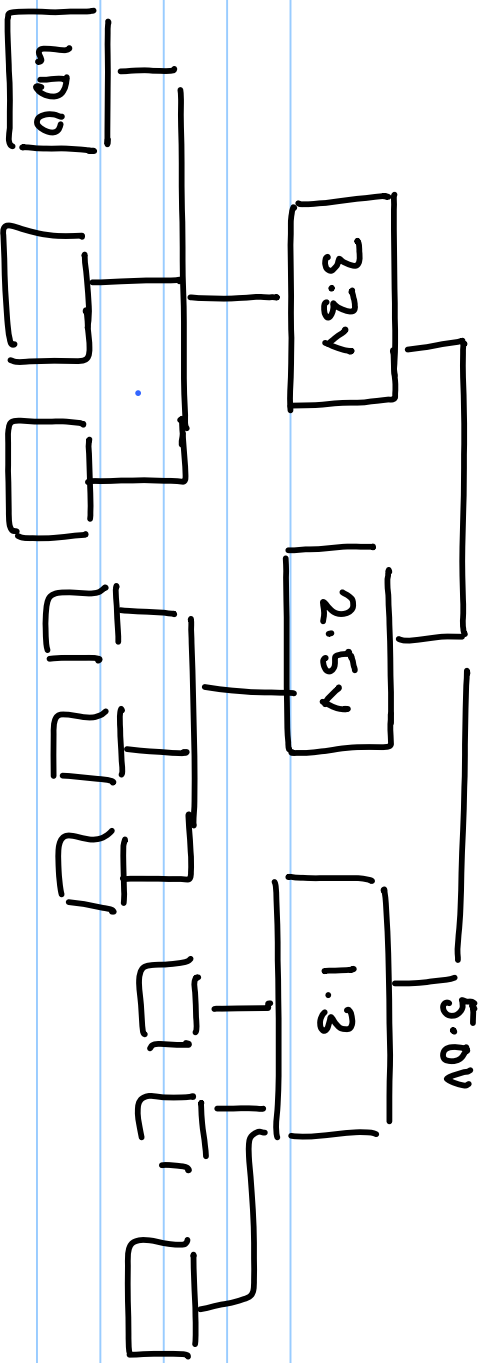

Linear dropout regulator

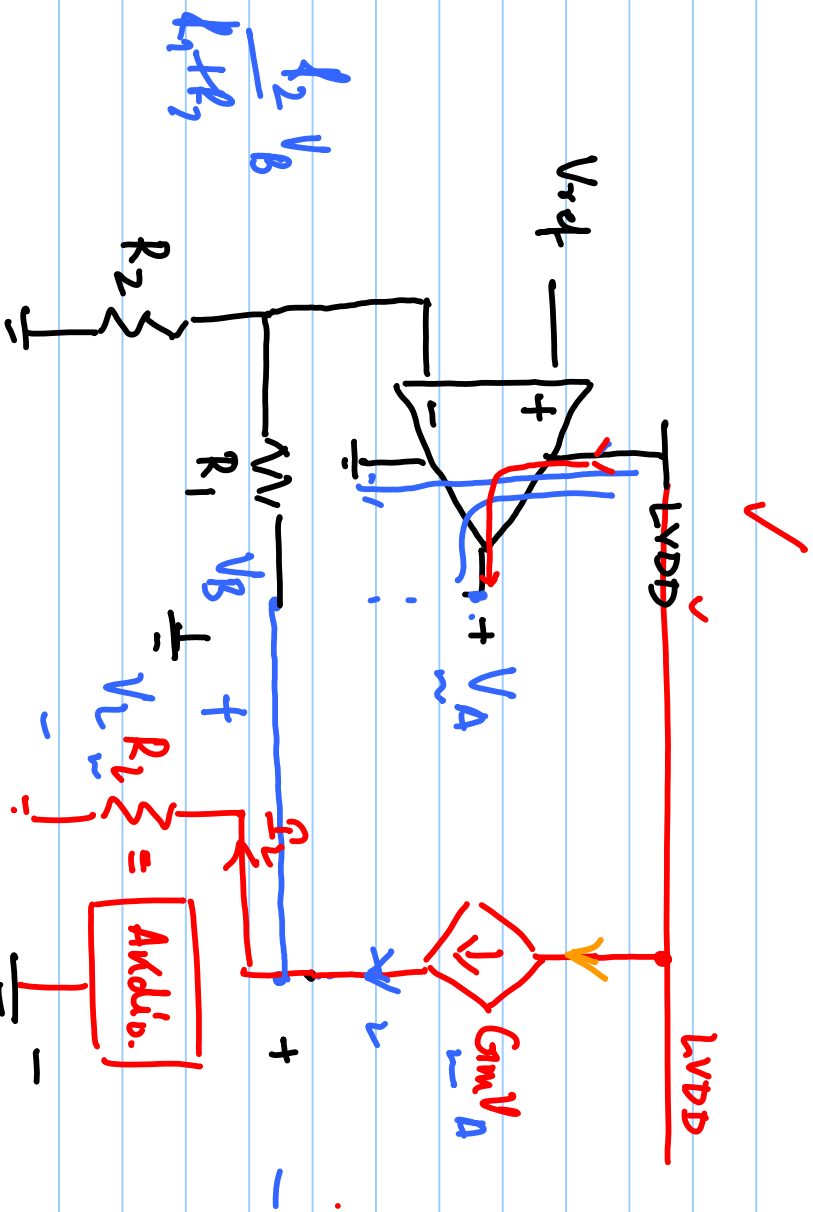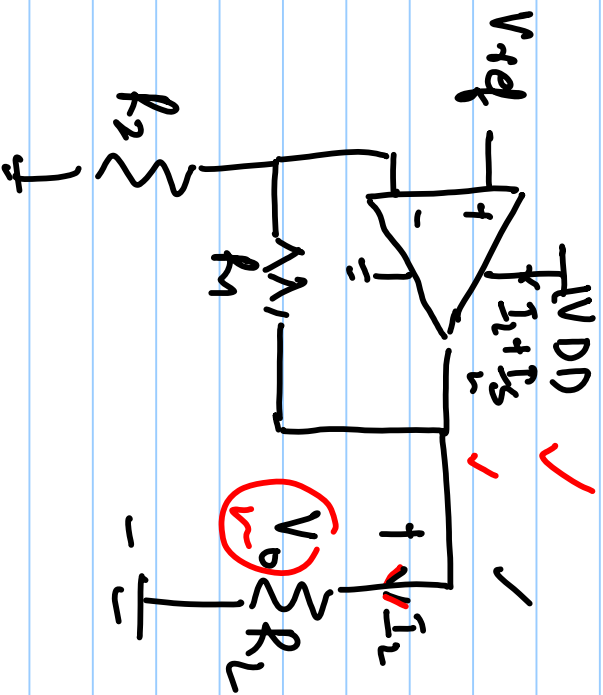

$$G_m V_o = I_L = \frac{V_o}{R_L}$$

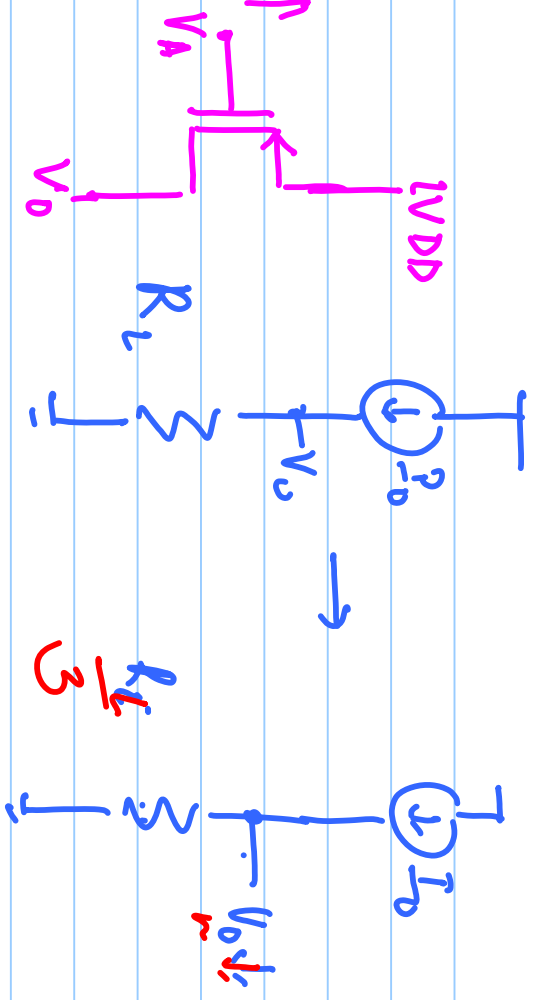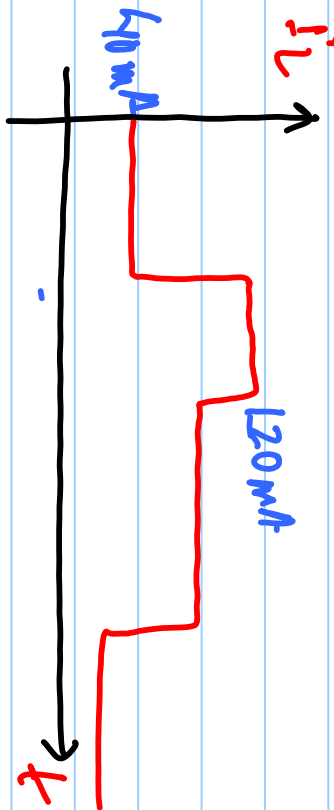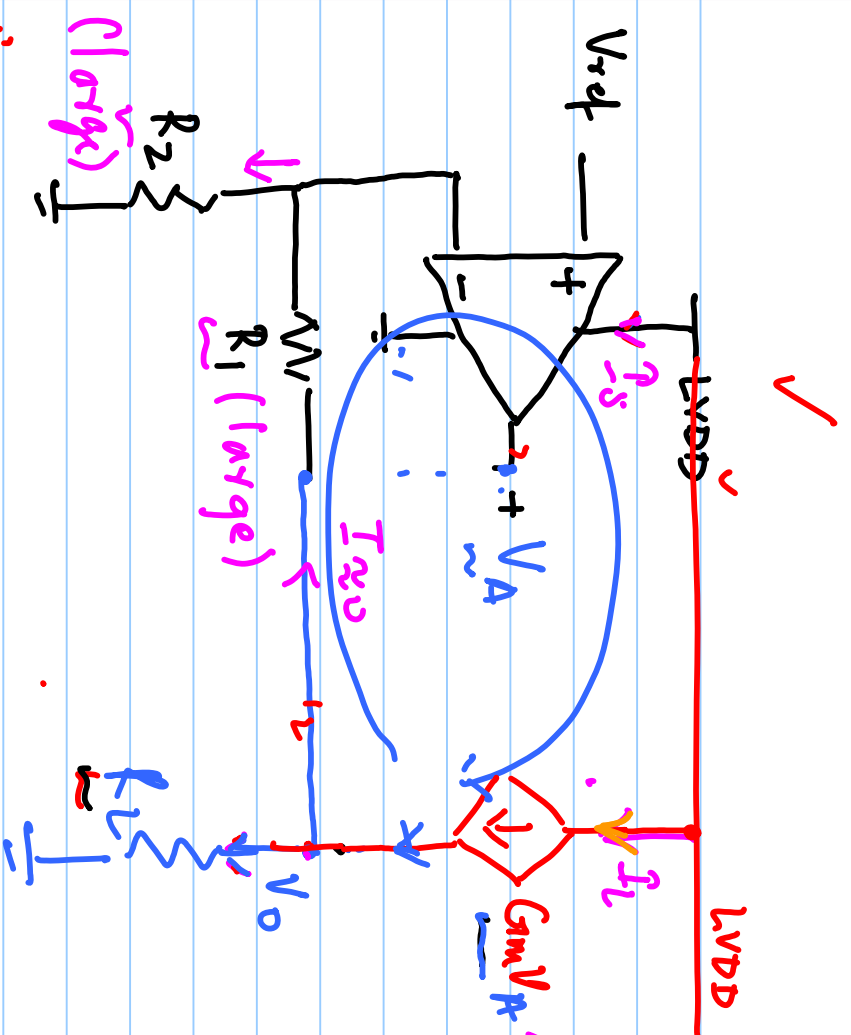

$$\mu = \frac{V_o \times I_T}{L_{VDD} \times I_L + L_{VDD} \times I_S} \times 100$$

I_S is not proportional to I_L

