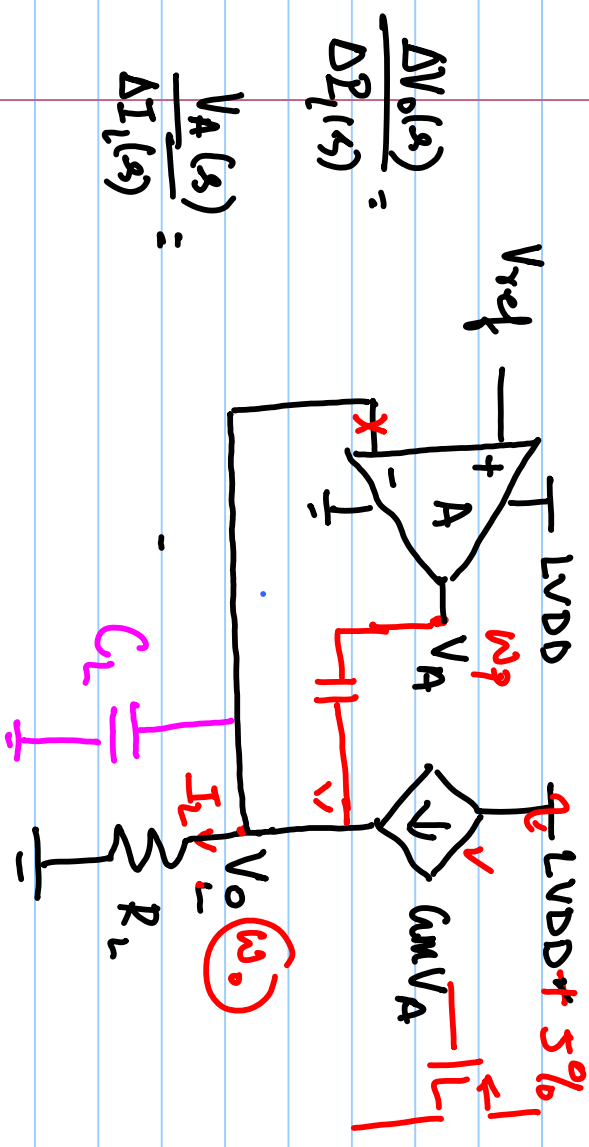


Low Dropout Regulator



$$\frac{\Delta V_o(s)}{\Delta I_L(s)} =$$

$$\frac{V_A(s)}{\Delta I_L(s)} =$$

$$LG(s) = \frac{G_m R_A}{1 + s R_L C_L} \cdot A =$$

$$\frac{G_m R_A}{1 + s R_L C_L} \cdot \frac{A_0}{1 + s/\omega_p}$$




$$\omega_o = \frac{1}{R_L C_L}, \omega_p$$

if $\omega_o \gg \omega_p$, $\phi_m = 30^\circ$

$\phi_m = 70^\circ$

$\omega_o \ll \omega_p$, $\phi_m = 30^\circ$

$\phi_m = 70^\circ$

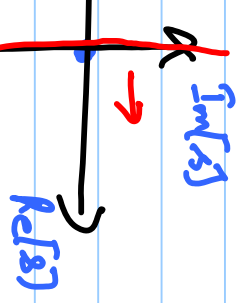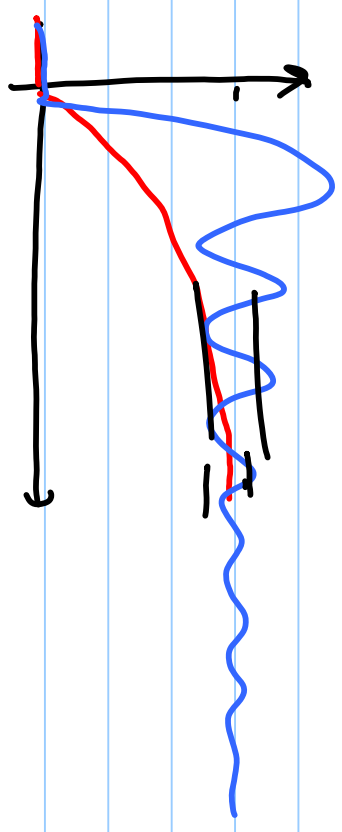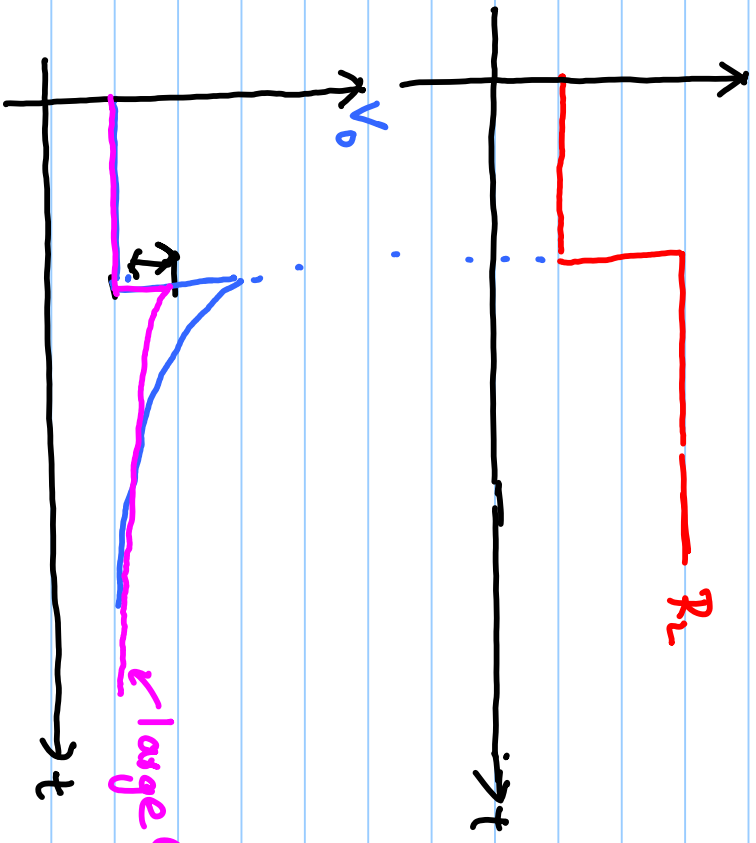

line regulation = $\frac{\Delta V_o}{\Delta V_{DD}}$ change in o/p voltage w.r.t change in V_{DD} .

✓ load Regulation = $\frac{\Delta V_o}{\Delta I_L}$ change in o/p voltage due to change in load current.

✓ load Transient = change in o/p due to change in load current.

