

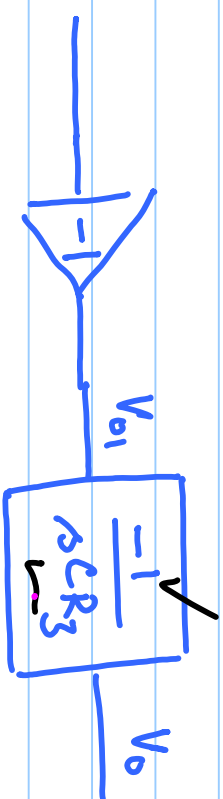
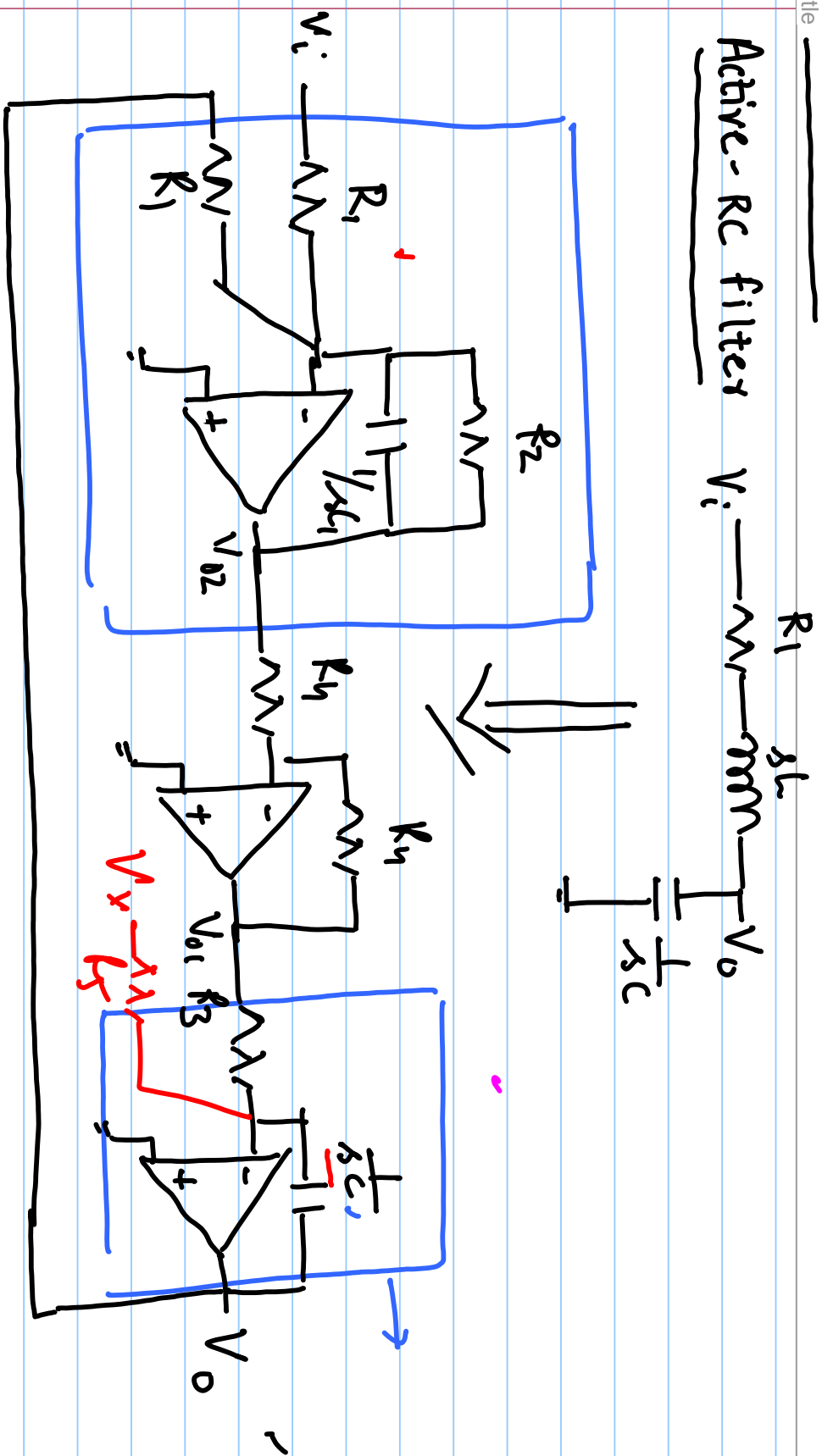




Lecture # 37




Active-RC filter

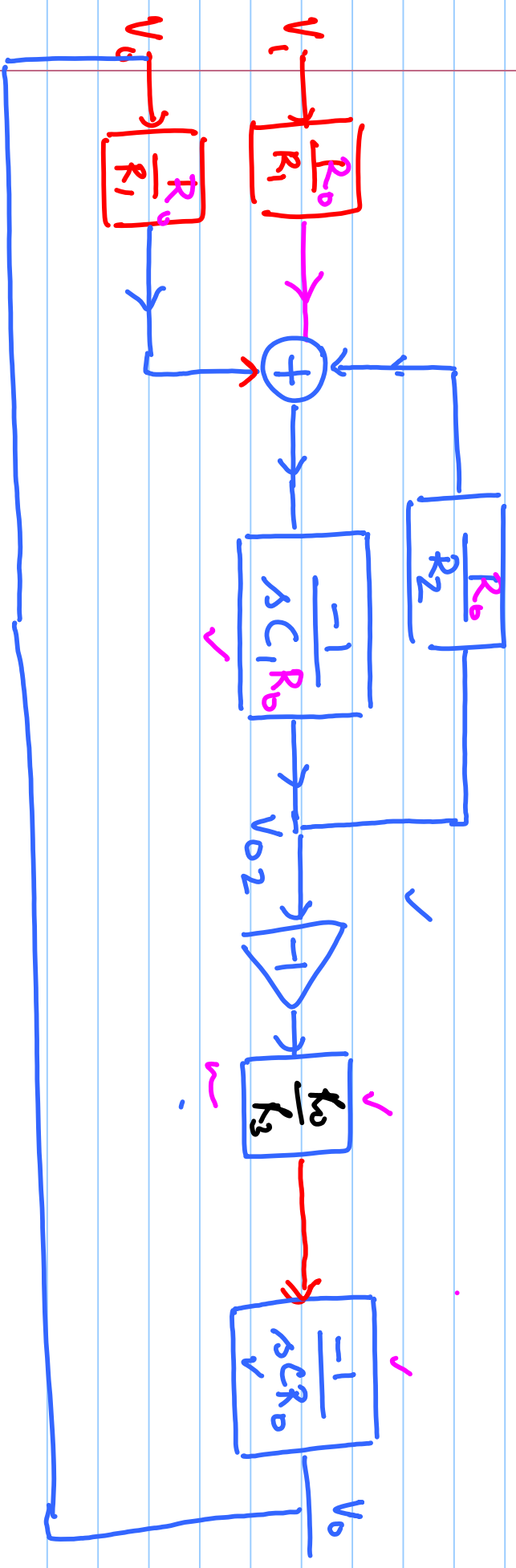
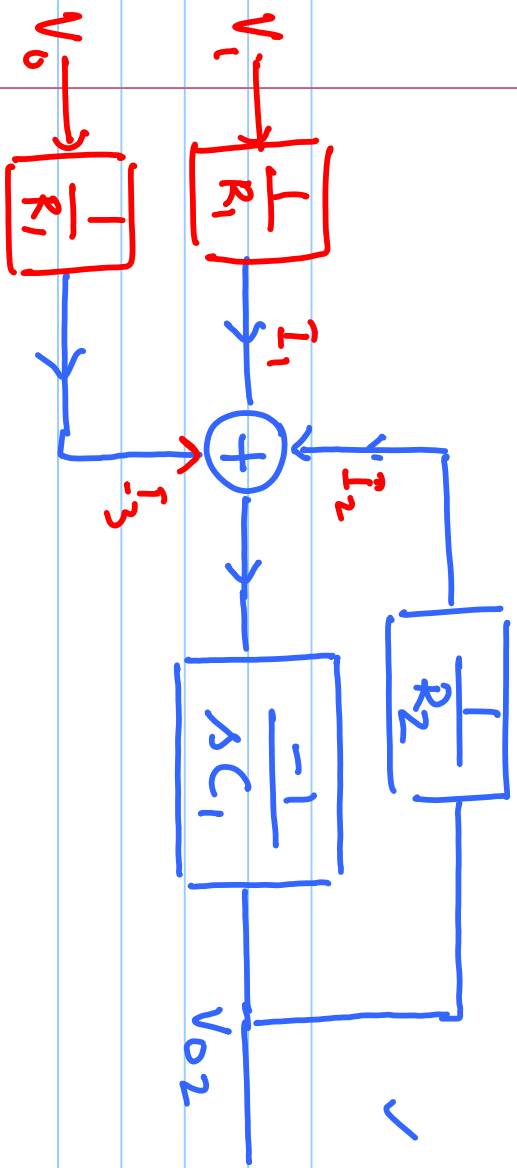
$$\frac{V_0}{V_{01}} = \frac{-1}{sCR_3} = \frac{-1}{sCR_3} \cdot \frac{R_3}{R_3}$$



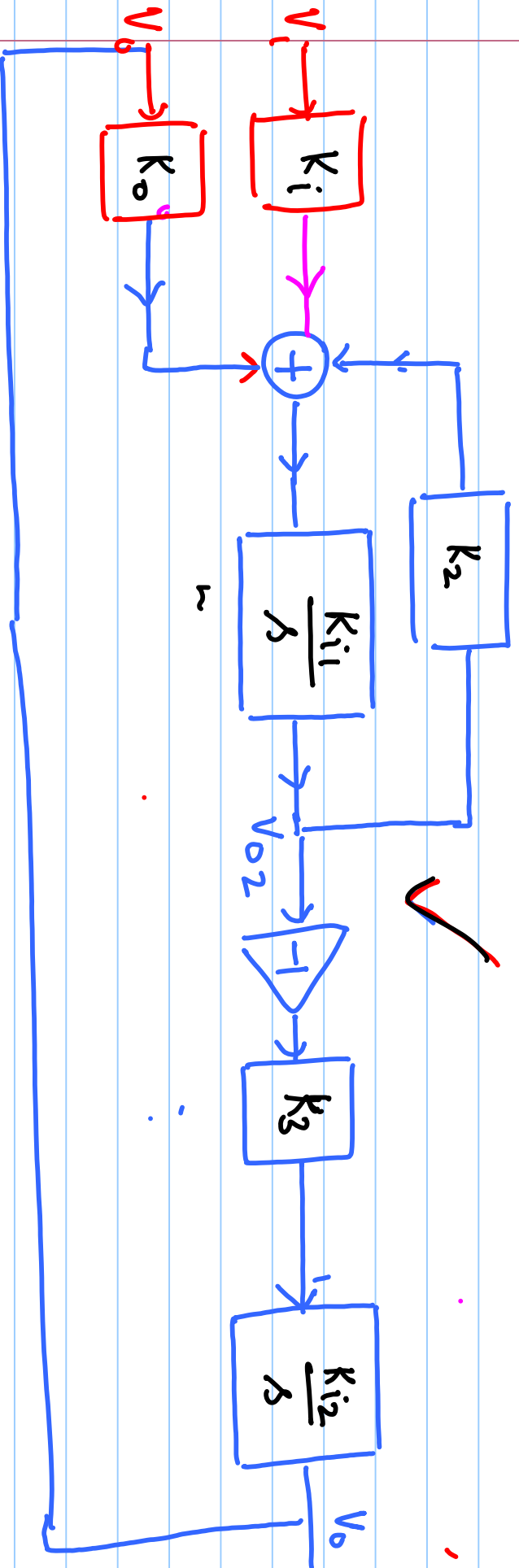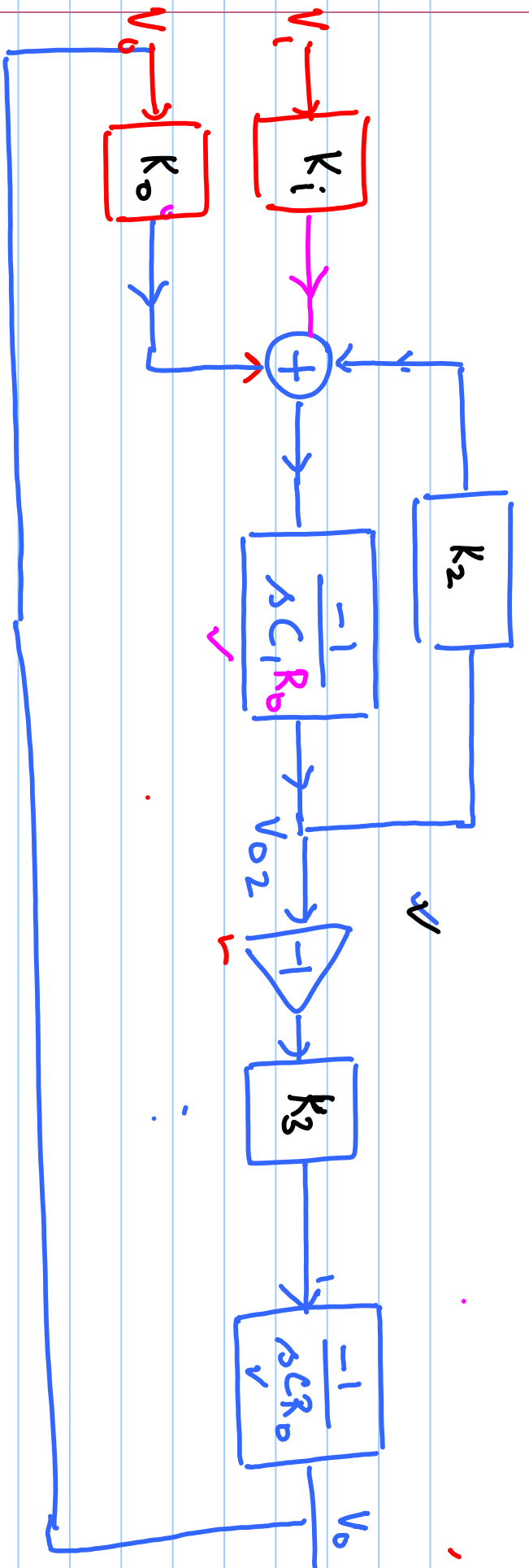

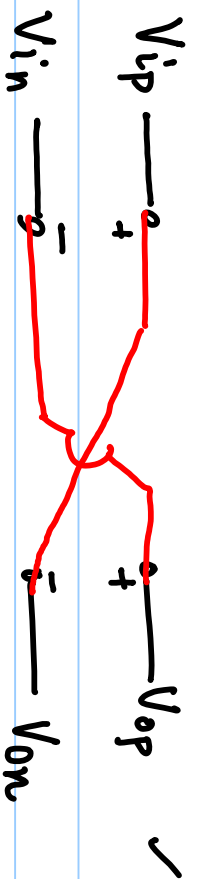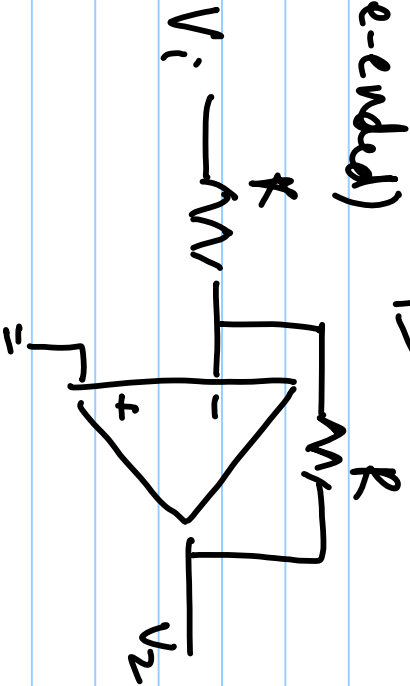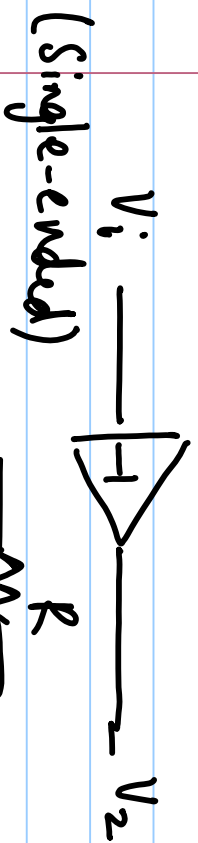


$$V_i = V_{ip} - V_{in} = U_{diff} \quad (\text{Differential})$$

$$V_{ip} - V_{in} = \frac{U_{diff}}{2}$$

$$V_{out} = V_{op} - V_{on} \quad \checkmark$$

$$= -(V_{ip} - V_{in})$$

$$= -U_{diff}$$

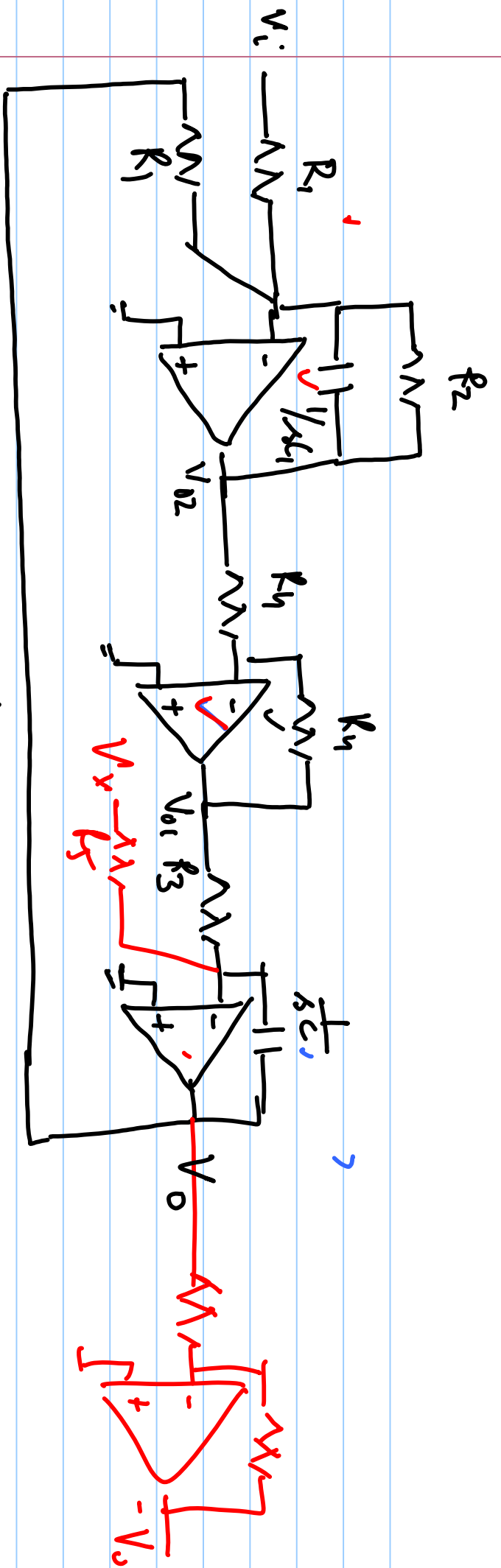

$$\left\{ \left( \frac{V_i + V_o}{R_1} \right) \frac{-R_2}{1 + sCR_2} \times \left( \frac{-1}{s} \right) \times \left( \frac{-1}{sCR_3} \right) \right\} = V_o$$

$$(V_i + V_o) = -V_o sCR_3 (1 + sCR_2) \frac{R_1}{R_2}$$

$$V_i = -V_o \left( 1 + sCR_3 \frac{R_1}{R_2} (1 + sCR_2) \right)$$

$$\frac{V_o}{V_i} = - \frac{1}{1 + sCR_3 \frac{R_1}{R_2} (1 + sCR_2)}$$



$$H(s) = \frac{1}{1 + \frac{s}{\omega_0 Q} + \frac{s^2}{\omega_0^2}} = \frac{V_o}{V_i} \quad \left( \begin{array}{l} H(s) = \frac{1 + s^2/\omega_0^2}{1 + \frac{s}{\omega_0 Q} + \frac{s^2}{\omega_0^2}} \end{array} \right.$$



$$V_o \left( 1 + \frac{s}{\omega_0 Q} + \frac{s^2}{\omega_0^2} \right) = V_i$$

$$V_o \left( \frac{-\omega_0^2}{s^2} + \frac{\omega_0}{s} \frac{1}{Q} + 1 \right) = V_i \frac{\omega_0^2}{s^2}$$

$$V_o = V_i \cdot \frac{\omega_0^2}{s^2} - V_o \left( \frac{\omega_0^2}{s^2} + \frac{\omega_0}{s} \frac{1}{Q} \right)$$
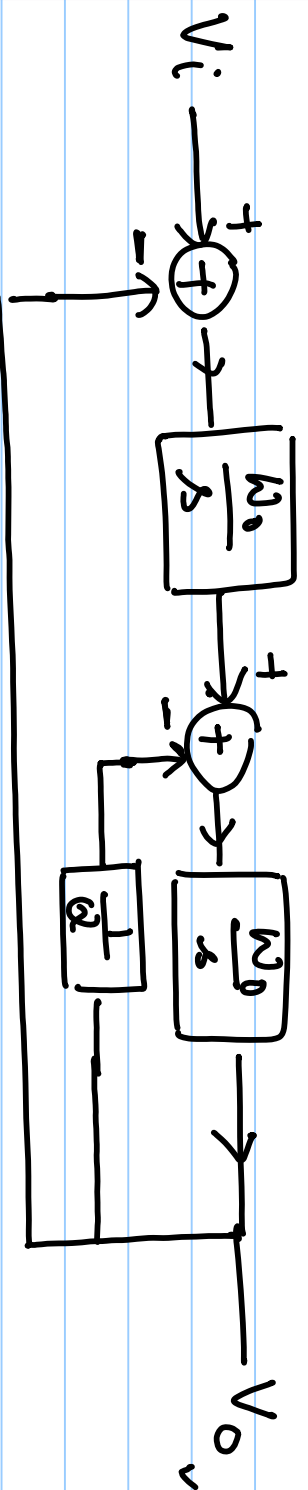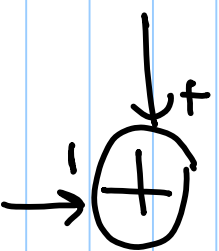
$$V_o = \left[ (V_i - V_o) \frac{\omega_0}{s} - \frac{1}{Q} V_o \right] \frac{\omega_0}{s}$$



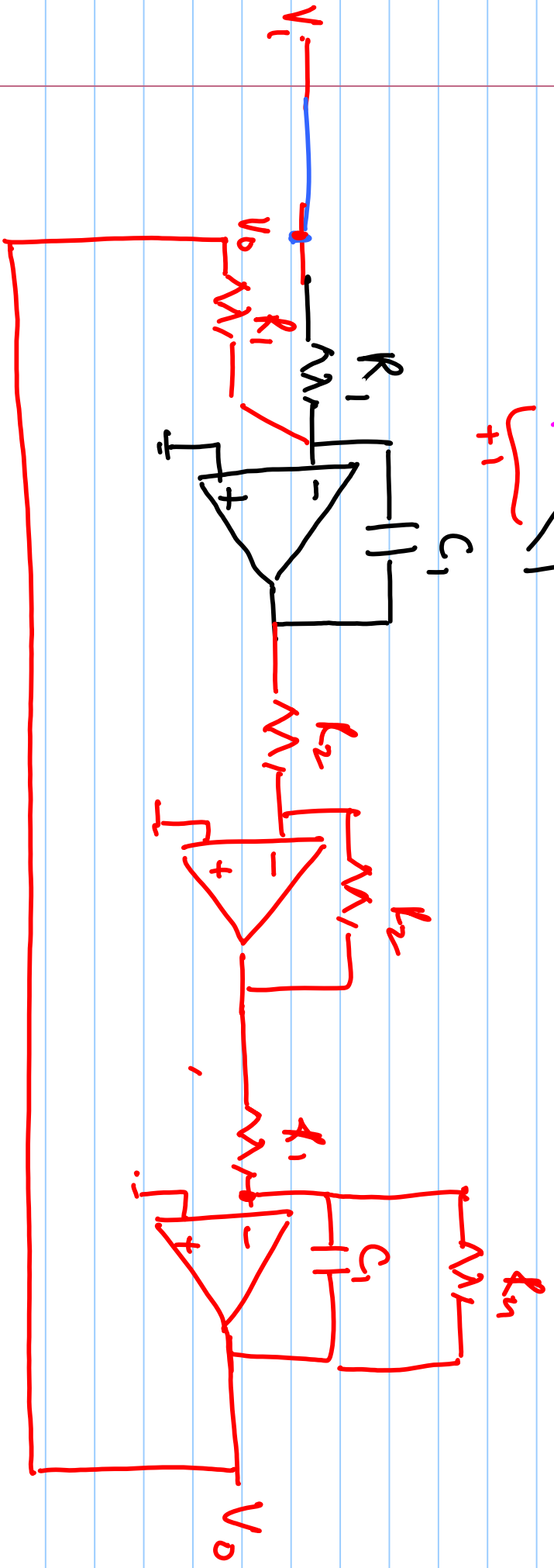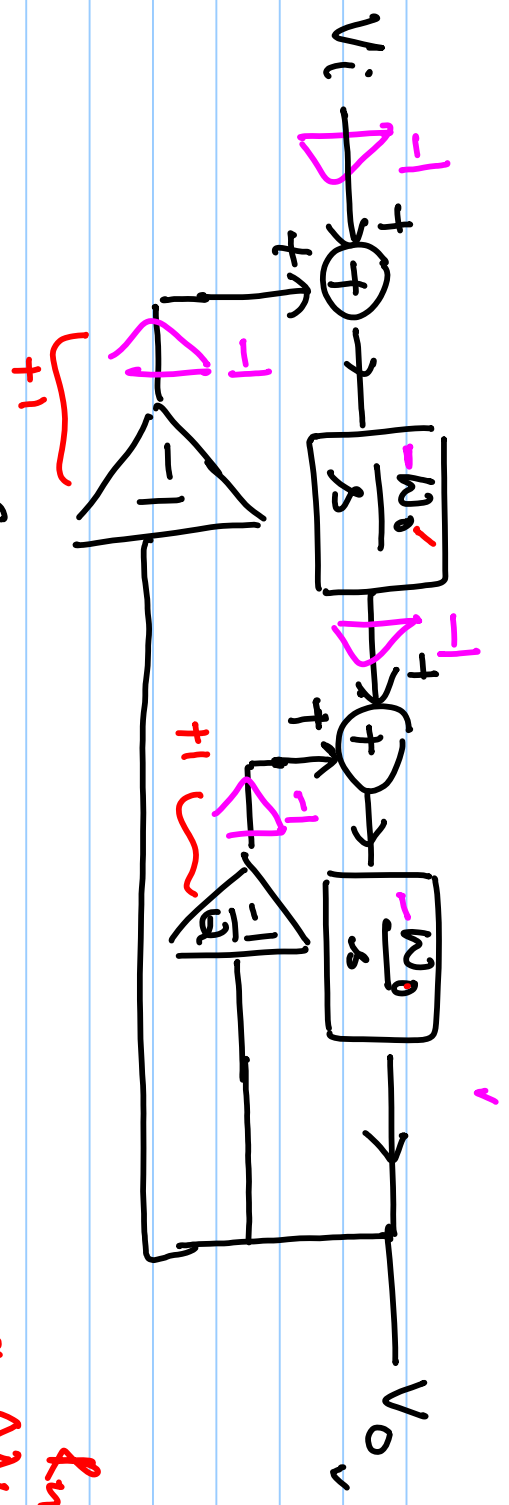

$$\frac{V_o}{V_i} = \frac{-1}{1 + \frac{s}{\omega_{Dp}} + \frac{s^2}{\omega_n^2}}$$