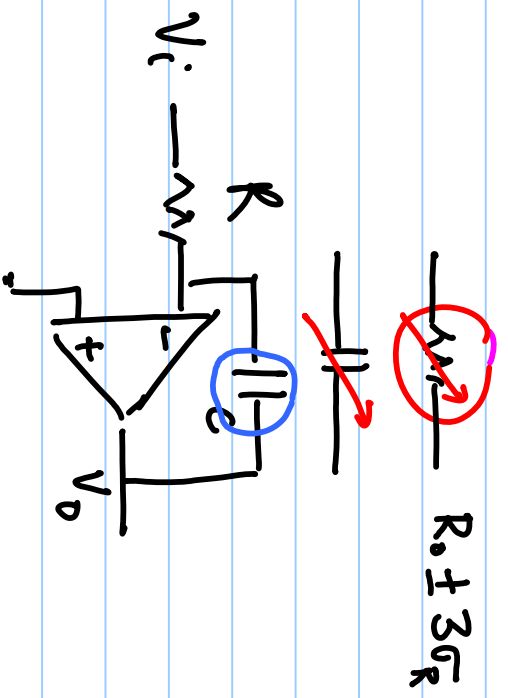



# Lecture # 38

Passive RLC  $\xrightarrow{-L}$  Active - RC




$$\frac{V_o}{V_i} = \frac{-1}{sRC_0}$$
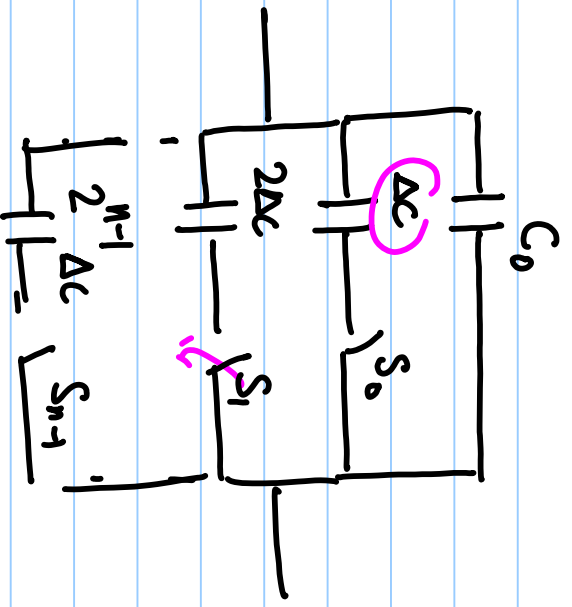
$$= \frac{-1}{s(R_0 \pm sR)(C_0 \pm \Delta C)}$$


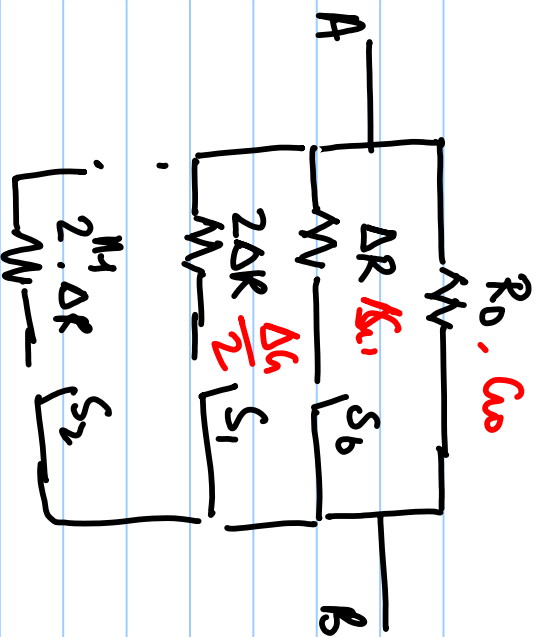
$$C_{total} = C_0 + (S_0 \cdot 2 \cdot \Delta C + S_1 \cdot 2^1 \cdot \Delta C + S_2 \cdot \dots + S_{n-1} \cdot 2^{n-1} \cdot \Delta C)$$





$$R_{total} = \frac{1}{\frac{1}{R_0} + \frac{S_0}{2 \cdot \Delta R} + \frac{S_1}{2 \cdot \Delta R} + \dots + \frac{S_M}{2 \cdot \Delta R}}$$

minimum change in  $R_{total}$


$$R_1 = \frac{1}{\frac{1}{R_0} + \frac{1}{2^{n_1} \cdot \Delta R}} = \frac{R_0 \cdot (2^{n_1} \cdot \Delta R)}{R_0 + 2^{n_1} \cdot \Delta R}$$

$$R_0 - R_1 = R_0 - \frac{R_0 \cdot 2^{n_1} \cdot \Delta R}{R_0 + 2^{n_1} \cdot \Delta R} = \frac{R_0^2}{R_0 + 2^{n_1} \cdot \Delta R}$$
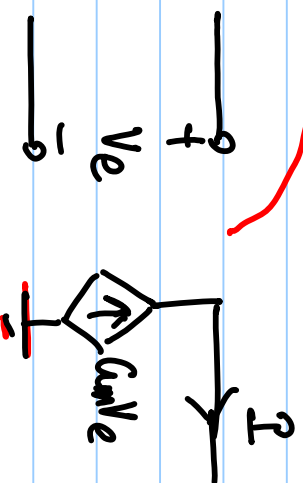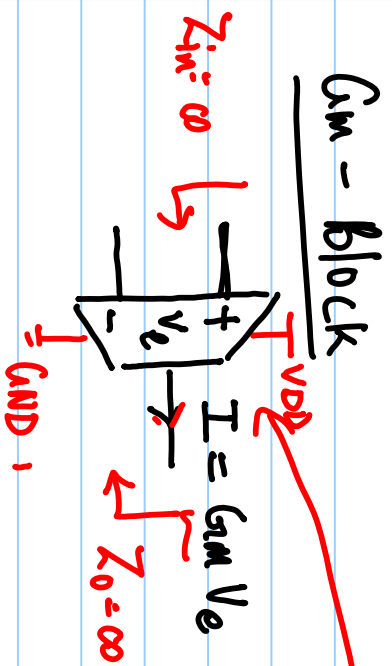
$$R_0 \parallel R(\rightarrow \infty) = R_0 \xrightarrow{\Delta} 0$$




(vecs)

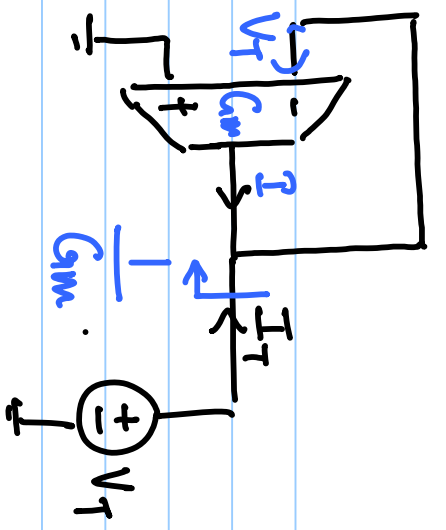

$$I = G_{m1} (-V_T) = -I_T$$


$$\frac{V_T}{I_T} = \frac{1}{G_{m1}} = R$$


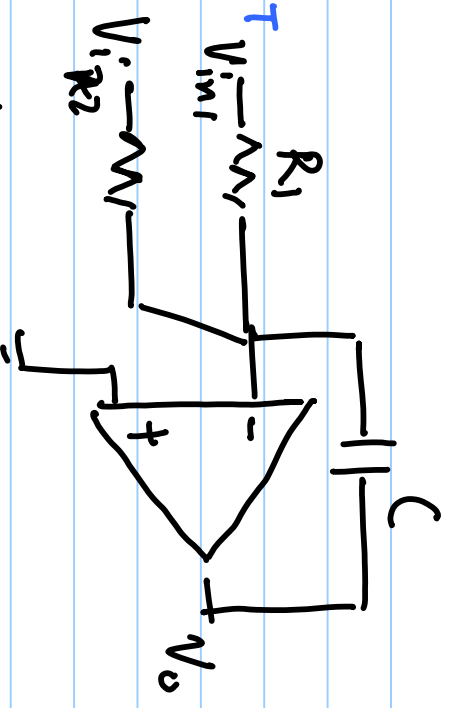
- Voltage gain
  - Integrator
  - RC filter
- Active-RC



$$V_o = \left( -\frac{V_{in1}}{R_1} - \frac{V_{in2}}{R_2} \right) \times \frac{1}{sC}$$

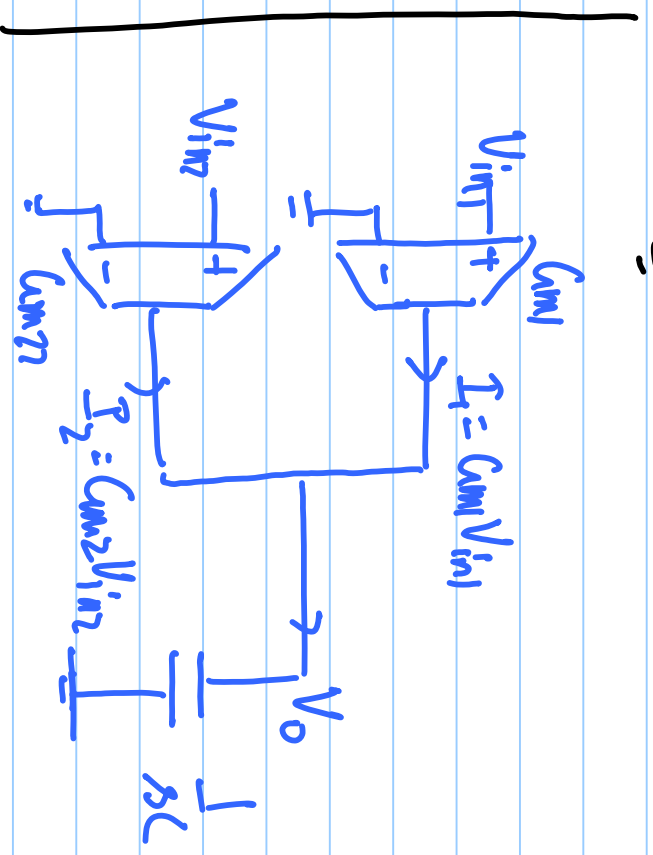
$$= -(G_{m1} V_{in1} + G_{m2} V_{in2}) \times \frac{1}{sC}$$



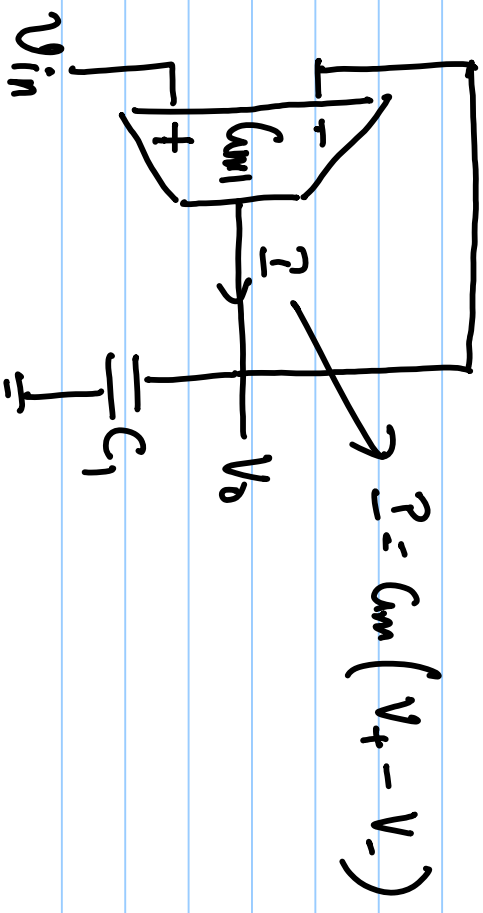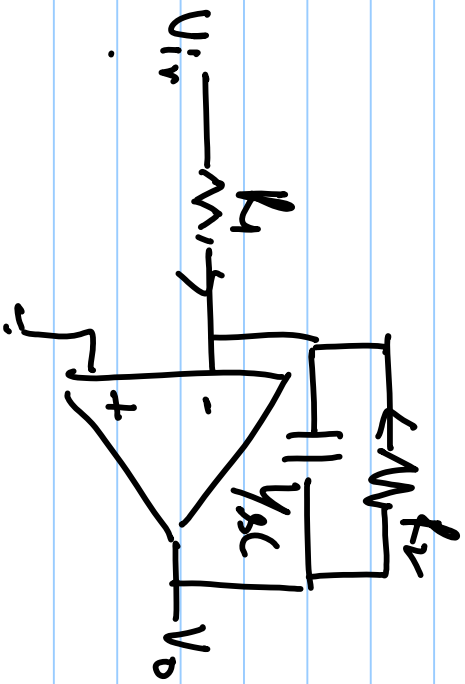

$$\left( \frac{V_{in}}{R_1} + \frac{V_o}{R_2} \right) \times \frac{1}{sC_1} = -V_o$$
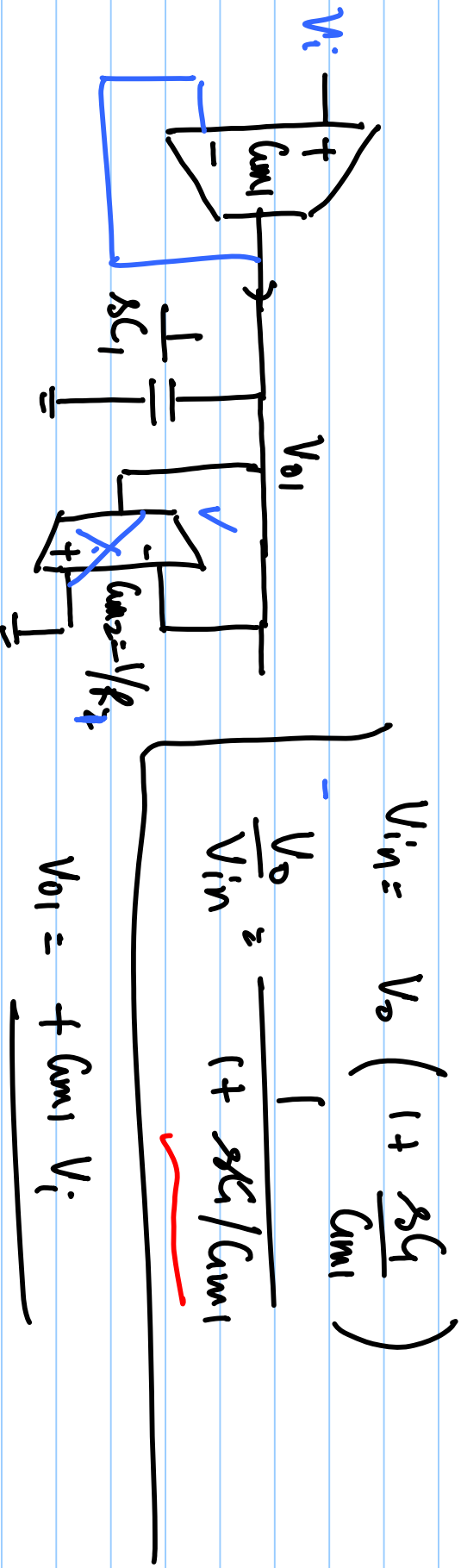
$$G_{m1} (V_{in} - V_o) \times \frac{1}{sC_1} = V_o$$




$$V_{in} = V_o \left( 1 + \frac{sC_1}{G_{m1}} \right)$$

$$\frac{V_o}{V_{in}} = \frac{1}{1 + \frac{sC_1}{G_{m1}}}$$


$$V_{o1} = \frac{+G_{m1} V_i}{sC_1 + G_{m1}}$$

$$sC_1 + G_{m1}$$

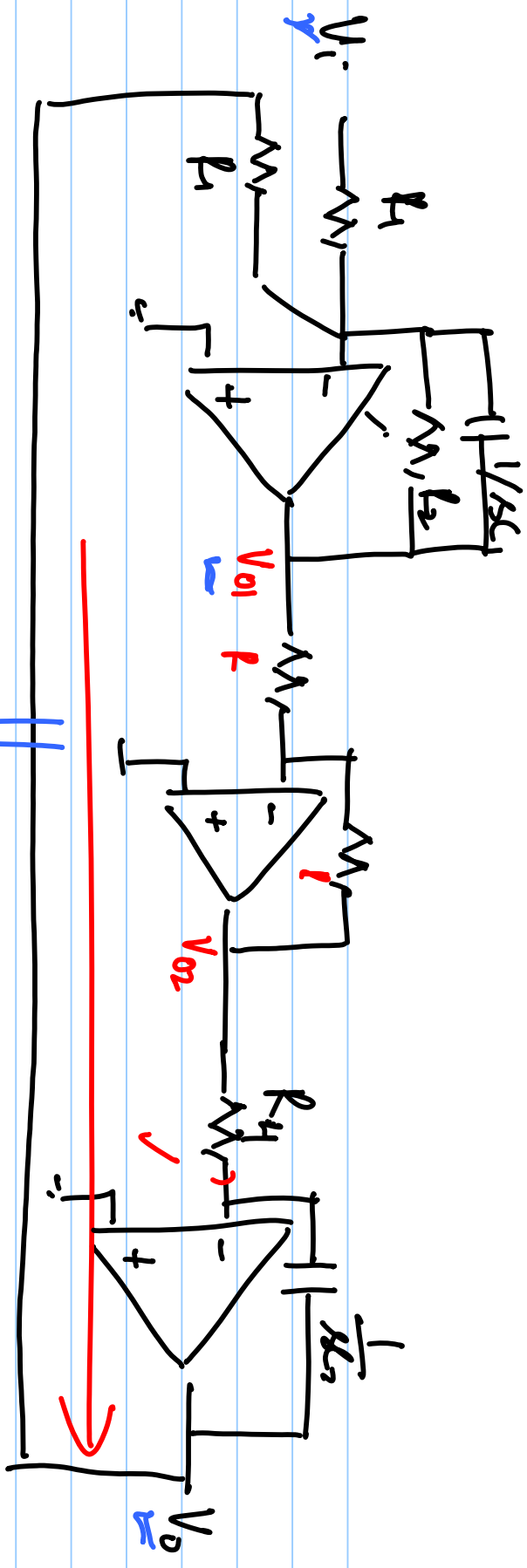

$$\frac{V_o}{V_{o1}} =$$

two

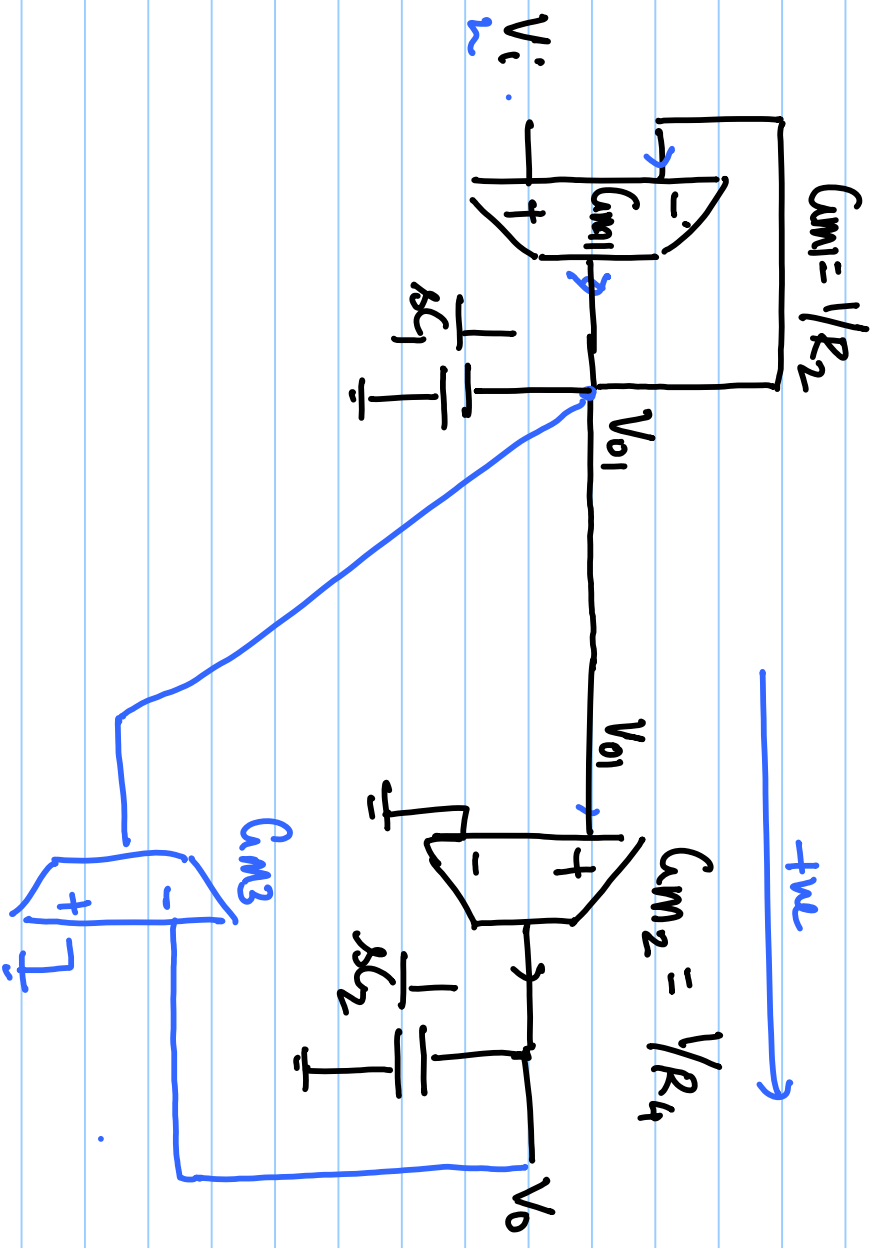


$$G_{m1} = 1/R_2$$

$$G_{m2} = 1/R_4$$


$$G_{m3}$$

# "Cm-C Filters"

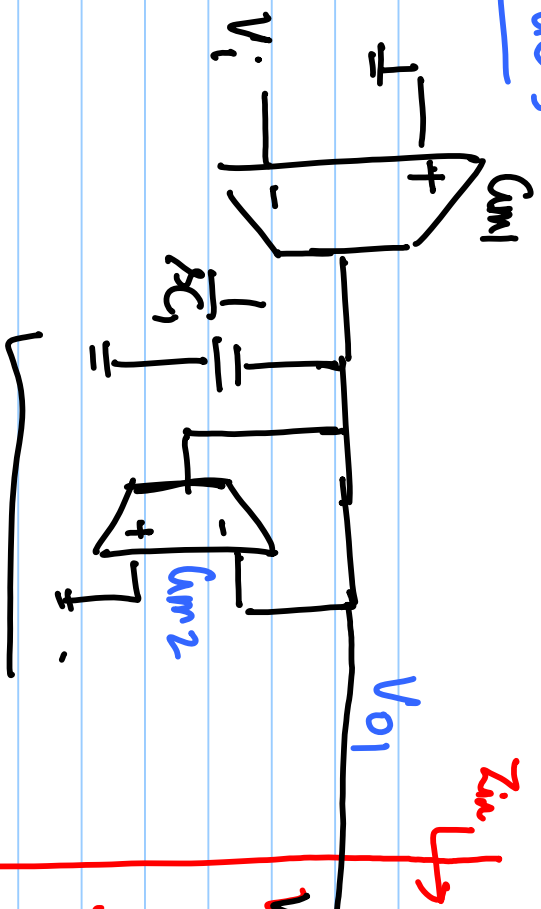

$$I_T = \frac{C_{m1} C_{m2} V_1}{R C_2}$$
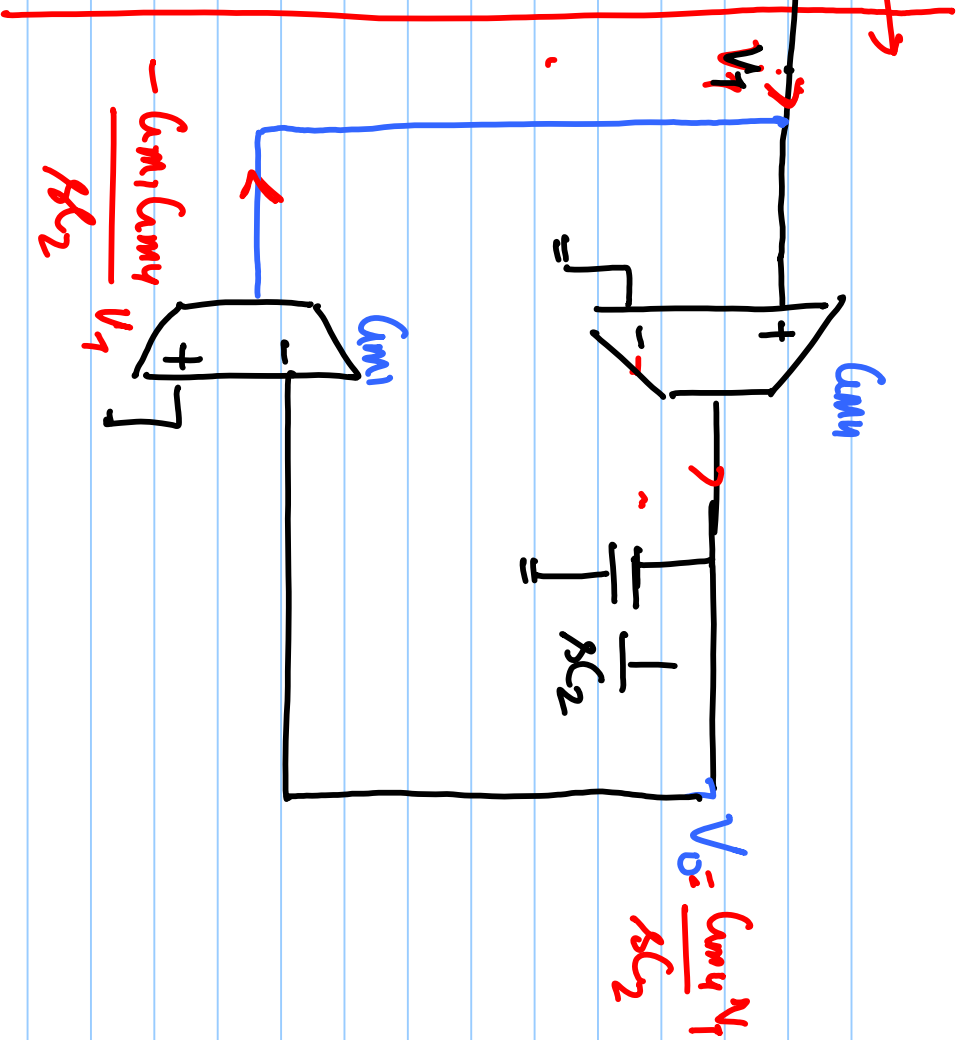
$$\frac{V_1}{I_T} = \frac{R C_2}{C_{m1} C_{m2}}$$



$$- \frac{C_{m1} C_{m2} V_1}{R C_2}$$

$$V_0 = \frac{C_{m1} V_1}{R C_2}$$