

# Lecture #14

Second - Order System .

$$H(s) = \frac{A_{DC} \cdot \omega_n^2}{s^2 + 2\zeta \omega_n s + \omega_n^2}$$



$$A_{DC} = \frac{K_c}{1 + K/A_0}$$




When  $\zeta \gg 1$  , Real poles along  $-w$  Re axis.


if  $\zeta < 1$  , Complex poles.

if  $\zeta \ll 1$


if  $\zeta$

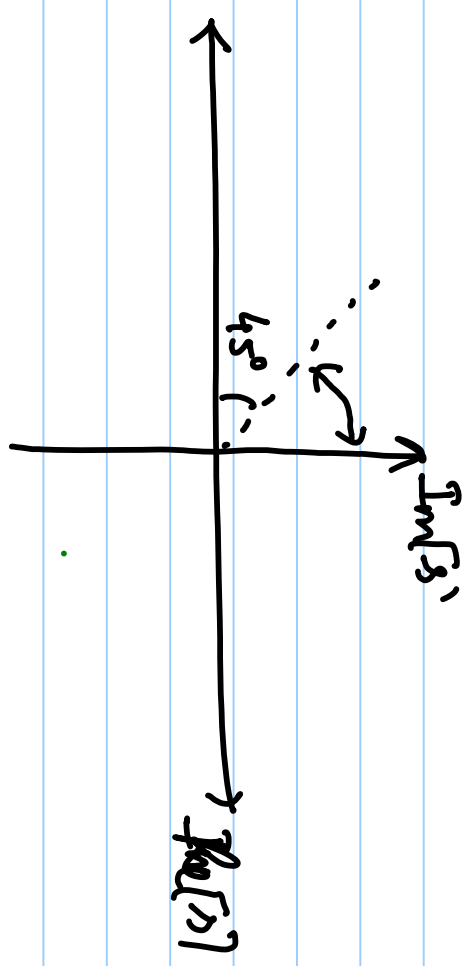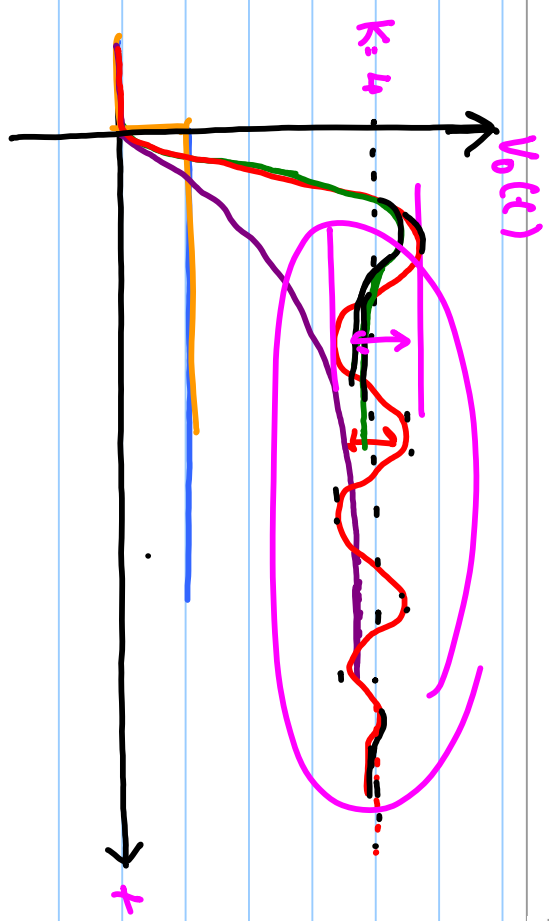

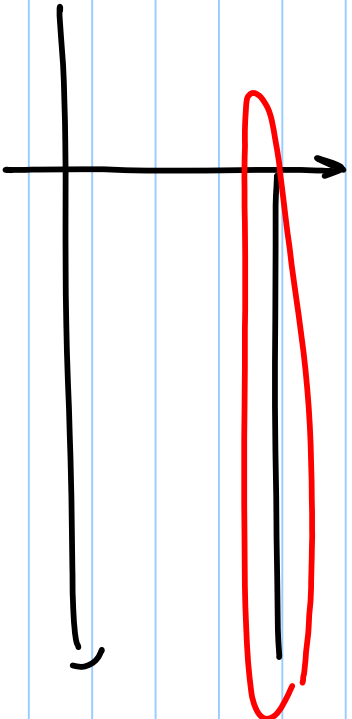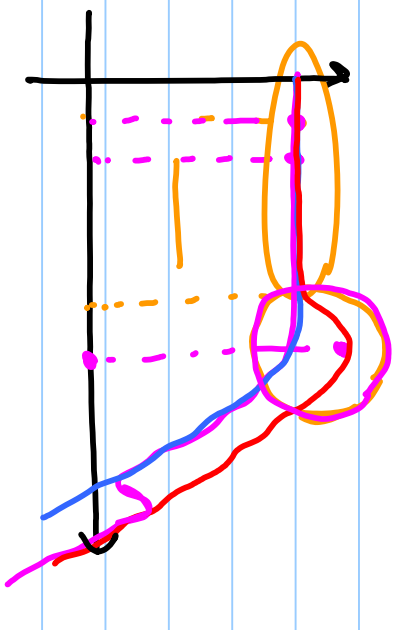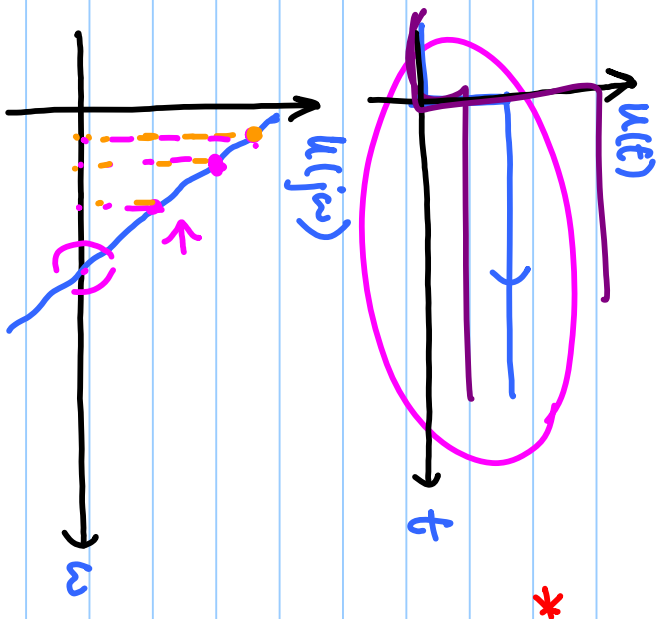

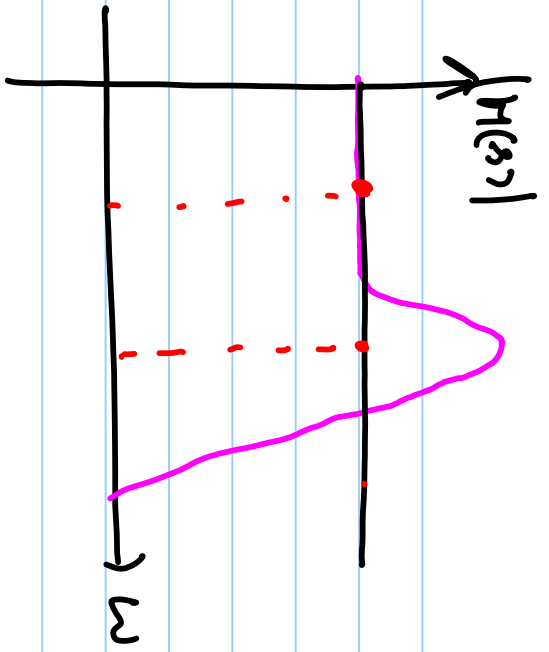

Phase - linear

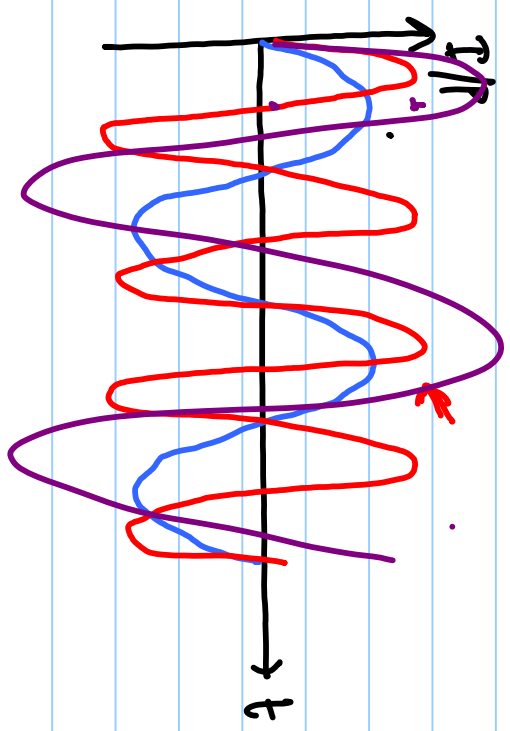

$$\frac{V_o}{V_{in}} = \frac{A_{DC} \cdot \omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

$$\omega_n = \sqrt{p_1 p_2 \left(1 + \frac{A_{DC}}{K}\right)}$$

$$\zeta = \frac{1}{2} \sqrt{\frac{1}{1 + \frac{A_{DC}}{K}}} \left( \sqrt{\frac{p_1}{p_2}} + \sqrt{\frac{p_2}{p_1}} \right)$$

$$\zeta = 1$$

$$\frac{V_o}{V_{in}} = \frac{A_{DC} \cdot \omega_n^2}{s^2 + 2\omega_n s + \omega_n^2}$$

$$= \frac{A_{DC} \cdot \omega_n^2}{(s + \omega_n)^2}$$

$$V_o(s) = V_{in}(s) \times \frac{A_{DC} \cdot \omega_n^2}{(s + \omega_n)^2}$$

if  $V_{in}(t) = u(t)$

$$V_o(t) = \mathcal{L}^{-1} \left\{ \frac{1}{s} \cdot \frac{A_{DC} \cdot \omega_n^2}{(s + \omega_n)^2} \right\}$$

$$= \mathcal{L}^{-1} \left\{ A_{DC} \left[ \frac{1}{s} + \frac{-1}{(s + \omega_n)} + \frac{-\omega_n}{(s + \omega_n)^2} \right] \right\}$$

$$= A_{DC} \left[ 1 - e^{-\omega_n t} (1 + \omega_n t) \right] u(t)$$

$$q = \frac{1}{2} \left[ \sqrt{\frac{p_1}{p_2}} + \sqrt{\frac{p_2}{p_1}} \right] \sqrt{\frac{1}{1+A_0/k}} \quad \checkmark$$

$$\checkmark q = 1 \Rightarrow \left[ \frac{1}{2} \sqrt{\frac{1}{1+A_0/k}} \right]^2 = 1$$

$$\frac{p_1 + p_2 + 2}{p_2 p_1} = 4 \left( 1 + \frac{A_0}{k} \right)$$

$$\frac{p_2 + 2}{p_1} \approx 4 \frac{A_0}{k} + 4 \Rightarrow$$

$$\frac{p_2}{p_1} \approx \frac{4A_0}{k} + 2$$

$$\frac{p_2}{p_1} \approx \frac{4A_0}{k}$$


$$p_2 = \frac{4A_0 p_1}{k} \quad \checkmark$$

$$\text{if } p_1 \ll p_2 \Rightarrow \frac{p_1}{p_2} \ll \frac{p_2}{p_1}$$

$$\frac{p_2}{p_1} \approx 4 \left( 1 + \frac{A_0}{k} \right) q^2 - 2$$

$$\approx \left( \frac{4A_0}{k} q^2 + 2 \right) \quad \checkmark$$
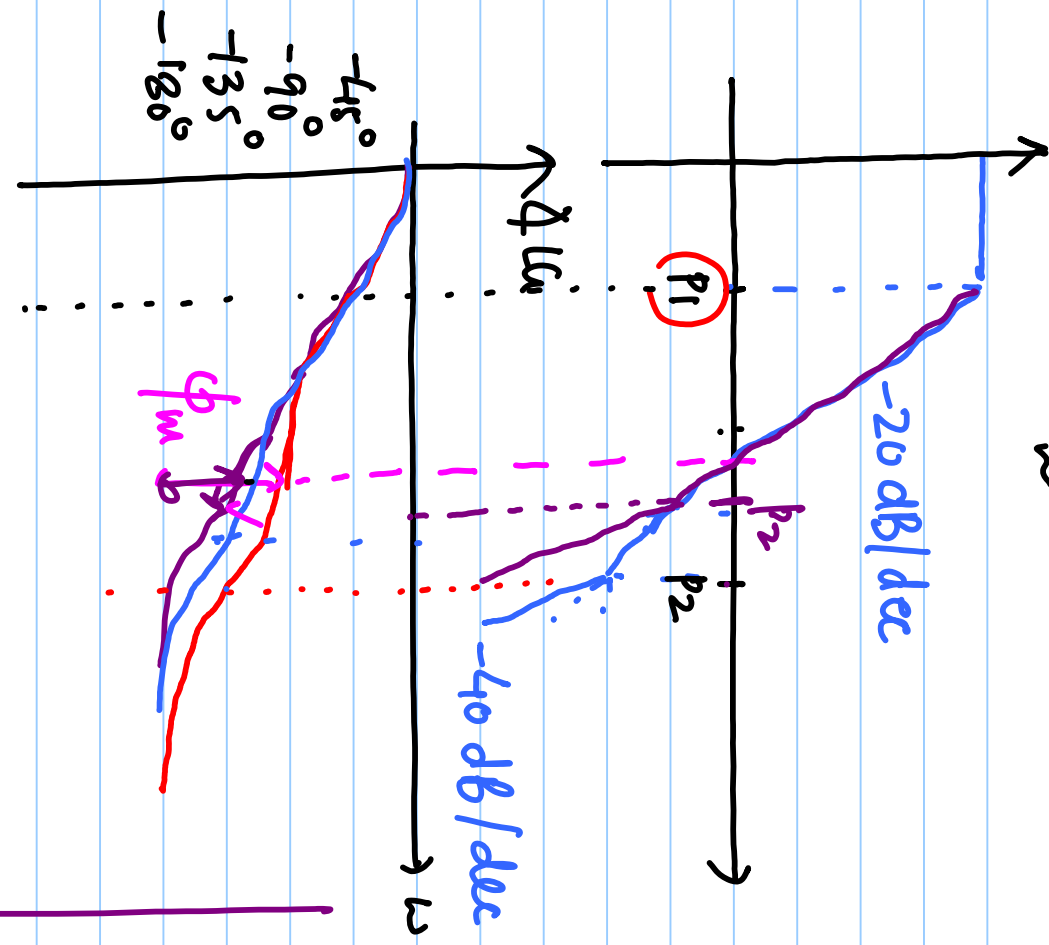
$$L_u = \frac{A_0}{K} \frac{1}{(1+s/p_1)} \frac{1}{(1+s/p_2)}$$



if  $\frac{p_2}{p_1} \gg 1$

$$|L_u(j\omega)| = 1$$


$$\frac{A_0}{K} \frac{1}{\sqrt{1+\frac{\omega^2}{p_1^2}}} \times \frac{1}{\sqrt{1+\frac{\omega^2}{p_2^2}}} = 1$$

$$\Rightarrow \frac{A_0}{K} \frac{1}{\omega_n} \times \frac{1}{1} = 1$$

$$\omega_n = \frac{A_0 p_1}{K}$$

$$\angle L_u = -\tan^{-1}\left(\frac{\omega}{p_1}\right) - \tan^{-1}\left(\frac{\omega}{p_2}\right)$$
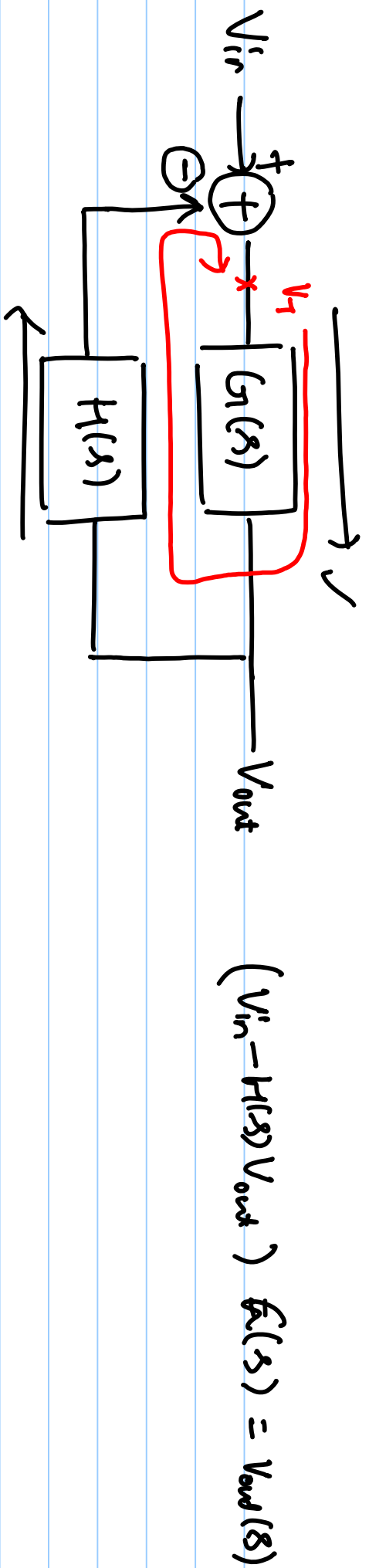
$$\phi_m = \angle L_u(\omega_n) - (-180^\circ) = 180^\circ - \tan^{-1}\left(\frac{\omega_n}{p_1}\right) - \tan^{-1}\left(\frac{\omega_n}{p_2}\right)$$



$$L_u = G_1(s) H(s)$$

$$\frac{V_o}{V_{in}} = \frac{G_1(s)}{1 + G_1(s)H(s)} = \frac{G_1(s) \cdot H(s)}{1 + G_1(s)H(s)} \times \frac{1}{H(s)}$$

$$\frac{V_o}{V_{in}} = \frac{1}{H(s)} \frac{L_u}{1 + L_u}$$

$$\phi_m = 180^\circ - \tan^{-1} \left( \frac{\omega_c}{p_1} \right) - \tan^{-1} \left( \frac{\omega_c}{p_2} \right)$$

$$\omega_c = \frac{A_o p_1}{K}, \quad p_2 = 4 \frac{A_o}{K} p_1 = 4 \omega_c$$

$$\begin{aligned} \phi_m &= 180^\circ - \tan^{-1} \left( \frac{A_o}{K} \right) - \tan^{-1} \left( \frac{1}{4} \right) \\ &= 180^\circ - 90^\circ - 14^\circ = 76^\circ \end{aligned}$$