
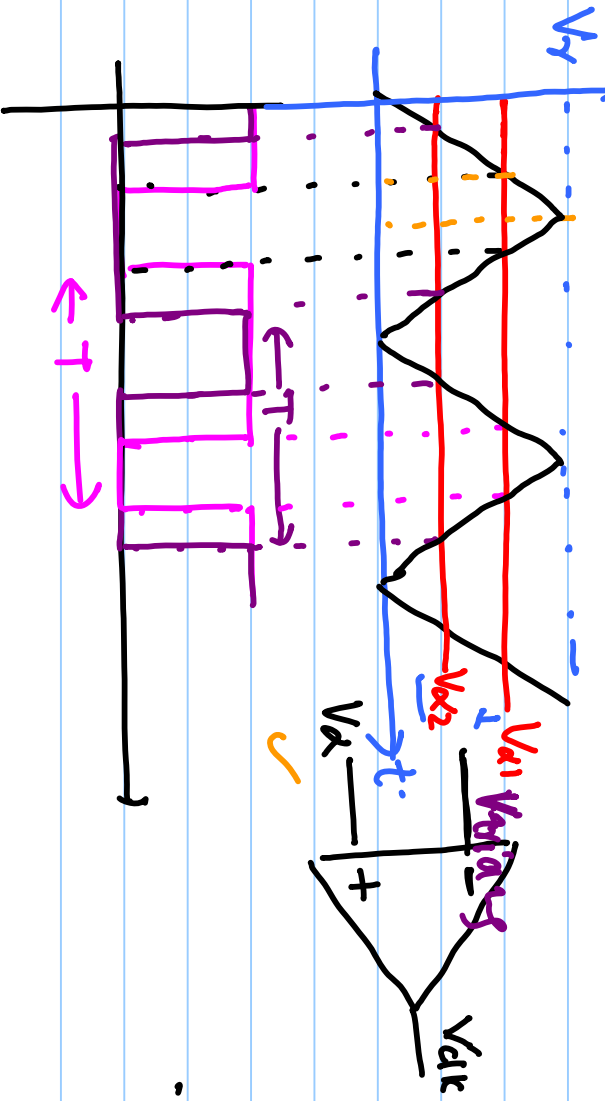


Lecture # 241

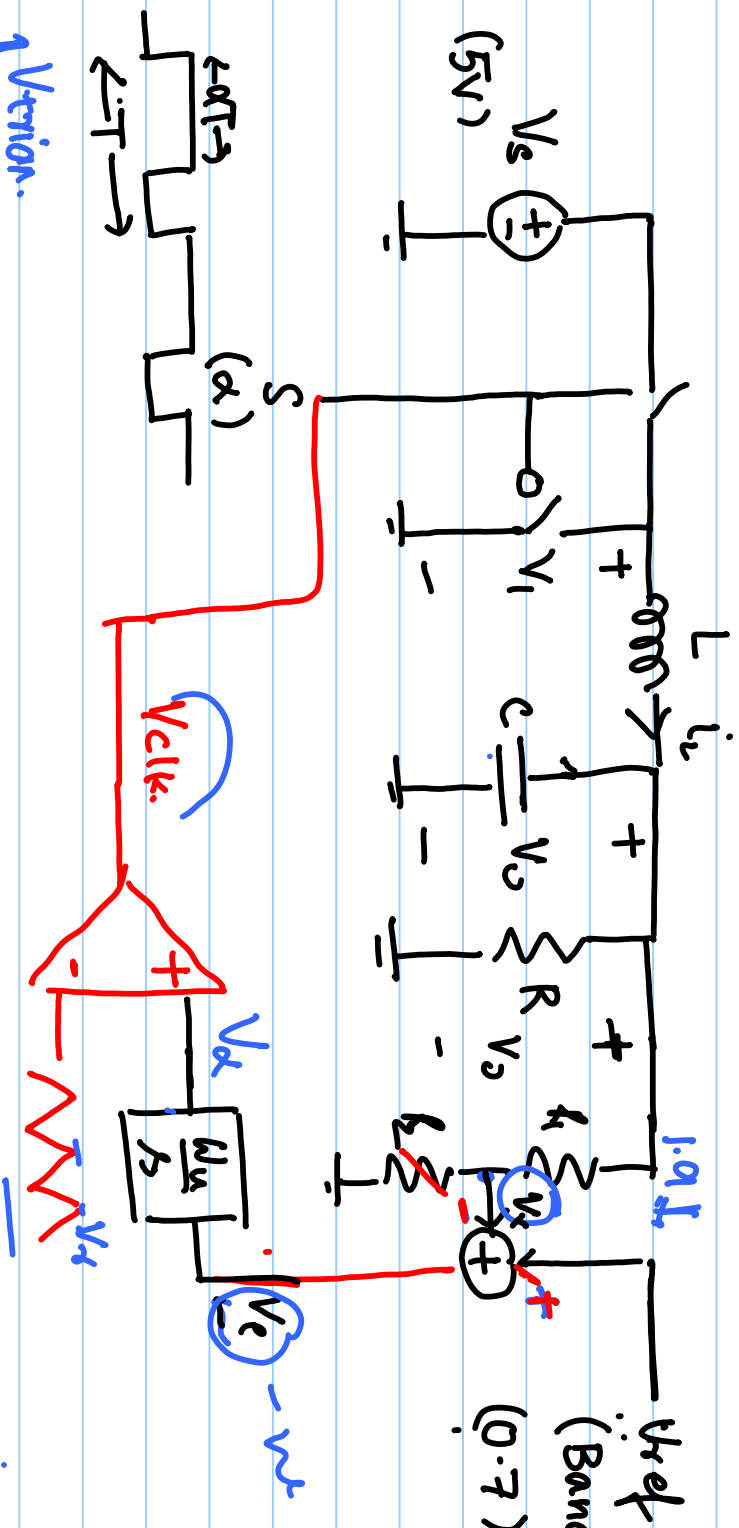



$$\frac{R_2}{R_2 + R_1} \cdot 1.8 = 0.7$$

$$V_0 = 1.8V$$

$$\alpha \frac{I}{2} = \frac{V_A}{\{V_T / (kT)\}} = \frac{V_A}{2V_T} \cdot T$$

$$\alpha = \frac{V_{AV}}{V_T}$$
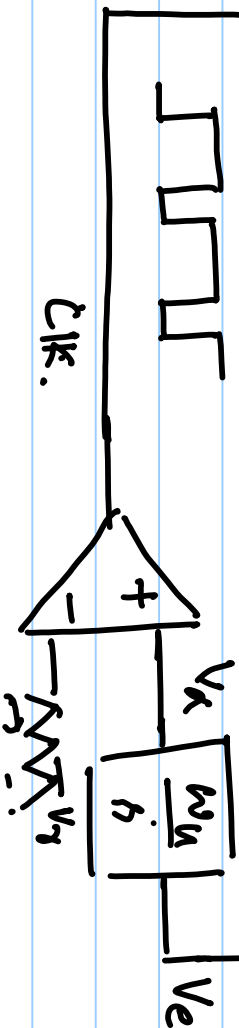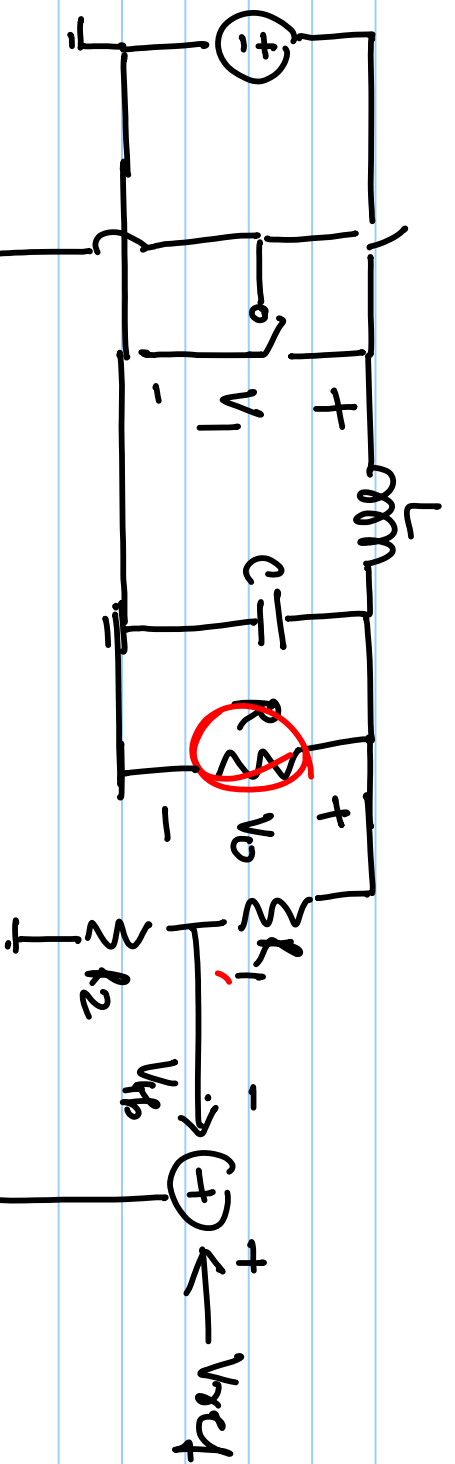
$$1.8 = \alpha V_{PD} = \alpha \times 5$$



$$\frac{V_0}{V_1} = \frac{1}{\frac{R_L^2}{\mu_p^2} + \frac{R_L}{\mu_p \alpha_p} + 1} \quad , \quad \frac{V_x}{V_e} = \frac{\alpha_p}{\beta} \quad , \quad \alpha = \frac{V_x}{V_e} \quad ,$$

