
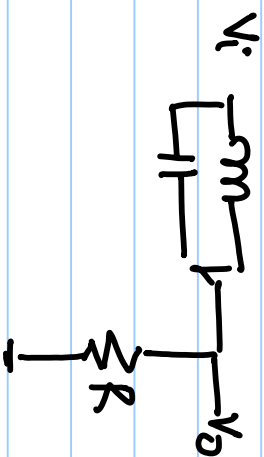
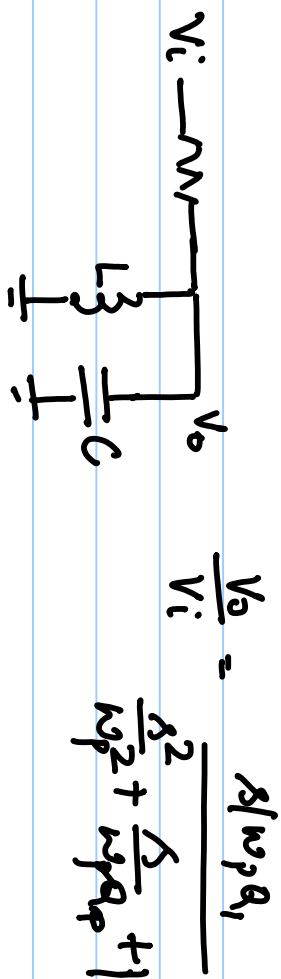
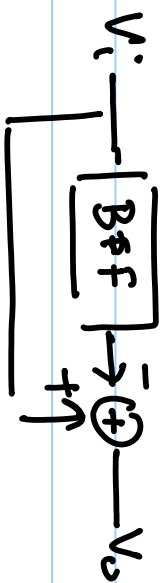


# Lecture # 33

## Band Reject Filter (BRF)

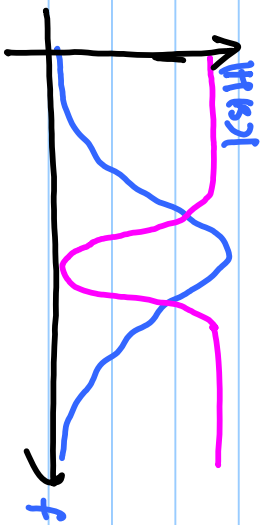

$$\frac{V_o}{V_i} = \frac{1 + \frac{s^2}{\omega_p^2}}{1 + \frac{s}{\omega_p Q} + \frac{s^2}{\omega_p^2}}$$

$$V_o \left( \frac{1}{s^2} + \frac{1}{s \omega_p Q} + \frac{1}{\omega_p^2} \right) = V_i \left( \frac{1}{s^2} + \frac{1}{\omega_p^2} \right)$$


$$\left\{ (V_o - V_i) \frac{1}{s} + \frac{V_o \omega_p}{\omega_p Q} \right\} \frac{1}{s} + V_o = V_i$$

# Active RC Filters

1. Opamp
2. Resistor
3. Capacitor


$$\frac{R_2}{R_1} \cdot \frac{1}{RC}$$

## Gm-C Filters

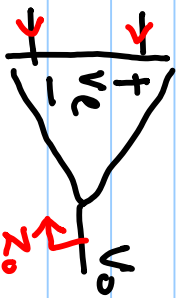

$$\frac{V_o}{V_c} = \frac{A}{(1+s/k\omega_p)}$$


$$Z_0 = 0$$

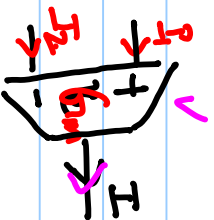


$$I = G_m V_c$$

$$I_1 = I_2 = 0$$




$$Z_0 = \infty$$

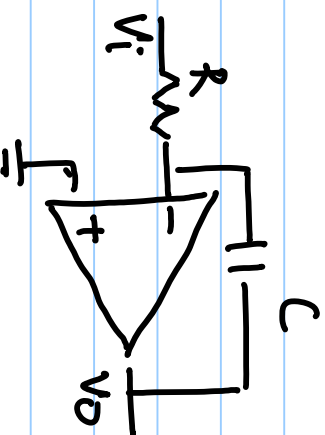

$$\frac{V_o}{V_i} = \frac{-1}{sRC}$$

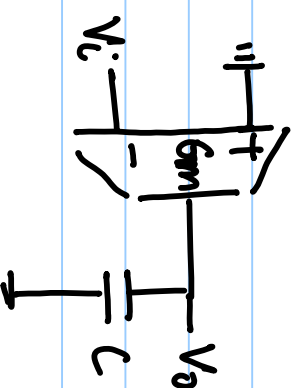

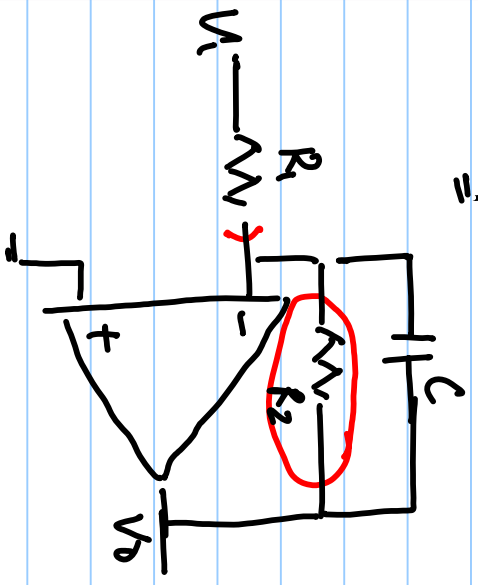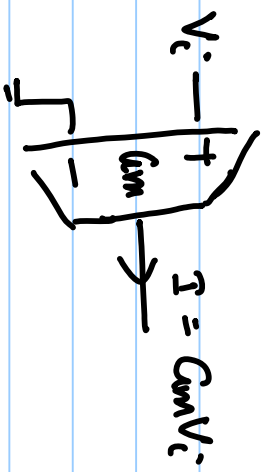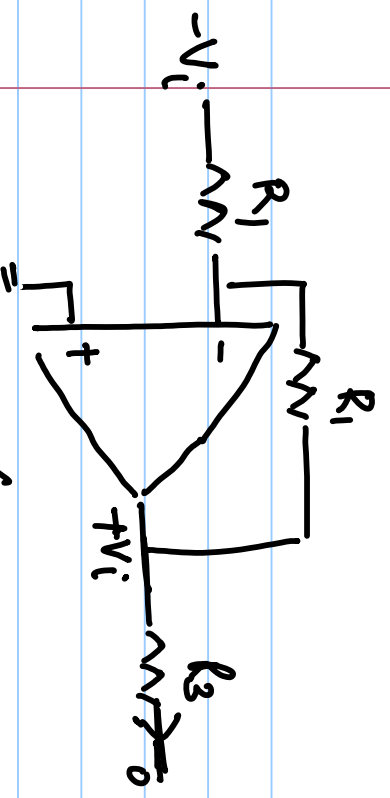
$$\frac{V_o}{V_i} = -G_m \times \frac{1}{sC} = \frac{-1}{s(C/G_m)}$$



$$\frac{V_o}{V_i} = \frac{-R_2/R_1}{(1 + R_2/R_3)}$$
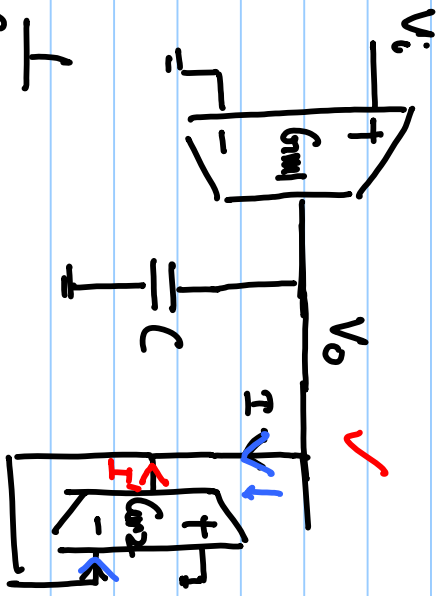
$$\frac{V_o}{V_i} = G_{m1} \left( \frac{1}{R_1} \parallel \frac{1}{G_{m2}} \right)$$






$$I' = -G_{m2} \cdot V_o$$

$$I = G_{m2} V_o$$

$$\frac{V_o}{I} = \frac{1}{G_{m2}}$$


$$\frac{V_i}{R_1}$$

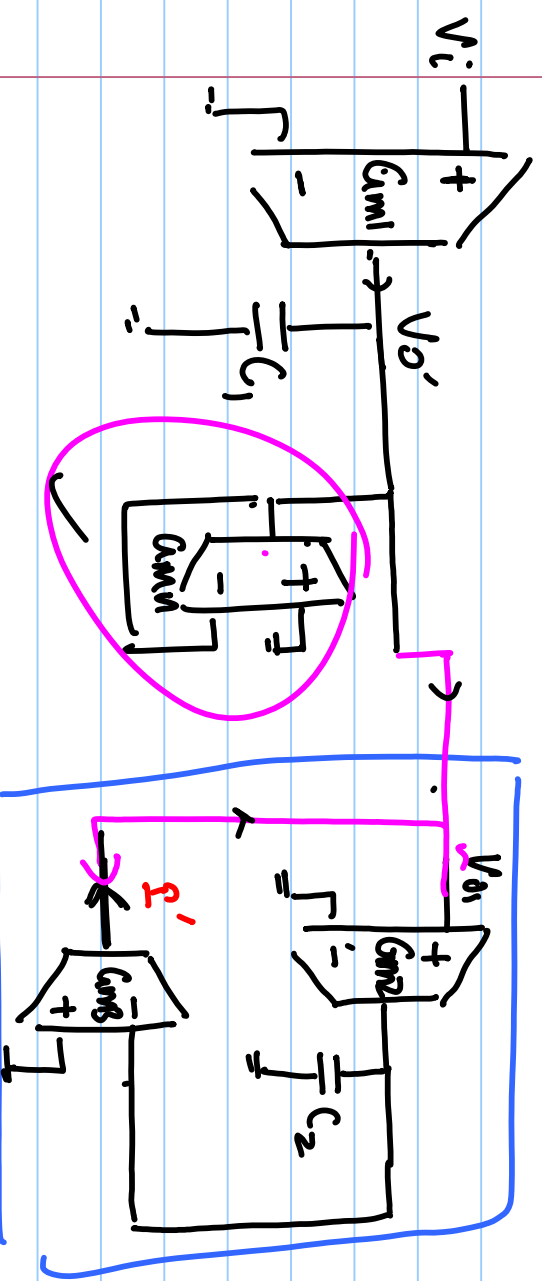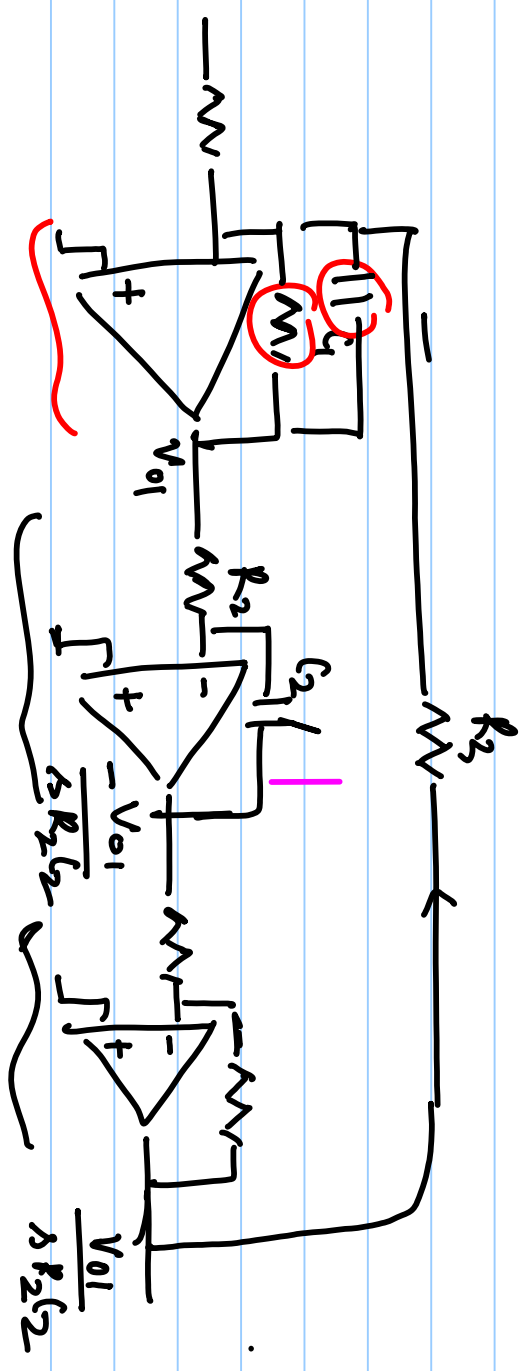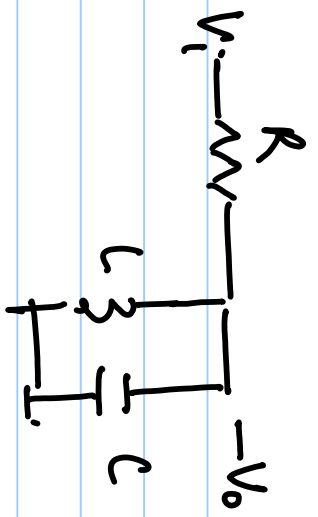


$$\frac{G_{m2} \cdot V_{o1}}{s C_2}$$

$$\tau' = - \frac{G_{m3} \cdot G_{m2} \cdot V_{o1}}{s C_2}$$
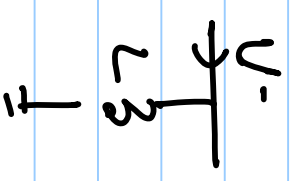
$$V_o = G_{m1} \cdot V_i \left( \frac{1}{R_{C1}} \parallel \frac{1}{G_{m2}} \parallel \frac{\beta C_2}{G_{m3} R_{C3}} \right)$$




$$I = \frac{V_o}{R_L}$$

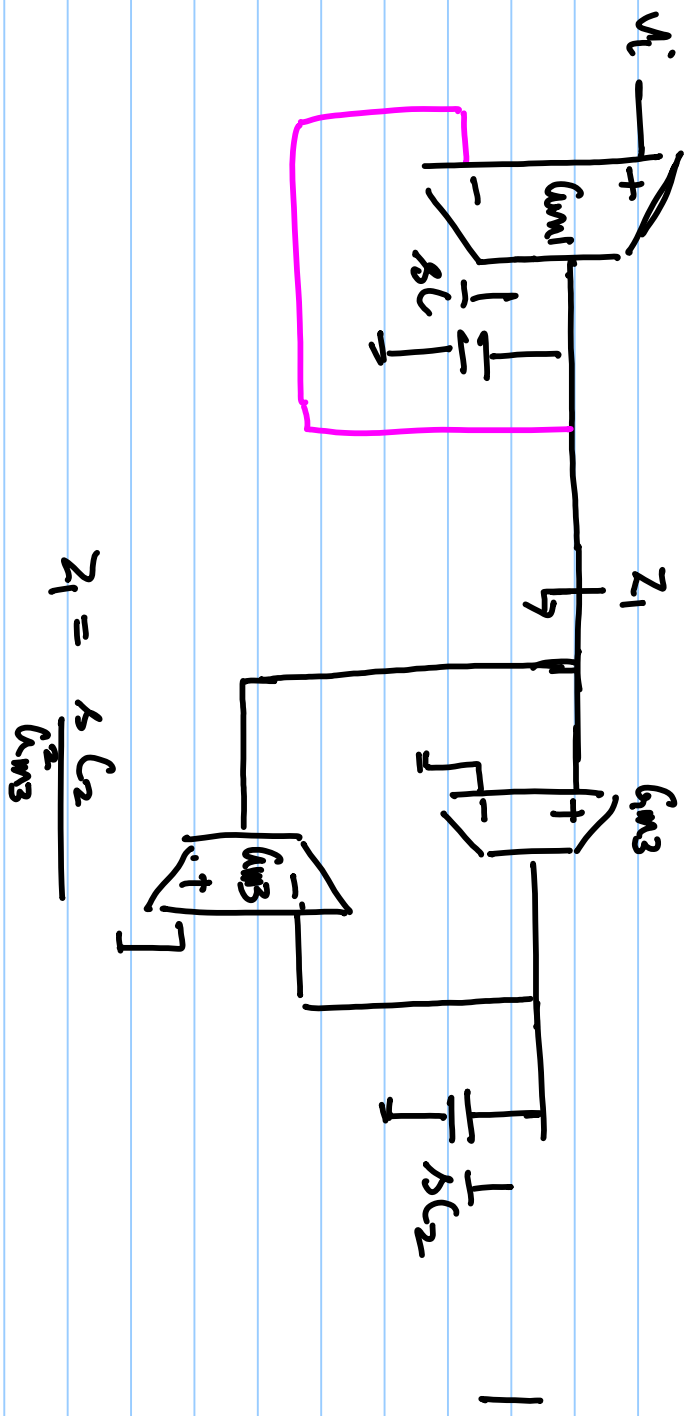


$$(V_i - V_o) g_{m1} = \frac{V_o}{1/sC_1} + \frac{V_o}{\frac{sC_2}{g_{m2}}}$$
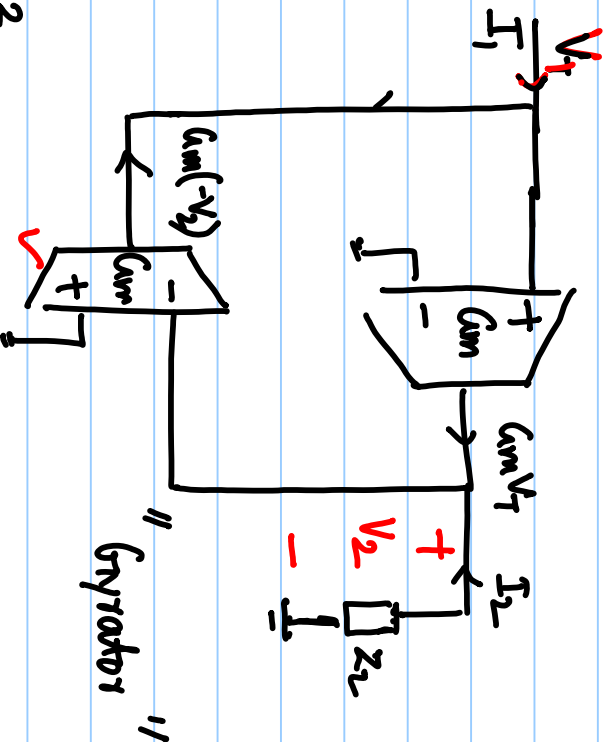
$$V_i \cdot g_{m1} = \frac{V_o}{1/sC_1} + \frac{V_o}{\frac{sC_2}{g_{m2}}} + g_{m2} V_o$$




$$I_T = g_{m1}^2 V_T \cdot Z_L$$
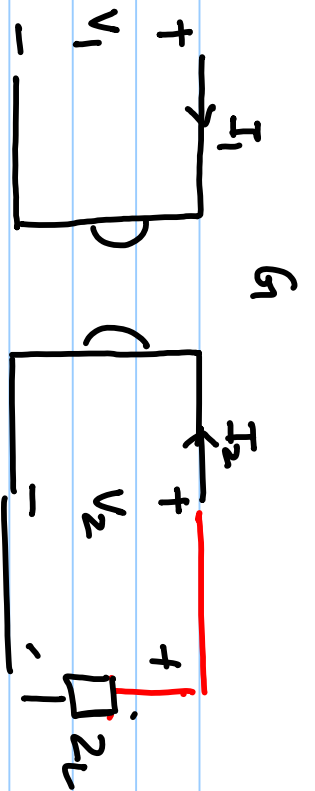
$$\frac{V_T}{I_T} = \frac{1}{g_{m1}^2 Z_L}$$




$$I_1 = r_G V_2, \quad I_2 = -G V_1$$
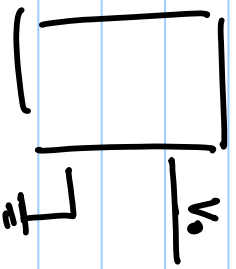
$$Z_{in} = \frac{V_1}{I_1} = \frac{V_1}{G V_2} = \frac{V_1}{G(-I_2 Z_L)} = \frac{V_1}{G(G V_1) Z_L} = \frac{1}{G^2 Z_L}$$



—  $V_1$

—  $V_2$

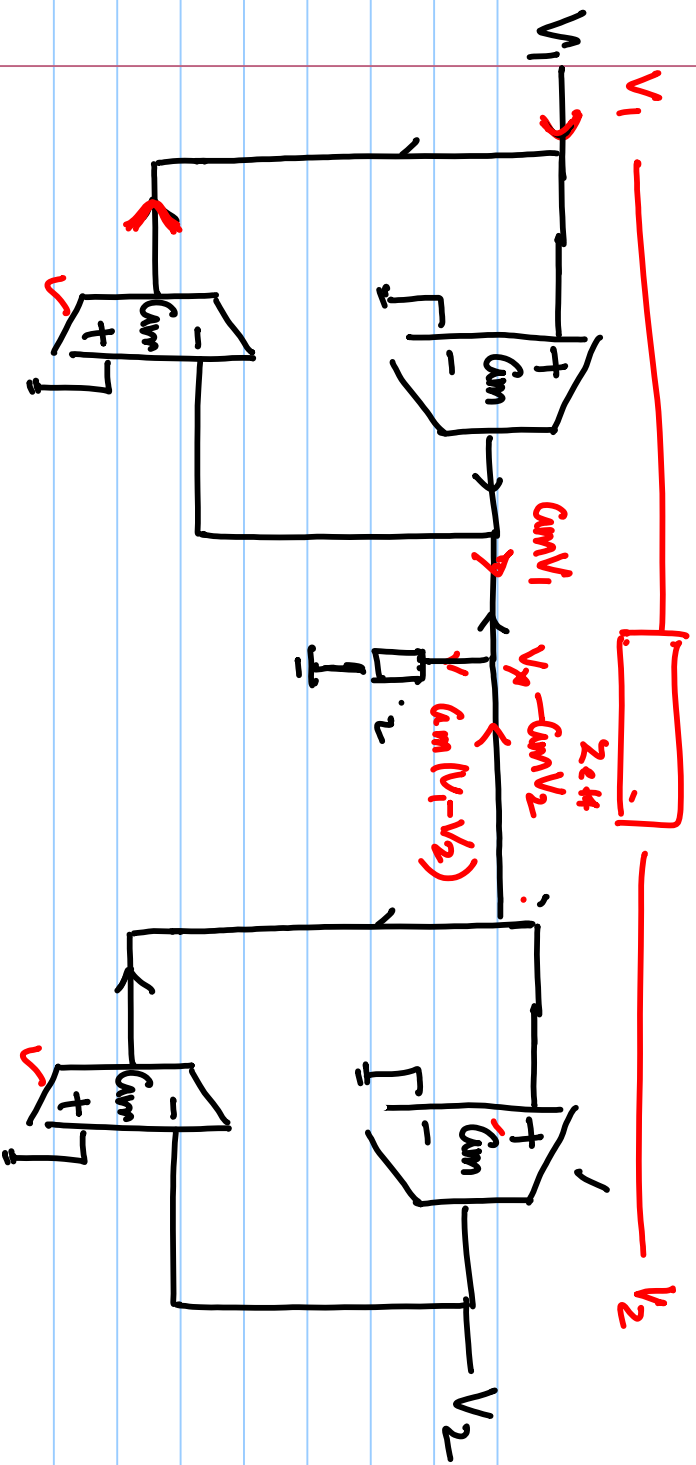

$$V_x = g_m (V_1 - V_2) Z_L$$

$$I = -g_m^2 (V_1 - V_2) Z_L$$