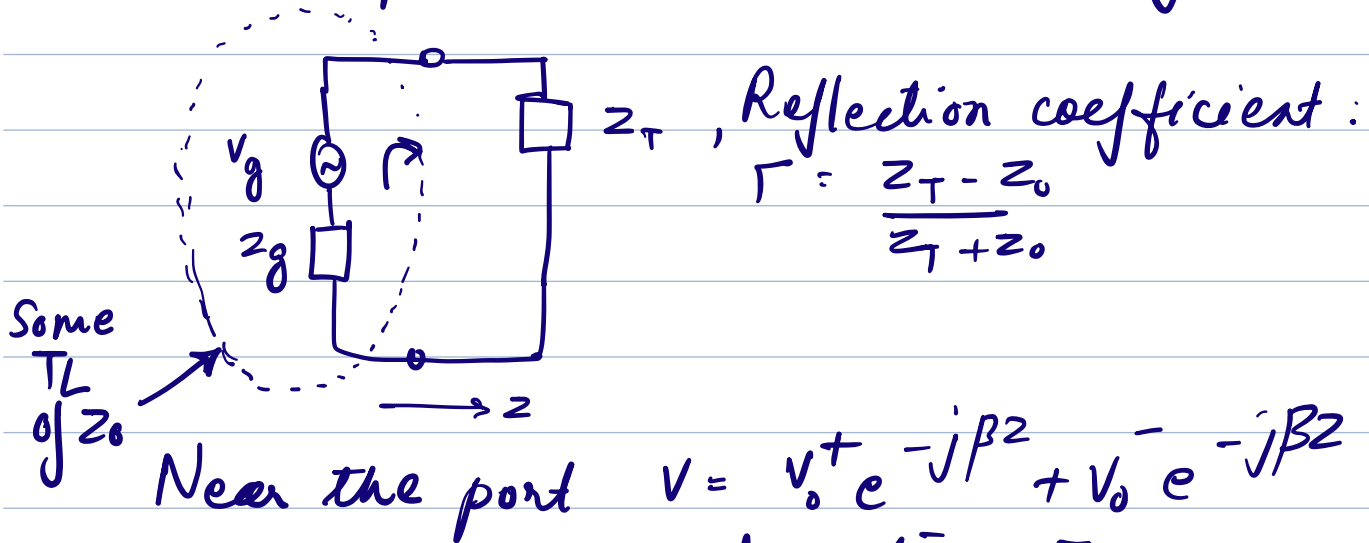


Microwave Network Theory

Lumped circuit equivalent of T_x art:



Near the port

$$V = V_0^+ e^{-j\beta z} + V_0^- e^{-j\beta z}$$

and $\frac{V_0^-}{V_0^+} = \Gamma$.


Rewrite as:

$$\therefore V_0^- = \Gamma V_0^+ \leftarrow \begin{array}{l} \text{incident} \\ \downarrow \\ \text{given the symbol 'a'} \end{array}$$

reflected \downarrow given the symbol 'b'


This is a simple 1-port network $b = S a$
 S is called the scattering matrix, also called S -parameters.

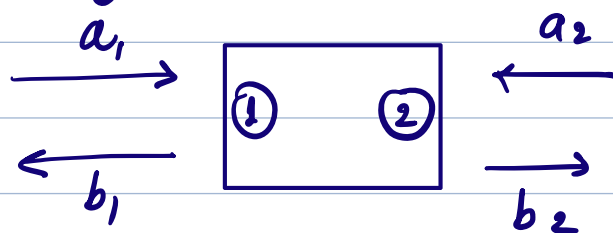↳ This can be generalized to 2 parameters



$$\therefore \begin{pmatrix} b_1 \\ b_2 \end{pmatrix} = \begin{pmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{pmatrix} \begin{pmatrix} a_1 \\ a_2 \end{pmatrix}$$

or generalized to N-ports

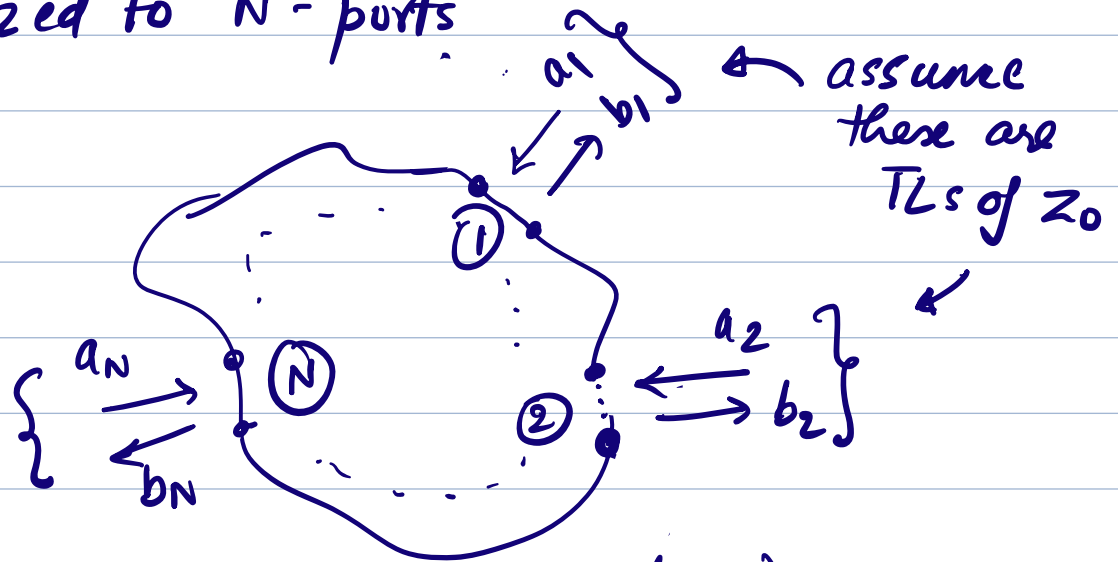

Similarly giving
$$\begin{pmatrix} b_1 \\ \vdots \\ b_N \end{pmatrix} = S \begin{pmatrix} a_1 \\ \vdots \\ a_N \end{pmatrix}$$


So
$$S_{ij} = \left. \frac{b_i}{a_j} \right|_{a_k=0, k \neq j}$$

Means what? ① Excite port j ONLY with a_j

② Measure b_i out of port i.

③ Make sure other ports have $a_k = 0$, i.e. no power from other ports leaks in. How to do this? Put matched loads at these ports.

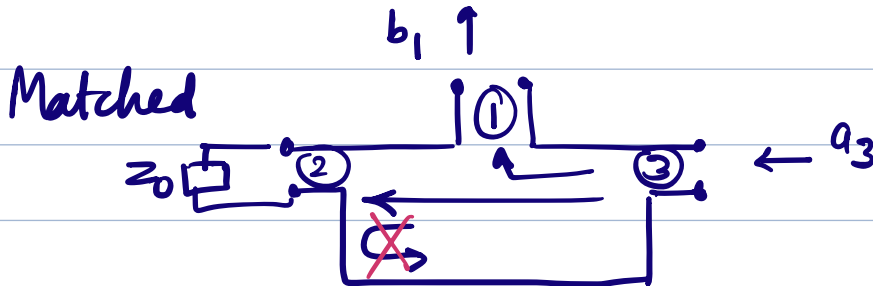eg. I want to measure S_{13} (3 port network)



$$S_{13} = \frac{b_1}{a_3}$$

3 properties of S-params w/o proof.


① For a reciprocal network (no nonlinear, active devices etc, same condns as the Lorentz reciprocity thm), $S = S^T$

② For a lossless network S is a unitary matrix, i.e. $SS^H = I$. (identity).
 $\Rightarrow \sum_j S_{ij} S_{kj}^* = \delta_{ik}$.

③ Recall that a, b are incident reflected voltages e.g. $a_n = V_n^+$, $b_n = V_n^-$. So the port voltages will be $V_n = V_n^+ + V_n^-$ ($x=0$ is taken to be at the port). Similarly the port current will be $I_n = I_n^+ - I_n^-$
 $I_n = \frac{1}{Z_0} (V_n^+ - V_n^-) = \frac{a_n - b_n}{Z_0}$ ↗ Zmatrix

$V_n = a_n + b_n$. Other matrices: $V = Z I$, $I = Y V$
— x —

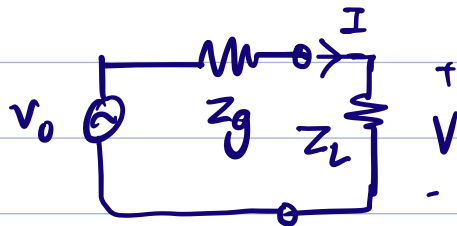The above discussion holds true when Z_0 is lossless and there is a TL connected at each port. e.g.



Here there is no voltage wave or TL (i.e. no Z_0). So, a generalization is: power waves. They can be applied to the above case as well as to regular TL cases.

To get the intuition consider a regular port

with voltage V & current I & a TL of z_0 .

$$V = V_0^+ + V_0^-, \quad I = (V_0^+ - V_0^-) / z_0$$

$$\Rightarrow \text{Power, } P_L = \frac{1}{2} \operatorname{Re}(VI^*) = \frac{1}{2z_0} \operatorname{Re} \left[|V_0^+|^2 - |V_0^-|^2 - \underbrace{V_0^+ V_0^{-*} + V_0^+ V_0^{-*}}_{\text{purely imag.}} \right]$$

$$P_L = \frac{1}{2z_0} \left[|V_0^+|^2 - |V_0^-|^2 \right]$$

Now switch to the ckt above and let's try to define power wave amplitudes like so

$$a = \frac{V + Z_R I}{2\sqrt{R_R}}, \quad b = \frac{V - Z_R^* I}{2\sqrt{R_R}}$$

where we define $Z_R = R_R + jX_R$ as a reference impedance.

Now, calculate V, I in terms of a, b ?

$$V = \frac{Z_R a + Z_R^* b}{\sqrt{R_R}}, \quad I = \frac{a - b}{\sqrt{R_R}}$$

$$\Rightarrow P_L = \frac{1}{2} \operatorname{Re}(VI^*) = \frac{1}{2} (|a|^2 - |b|^2)$$

Good, similar to our result above when $z_0 = 1$.

Last bit, what about ρ_{ref} between a & b ?

Use $V = Z_L I$ for the port

$$\frac{b}{a} = \Gamma_p = \frac{V - Z_R^* I}{V + Z_R I} = \frac{Z_L - Z_R^*}{Z_L + Z_R^*}$$

Same as our usual Γ when Z_R is real.


Since Z_R is arbitrary & in our hand, common choices are (i) $Z_R = Z_L^*$ or

(ii) $Z_R = Z_0$


chosen out of convenience depending on appl.

We can generalize this power wave defn for n -ports, choosing ref impedances for each port & get a matrix: $b = S_p a$.
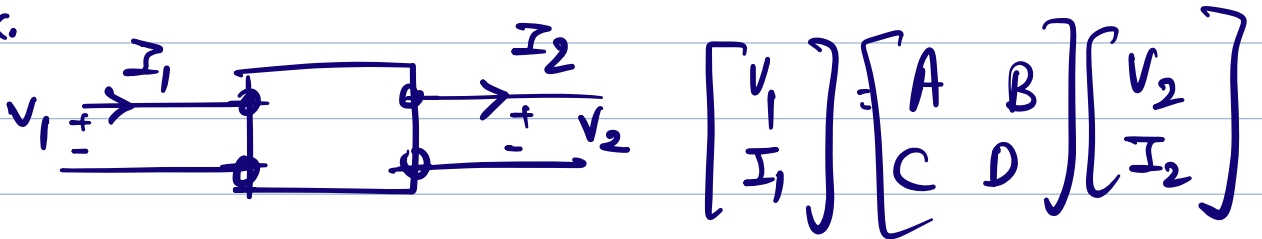
<Aside: another useful matrix is the ABCD matrix.



This is great for cascading!

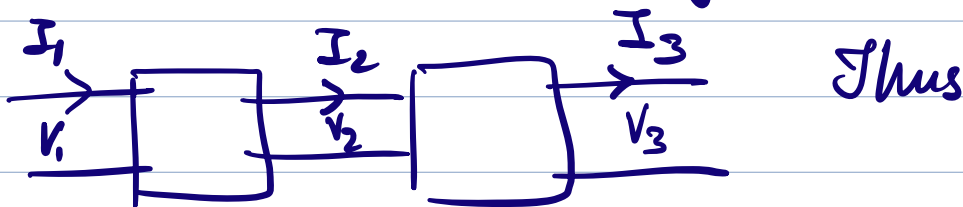


$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_3 \\ I_3 \end{bmatrix} \text{ \& so on.}$$

keep in mind the change in sign convention for I_2, I_3 .

end aside >

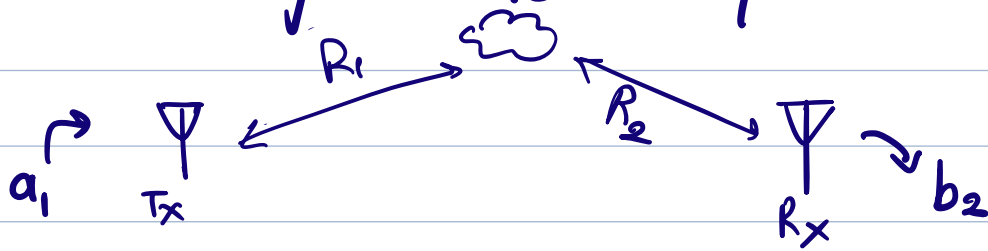
lets connect the S-parameters with EM fields in the case of 2 antenna systems.




$$\left[a_n = \frac{V_n + Z_0 I_n}{2\sqrt{R_0}}, b_n = \frac{V_n - Z_0^* I_n}{2\sqrt{R_0}} \quad \text{Recal} \right]$$

Logical flow: $a_1 \rightarrow \text{obj} \rightarrow b_2, S_{21} = \frac{b_2}{a_1}$

In more detail:

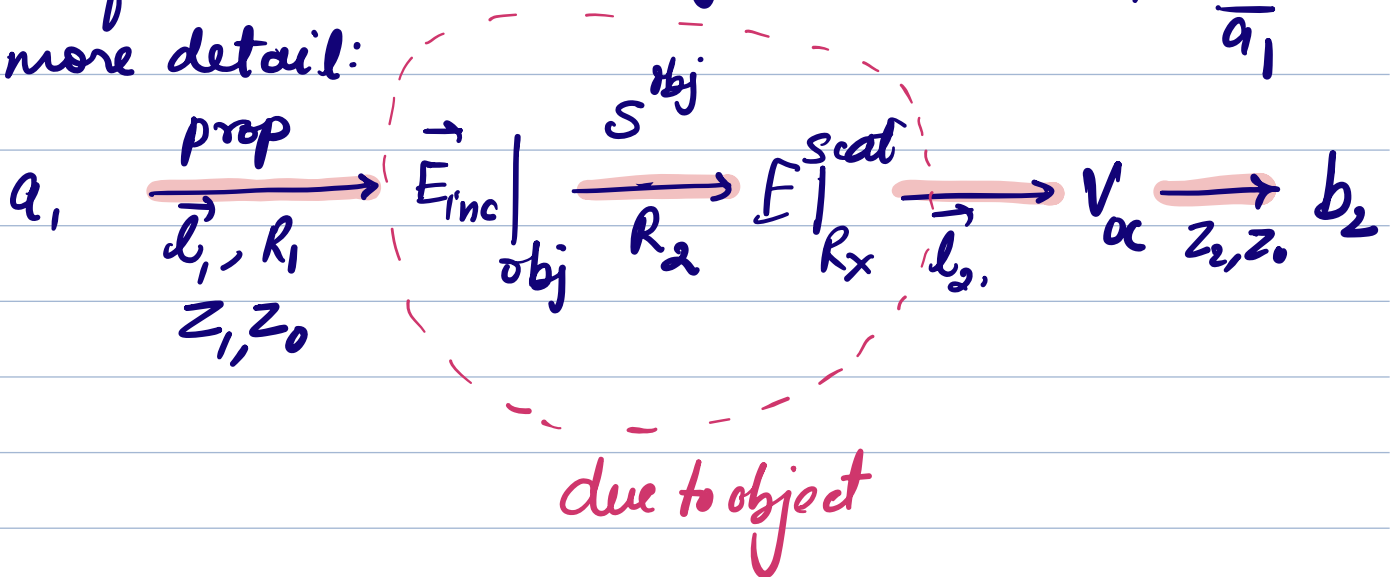

① At the t_x post:

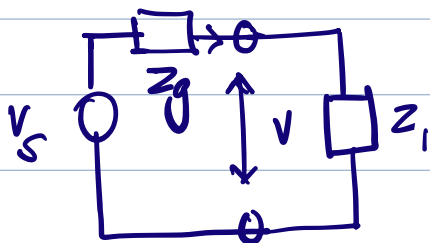

Assume a ref imp Z_0
(need not be real, need not be a TL).

$$a_1 = \frac{V_1 + Z_0 I_1}{2\sqrt{R_0}} = \frac{Z_L I_1 + Z_0 I_1}{2\sqrt{R_0}} = \frac{(Z_L + Z_0) I_1}{2\sqrt{R_0}} \quad \text{①}$$

② Field emitted by the antenna, landing on the object (farfield approx).

$$\vec{E}^{inc}(R_1) = j \frac{\eta k}{4\pi R_1} e^{-jkR_1} I_1 \vec{l}_1$$

effective vector length of ant

e.g. $\sin\theta \hat{\theta}$ for Hertz dipole

Let's make it more general: Instead of just \vec{l}_1 , let's

write it as $\begin{bmatrix} l_1^{co} \\ l_1^{xp} \end{bmatrix}$

$\begin{matrix} \rightarrow \text{co-pol} \\ \rightarrow \text{x-pol} \end{matrix}$

e.g. antenna generates both $\hat{\theta}$ & $\hat{\phi}$.

So $\vec{E}^{inc} = \begin{bmatrix} E_i^{co} \\ E_i^{xp} \end{bmatrix} = j \frac{\eta k}{4\pi R_1} e^{-jkR_1} I_1 \begin{pmatrix} l_1^{co} \\ l_1^{xp} \end{pmatrix}$

②
2x1 vectors

③ How does the object react? we model it as a polarimetric scatterer:

$$\vec{E}^{scat} = \frac{e^{-jkR_2}}{R_2} [S^{obj}] \vec{E}^{inc} \Big|_{\text{at object}}$$

③
2x2 matrix.


We can put ② into ③.

$$\vec{E}^{scat} = j \frac{\eta}{4\pi} \frac{e^{-jk(R_1+R_2)}}{R_1 \cdot R_2} I_1 S^{obj} \begin{pmatrix} l_1^{co} \\ l_1^{xp} \end{pmatrix}$$

④

④ Now we have to convert this \vec{E}_{scat} into ' b_2 '.

Rx ant ckt?

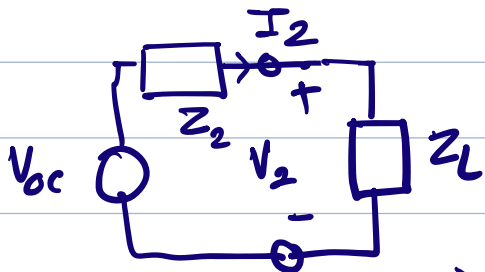

This $V_{oc} = \vec{E}_{scat} \cdot \vec{l}_2 = \vec{l}_2 \cdot \vec{E}_{scat}$

In our case: $V_{oc} = [\vec{l}_2^{co} \vec{l}_2^{xp}] \cdot \vec{E}_{scat}$

$$\begin{bmatrix} E_s^{co} \\ E_s^{xp} \end{bmatrix}$$

i.e. cross coupling can also contribute to V_{oc} .

$$\therefore V_{oc} = \frac{j\eta k}{4\pi} \frac{e^{-jk(R_1+R_2)}}{R_1 R_2} I_1 \underbrace{[\vec{l}_2^{co} \vec{l}_2^{xp}] S^{obj}}_{\vec{l}_2^T} \begin{bmatrix} \vec{l}_1^{co} \\ \vec{l}_1^{xp} \end{bmatrix} \leftarrow \vec{l}_1$$

purely fn of Tx / obj / Rx geometry.

from the ckt: $V_{oc} = I_2 Z_2 + V_2$ (KVL)

and $V_2 = Z_L I_2 \Rightarrow I_2 = V_{oc} / (Z_2 + Z_L)$

Recall the convention for a_n, b_n had port v & I to be going into the port.

$$\Rightarrow a_2 = \frac{V_2 + Z_0(-I_2)}{2\sqrt{R_0}} = \frac{(Z_L - Z_0) I_2}{2\sqrt{R_0}}$$

[going into the port]

$$b_2 = \frac{V_2 - Z_0^*(-I_2)}{2\sqrt{R_0}} = \frac{(Z_L + Z_0^*) V_{oc}}{2\sqrt{R_0} (Z_2 + Z_L)}$$

⑤ Finally:

$$T_{21} = \frac{b_2}{a_1} = \frac{(z_L + z_0^*) V_{oc}}{2\sqrt{R_0}(z_2 + z_L)} \times \frac{2\sqrt{R_0}}{(z_0 + z_1) I_1}$$

$$T_{21} = \frac{z_L + z_0^*}{(z_2 + z_L)(z_0 + z_1)} \frac{V_{oc}}{I_1} \quad \text{--- } (*)$$

$$I_2 = \frac{(z_L + z_0^*)}{(z_2 + z_L)(z_0 + z_1)} \frac{j\eta k}{4\pi} e^{-jk(R_1 + R_2)} \frac{z}{R_1 R_2}$$

Subtle distinction betn T_{21} & S_{21} .

$$S_{21} = b_2/a_1 \Big|_{a_2=0}$$

$a_2 = 0 \Rightarrow z_L = z_0$ (matched load). Then,

$$S_{21} = \frac{j\eta k}{2\pi} \frac{e^{-jk(R_1 + R_2)}}{R_1 R_2} \frac{\text{Re}(z_0)}{(z_1 + z_0)(z_2 + z_0)} \cdot \vec{d}_2^T S^{obj} \vec{d}_1$$

else

$$T_{21} = \frac{j\eta k}{4\pi} \frac{e^{-jk(R_1 + R_2)}}{R_1 R_2} \frac{(z_L + z_0^*)}{(z_1 + z_0)(z_2 + z_0)} \cdot \vec{d}_2^T S^{obj} \vec{d}_1$$