

Lecture 6: Laplace domain analysis

Lecturer: Dr. Vinita Vasudevan

Scribe: RSS Chaithanya

Laplace TransformKCL: $\sum i_k(t) = 0$ at any node, at any instant of time.

$$i_1(t) + i_2(t) + \dots + i_n(t) = 0$$

Taking Laplace transform (L.T) on both sides

$$\begin{aligned} \int_{0^-}^{\infty} \left(\sum_k i_k(t) \right) e^{-st} dt &= 0 \\ \Rightarrow \sum_k \left(\int_{0^-}^{\infty} i_k(t) e^{-st} dt \right) &= 0 \\ \Rightarrow \sum_k I_k(s) &= 0, \quad I_k(s) : \text{Ampere-sec units} \end{aligned}$$

Similarly KVL: $\sum_k v_k(t) = 0 \Rightarrow \sum_k V_k(s) = 0$, Units: Volt-sec. Consider all circuits to be LTI unless mentioned otherwise.**Resistor**

$$v(t) = Ri(t)$$

Taking L.T on both sides


$$V(s) = RI(s)$$

Capacitor

$$i(t) = C \frac{dv(t)}{dt}$$

Taking L.T on both sides


$$\begin{aligned} I(s) &= C \int_{0^-}^{\infty} \frac{dv(t)}{dt} e^{-st} dt \\ &= C \left(v(t) e^{-st} \Big|_{0^-}^{\infty} + s \int_{0^-}^{\infty} v(t) e^{-st} dt \right) \\ &= C \left(-v(0^-) + sV(s) \right) = -Cv(0^-) + sCV(s) \end{aligned}$$

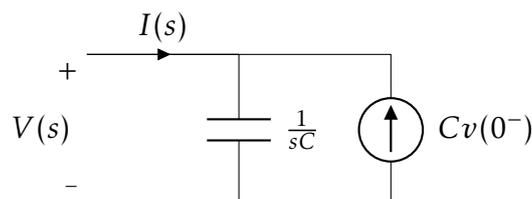where $v(0^-)$ is the initial voltage across the capacitor. sC is called admittance of capacitor.

Circuit representation 1

$$V(s) = \frac{1}{sC}I(s) + \frac{1}{s}v(0^-)$$

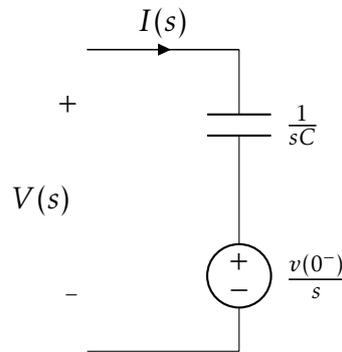$\frac{1}{sC}$ is called as impedance of capacitor = 1/admittance. Units of impedance is same as resistance.



Circuit representation 2

Both circuit representation 1 and 2 equivalent. Choose the one which is easy for analysis.


Inductor

$$v(t) = L \frac{di(t)}{dt}$$


taking L.T

$$V(s) = -Li(0^-) + sLI(s)$$
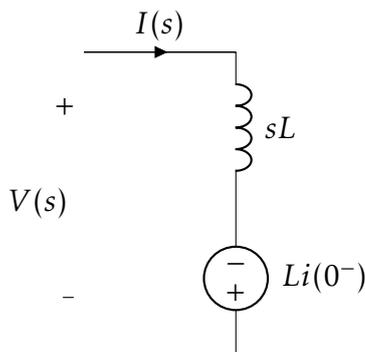
$$I(s) = \frac{1}{sL}V(s) + \frac{1}{s}i(0^-)$$



Circuit representation 1

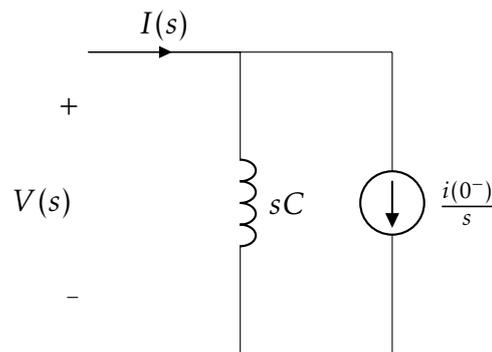

Circuit representation 2

sL is called as impedance of inductor.

Time domain vs Laplace domain

<u>Time domain</u>	<u>Laplace domain</u>
R 	R 
C 	$\frac{1}{sC}$ 
L 	sL 


Zero initial conditions

Under zero initial conditions

- For a resistor $V(s) = RI(s)$
- For a capacitor $V(s) = (1/sC)I(s)$
- For an inductor $V(s) = sLI(s)$


Impedance is represented with $Z(s)$ and admittance is represented with $Y(s) = \frac{1}{Z(s)}$. Impedance in Laplace domain behaves exactly like resistance in time domain.

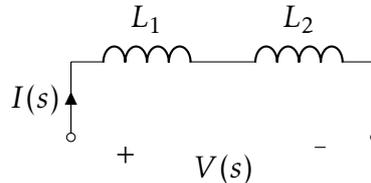Example 1. Impedance for the following circuit




$$\begin{aligned}
 V(s) &= I(s)(sL_1) + I(s)(sL_2) \\
 &= I(s)(sL_1 + sL_2) \\
 Z(s) &= sL_1 + sL_2
 \end{aligned}$$

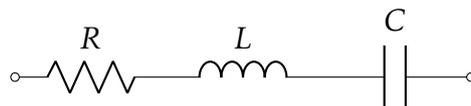Example 2. Impedance for the following circuit




$$Z(s) = R + 1/sC + sL$$

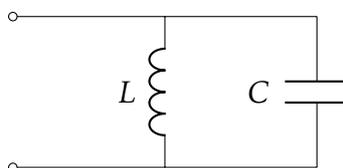Example 3. Admittance for the following circuit




$$Y(s) = sC + 1/sL$$

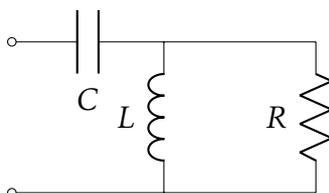Example 4. Admittance for the following circuit



$$Y(s) = \frac{sC(1/R + 1/sL)}{sC + 1/R + 1/sL}$$

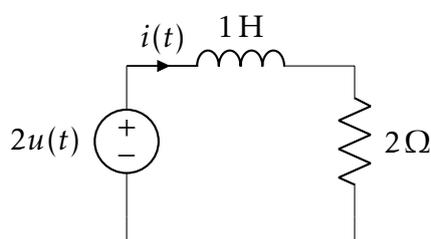
Example 5. Calculate $i(t)$ in the following circuit. Zero initial conditions.



$$\begin{aligned} V(s) &= L.T(2.u(t)) = 2/s \\ \Rightarrow 2/s &= I(s)(s + 2) \\ \Rightarrow I(s) &= \frac{2}{s(s + 2)} = \frac{1}{s} - \frac{1}{s + 2} \end{aligned}$$

$i(t) = L.T^{-1}(I(s)) = (1 - e^{-2t})u(t)$. As $t \rightarrow \infty$, $i(t) = 1$. At $t = 0^+$, $i(t) = 0$. For a DC, if the circuit is ON for a long time then the inductor is a short circuit.

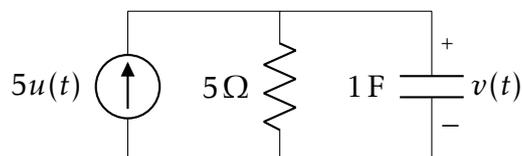Example 6. Calculate $v(t)$ in the following circuit



$$\begin{aligned} Y(s) &= 1/5 + s \\ I(s) &= Y(s) \cdot V(s) \\ \Rightarrow V(s) &= \frac{5}{s} \left(\frac{5}{1 + 5s} \right) = 25 \left(\frac{1}{s} - \frac{1}{s + 1/5} \right) \end{aligned}$$

$v(t) = L.T^{-1}(V(s)) = 25(1 - e^{-t/5})u(t)$. As $t \rightarrow \infty$, $v(t) = 25V \Rightarrow$ Capacitor is an open circuit.

In DC, Inductor is a short circuit and capacitor is an open circuit.